

Effective or RMS Values

- The idea of effective value arises from the need to measure the effectiveness of a voltage or current source in delivering power to a resistive load (recall:  $\text{Avg}\{\sin\} = 0$ )
- The effective value of a periodic signal is its root-mean-square (RMS) value
- The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current (similar for effective voltage)
  - see Sec E-4 in e-Notes Ch 8
  - (Coffee pot - car batteries example)

Average Power delivered/dissipated in a resistor,  $R$ , is

(General periodic excitation)  $P_R = I_{\text{rms}}^2 R \quad \text{W}$


For a sinusoidal excitation current  
 $i(t) = I_m \cos(\omega t + \phi) \text{ A}$

(Sinusoidal Excitation)  $P_R = \frac{1}{2} I_m^2 R \quad \text{W}$

# Maximum Average Power Transfer


Problem:

For an ac circuit:

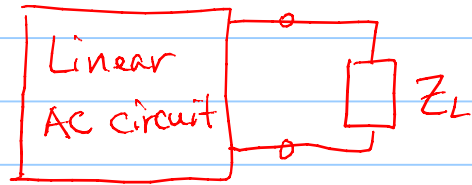

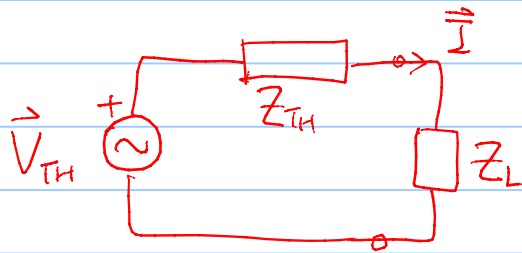- (a) What is  $Z_L$  for maximum average power transfer?
- (b) What is the maximum average power delivered to the load?

Soln: (a) Represent the linear ac circuit by its Thévenin equivalent:



In rectangular form:

$$Z_{TH} = R_{TH} + jX_{TH} \quad (1)$$

$$Z_L = R_L + jX_L \quad (2)$$

The current,  $\vec{I}$ , through the load is :

$$\vec{I} = \frac{\vec{V}_{TH}}{Z_{TH} + Z_L} = \frac{\vec{V}_{TH}}{(R_{TH} + jX_{TH}) + (R_L + jX_L)} \quad (3)$$

Recall, the average power delivered to the load is:

$$P = \frac{1}{2} |\vec{I}|^2 R_L \quad (4)$$

Substituting (3) into (4) yields :

$$P = \frac{1}{2} R_L \frac{|\vec{V}_{TH}|^2}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} \quad (5)$$

For maximum  $P$  w.r.t.  $R_L$  and  $X_L$ , set

$$\frac{\partial P}{\partial X_L} = 0 \text{ and } \frac{\partial P}{\partial R_L} = 0$$

From (5), we have

$$\frac{\partial P}{\partial X_L} = -|\vec{V}_{TH}|^2 R_L \frac{(X_{TH} + X_L)}{[(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2]^2} \quad (6)$$

and

$$\frac{\partial P}{\partial R_L} = |\vec{V}_{TH}|^2 \frac{[(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2 - 2R_L(R_{TH} + R_L)]}{2[(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2]^2} \quad (7)$$

Setting (6) to zero gives:

$$X_L = -X_{TH} \quad (8)$$

and setting (7) to zero gives:

$$R_L = \sqrt{R_{TH}^2 + (X_{TH} + X_L)^2} \quad (9)$$

Combining (8) and (9) leads to the conclusion that, for maximum average transfer,  $Z_L$  must be selected such that

$$Z_L = R_L + jX_L \quad (10)$$

where

$$R_L = R_{TH} \quad (11)$$

and

$$X_L = -X_{TH} \quad (12)$$

Thus, for max. avg. pwr. transfer in sinusoidal steady state,

$$Z_L = R_L + jX_L = R_{TH} - jX_{TH} \quad (13)$$

$$Z_L = Z_{TH}^*$$

( $\therefore$  Load = complex conjugate of the Thevenin impedance  $Z_{TH}$   
= conjugate-matched to  $Z_{TH}$ )

(b) Substituting (11) and (12) into (5) gives the maximum average power

(i) delivered to the load

(ii) absorbed by the load

as:

$$P_{\max} = \frac{|\vec{V}_{\text{TH}}|^2}{8 R_{\text{TH}}} \quad (\text{W}) \quad (14)$$

Note:

- Conjugate matching applies only when the source is fixed and the load is adjustable (e.g., in power-limited communication systems).
- Conjugate matching does not apply to electrical power systems due to different power transfer constraints. (See Ch. 16)
- See Example 8-28 in text
- Work Exercise 8-20 in text