

Name: Solution Key

ECE 202 Circuits and Systems II

Fall 2007

Examination III

November 16, 2007

Problem	Points	Score
1	21	21
2	19	19
3	30	30
4	30	30
Total:	100	100

V.G.!!

Notes:

- 1) You have 50 minutes to complete this examination.
- 2) This exam has 4 problems and a total of 8 pages.
- 3) Please write your name in the space provided on each page.
- 4) Please draw a box around to clearly indicate each answer.
- 5) You must show your work to receive full or partial credit (where applicable).
- 6) Some questions may have little or no partial credit.
- 7) *Please, please, please check and double-check your work and calculations!!*
- 8) All answers must have units where appropriate, and be in proper engineering notation.

1. [2] pts] Answer the following questions:

- (a) [1] For a series RLC bandpass filter, which element would you adjust, and by how much, to double the bandwidth without changing the center frequency?

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = \frac{R}{L}$$

Double R to $2R$ changes B
but not ω_0

- (b) [1] For a system with transfer function $H(s) = \frac{s+1}{(s-2)(s+3)}$, determine whether this system is stable or not. Explain why.

The pole at $s=2$ is in the Right-half plane, thus causing the system to be unstable

- (c) [2] pts] For the transfer function $H(s) = \frac{2}{(s+3)(s+1)}$, what is the Laplace domain response, $G(s)$, of the circuit due to a time-domain unit step input?

$$G(s) = \frac{H(s)}{s} = \frac{2}{s(s+3)(s+1)}$$

2. [19 pts] Write a PSPICE netlist file that maybe used to generate the Bode plots for the circuit in Figure 1. Let $C = 20 \text{ nF}$, $R = 500$, and $L = 50 \text{ uH}$. Scan your frequency from 10 kHz to 10 MHz, with 20 steps per decade.

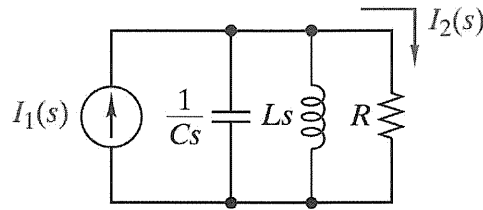



Figure 1 Circuit for Problem 2

5 pts

```


1 *Exam III Problem 2
8 I1 0 1 AC 1Aac DC 0Aac optional
1 C1 1 0 20n
1 L1 1 0 50u
1 R1 1 0 500
1 .probe
5 .ac dec 20 10000 10000000
1 .end
    
```

or [1k 10meg]

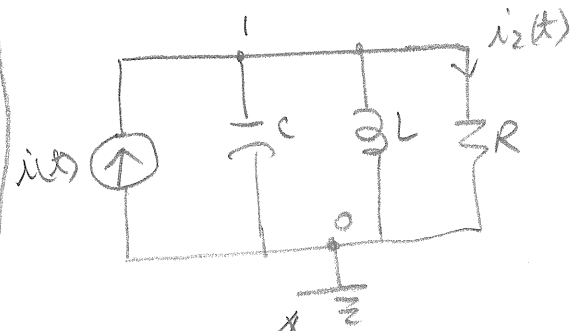

add grounding to diagram

for current source

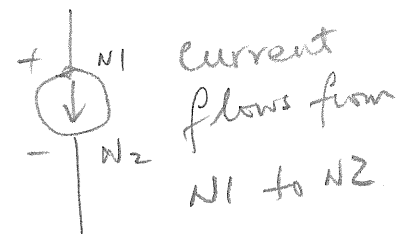

3. [30 pts] For the waveform in Figure 1:

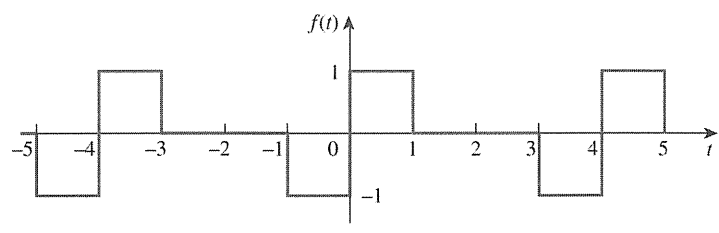


Figure 2 Waveform for Problem 3

(a) [6 pts] Identify all symmetry properties for $f(t)$. Briefly explain your reasoning.

$$f(t) = -f(-t) \Rightarrow \text{odd symmetry.}$$

(3) (3)

(b) [24 pts] Find the Fourier series representation of $f(t)$ in closed form (i.e., the expression of $f(t)$ should use the summation symbol and contain no " a_n "s, " b_n "s or ellipsis "...").

Odd symmetry:

$$a_0 = 0 \quad (4)$$

$$a_n = 0 \quad (4)$$

$$T = 4$$

$$b_n = \frac{2}{T} \left[\int_{-1}^0 (-1) \sin\left(\frac{2\pi n}{T} t\right) dt + \int_0^1 (1) \sin\left(\frac{2\pi n}{T} t\right) dt \right]$$

$$= \frac{2}{T} \left[\frac{T}{2\pi n} \cos\left(\frac{2\pi n}{T} t\right) \Big|_{-1}^0 - \frac{T}{2\pi n} \cos\left(\frac{2\pi n}{T} t\right) \Big|_0^1 \right]$$

3. Cont'd (work space)

$$= \frac{1}{\pi n} \left[1 - \cos\left(\frac{2\pi n}{T} \cdot -1\right) - \cos\left(\frac{2\pi n}{T} \cdot 1\right) + 1 \right]$$

$$b_n = \frac{2}{\pi n} \left[1 - \cos\left(\frac{2\pi n}{T}\right) \right]$$

Recall $T=4$

$$\therefore b_n = \frac{2}{\pi n} \left[1 - \cos\left(\frac{\pi n}{2}\right) \right]$$

$$\therefore f(t) = \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \left[1 - \cos\left(\frac{\pi n}{2}\right) \right] \sin\left(\frac{\pi n}{2} t\right)$$

4. [30 pts] For the RC circuit in Figure 3(b), the response $v_o(t)$ is due to the excitation shown in Figure 3(a).
 (Note: there are 3 parts to this problem; part (c) is on the next page)


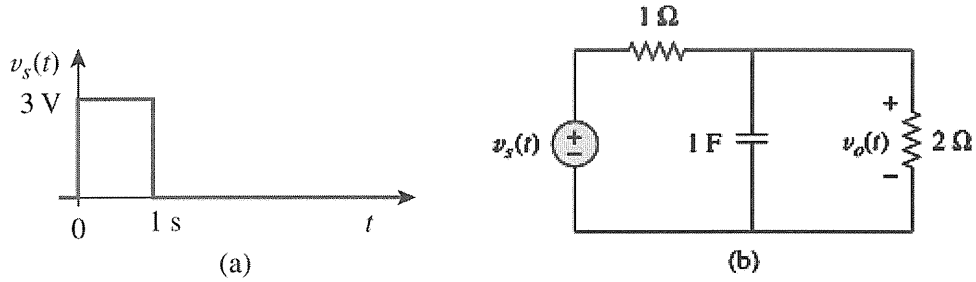


Figure 3 Input signal (a) and circuit diagram (b) for Problem 4

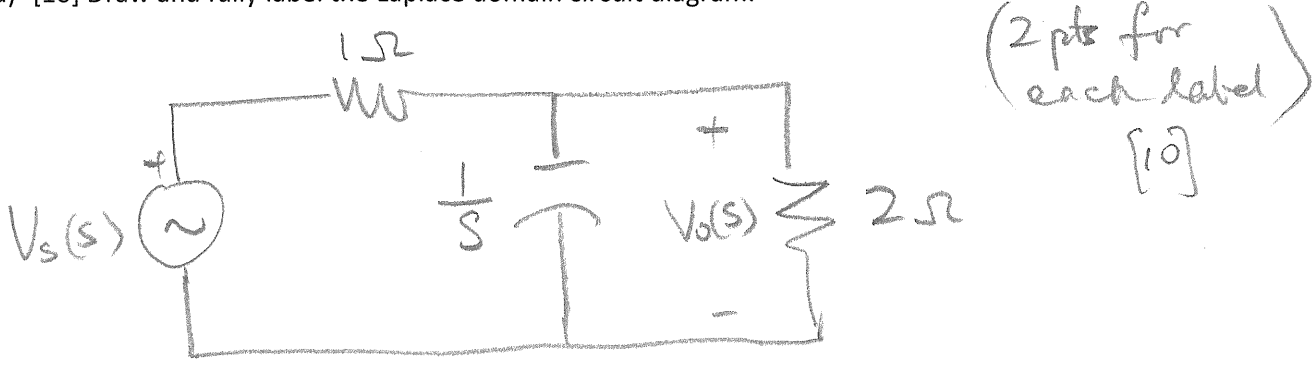(a) [10] Draw and fully label the Laplace domain circuit diagram.



(b) [4] What is the impulse response of this circuit in time domain?

impulse response $\Rightarrow h(t) \leftrightarrow H(s) = \text{transfer fn.}$
 let $Z = \frac{1/s // 2}{2 + 1/s} = \frac{\frac{2}{s}}{2 + 1/s} = \frac{1}{s + 1/2}$

$$V_o(s) = V_s(s) \cdot \frac{Z}{Z + 1} = \frac{\frac{1}{s + 1/2}}{\frac{1}{s + 1/2} + 1} = \frac{1}{1 + s + 1/2} = \frac{1}{s + 3/2}$$

$$\therefore H(s) = \frac{V_o(s)}{V_s(s)} = \frac{1}{s + 1.5}$$

Thus $h(t) = e^{-1.5t} u(t)$
 or $h(t) = e^{-\frac{3}{2}t} u(t)$ (4)


(c) [This part is on the next page]

4 (c) [16 pts] Using convolution integrals, find the zero-state response for $t > 0$.Zero-state response = $v_o(t)$

$$v_o(t) = v_s(t) * h(t)$$

$$v_s(t) = 3[u(t) - u(t-1)]$$

$$h(t) = e^{-\frac{3}{2}t} u(t)$$

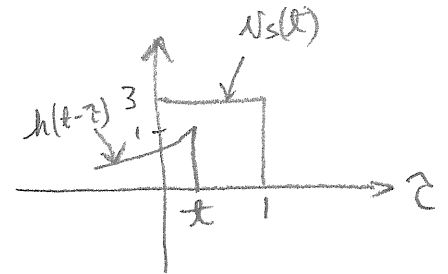for $0 \leq t < 1$

$$v_o(t) = \int_0^t 3 \cdot e^{-\frac{3}{2}(t-\tau)} d\tau$$

$$= 3 \cdot e^{-\frac{3}{2}t} \int_0^t e^{+\frac{3}{2}\tau} d\tau$$

$$= 3 \cdot e^{-\frac{3}{2}t} \left(\frac{2}{3}\right) \left[e^{\frac{3}{2}\tau} \right]_0^t$$

$$= 2e^{-\frac{3}{2}t} \left[e^{\frac{3}{2}t} - 1 \right] = 2 \left[1 - e^{-\frac{3}{2}t} \right]$$

 $0 \leq t < 1$ for $t > 1$

$$v_o(t) = \int_0^1 3 \cdot e^{-\frac{3}{2}(t-\tau)} d\tau$$

$$= 3e^{-\frac{3}{2}t} \left(\frac{2}{3}\right) \left[e^{\frac{3}{2}\tau} \right]_0^1 = 2e^{-\frac{3}{2}t} \left[e^{\frac{3}{2}} - 1 \right]$$

4. Cont'd (work space)

$$v_0(t) = \begin{cases} 2 \left[1 - e^{-\frac{3}{2}t} \right] & 0 \leq t < 1 \\ 2 e^{-\frac{3}{2}t} \left[e^{\frac{3}{2}} - 1 \right] & t > 1 \end{cases} \quad \text{Volts}$$

Optionally:

$$v_0(t) = 2 \left[1 - e^{-\frac{3}{2}t} \right] [u(t) - u(t-1)] + 2 e^{-\frac{3}{2}t} \left[e^{\frac{3}{2}} - 1 \right] u(t-1)$$

$$= 2 \left(1 - e^{-\frac{3}{2}t} \right) u(t) - 2 \left(1 - e^{-\frac{3}{2}t} \right) u(t-1)$$

$$+ 2 e^{-\frac{3}{2}t} e^{\frac{3}{2}} u(t-1) - 2 e^{-\frac{3}{2}t} u(t-1)$$

$$= 2 u(t) - 2 e^{-\frac{3}{2}t} u(t) - 2 u(t-1) + 2 e^{-\frac{3}{2}t} u(t-1)$$

$$+ 2 e^{-\frac{3}{2}(t-1)} u(t-1) - 2 e^{-\frac{3}{2}t} u(t-1)$$

$$v_0(t) = 2 \left[1 - e^{-\frac{3}{2}t} \right] u(t) - 2 \left[1 - e^{-\frac{3}{2}(t-1)} \right] u(t-1) \quad \text{V}$$

[16]