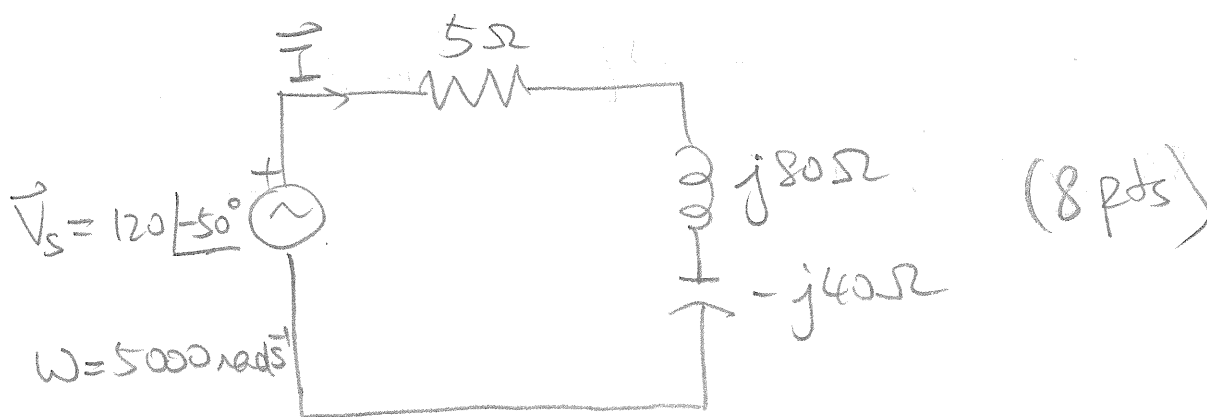


(a) In phasor domain:

$$v_s(t) = 120 \cos(5000t - 50^\circ) \leftrightarrow \vec{V}_s = 120 \angle -50^\circ \text{ V}$$

$$Z_L: j\omega L = j(5000)(16 \times 10^{-3}) = j80 \Omega$$

$$Z_C: \frac{1}{j\omega C} = \frac{1}{j(5000)(5 \times 10^{-6})} = -j40 \Omega$$



$$\begin{aligned} \text{(b)} \quad Z_{eq} &= 5 + j80 - j40 = 5 + j40 \Omega \quad (2 \text{ pts}) \\ &= 40.31 \angle 82.87^\circ \Omega \end{aligned}$$

$$\text{(c)} \quad \vec{I} = \frac{\vec{V}_s}{Z_{eq}} = \frac{120 \angle -50^\circ}{40 \angle 82.87^\circ} = 2.977 \angle -132.87^\circ \text{ A} \quad (2 \text{ pts})$$

$$\text{(d)} \quad i(t) = 2.977 \cos(5000t - 132.87^\circ) \text{ A} \quad (2 \text{ pts})$$

(e) The Equivalent Impedance is

$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C} \quad (2 \text{ pts})$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right) = R_{eq} + jX_{eq}$$

At resonance frequency, f_0 ,
the reactance $X_{eq} = 0$.

(2 pts)


thus, $\omega_0 L - \frac{1}{\omega_0 C} = 0$

and $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore \omega_0 = \frac{1}{\sqrt{(16 \times 10^{-3})(5 \times 10^{-6})}} = 3535.53 \text{ rad/s}$$

$$\therefore f_0 = \frac{\omega_0}{2\pi} = \underline{\underline{562.70 \text{ Hz}}} \quad (2 \text{ pts})$$

(P2)

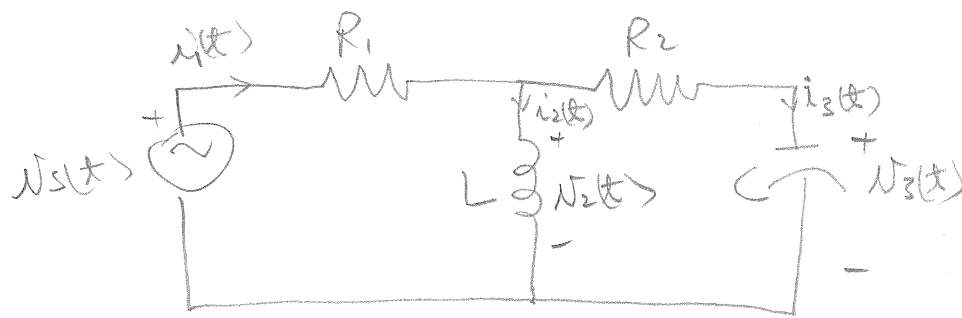

Convert to phasors:

$$\vec{V}_s = 24 \angle 60^\circ \text{ V}$$

$$Z_{R1} = 4 \Omega$$

$$Z_{R2} = 8 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{(1000)(250 \times 10^{-6})} = -j4 \Omega$$

$$Z_L = j\omega L = j(1000)(6 \times 10^{-3}) = j6 \Omega$$


$$v_s(t) = 24 \cos(1000t + 60^\circ) \text{ V}$$

$$R_1 = 4 \Omega$$

$$R_2 = 8 \Omega$$

$$C = 250 \mu\text{F}$$

$$L = 6 \text{ mH}$$

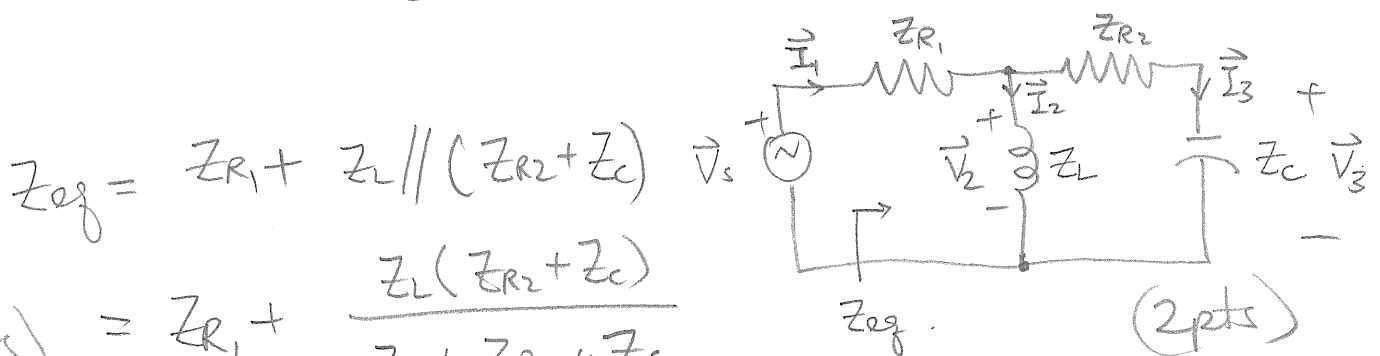

$$Z_{eq} = Z_{R1} + Z_L \parallel (Z_{R2} + Z_C)$$

$$= Z_{R1} + \frac{Z_L(Z_{R2} + Z_C)}{Z_L + Z_{R2} + Z_C}$$

$$= 4 + \frac{(j6)(8 - j4)}{j6 + 8 - j4} = 4 + \frac{24 + j48}{8 + j2}$$

$$= 4 + \frac{53.665 \angle 63.43^\circ}{8.246 \angle 14.04^\circ} = 4 + 6.508 \angle 49.40^\circ$$

$$= 4 + 4.235 + j4.941 = 8.235 + j4.941 \Omega$$

$$\boxed{Z_{eq} = 9.604 \angle 30.96^\circ \Omega} \quad (2 \text{ pts})$$

$$\vec{I}_1 = \frac{\vec{V}_s}{Z_{eq}} = \frac{24 \angle 60^\circ}{9.604 \angle 30.96^\circ} = 2.50 \angle 29.04^\circ \text{ A}$$

$$i_1(t) = 2.50 \cos(1000t + 29.04^\circ) \text{ A} \quad (4 \text{ pts})$$

Note that \vec{V}_2 may be obtained in two ways:
using KVL or voltage division

using KVL

$$\begin{aligned} \vec{V}_2 &= \vec{V}_s - \vec{I}_1 Z_{R_1} \quad (2 \text{ pts}) \\ &= 24 \angle 60^\circ - 10 \angle 29.06^\circ \\ &= 3.26 + j15.93 \\ \vec{V}_2 &= 16.26 \angle 78.43^\circ \text{ V} \end{aligned}$$

using voltage division

$$\begin{aligned} \vec{V}_2 &= \vec{V}_s \frac{Z_L \parallel (Z_{R_2} + Z_C)}{Z_{R_1} + Z_L \parallel (Z_{R_2} + Z_C)} \\ &= 24 \angle 60^\circ \left(\frac{6.508 \angle 49.40^\circ}{9.604 \angle 30.96^\circ} \right) \\ \vec{V}_2 &= 16.26 \angle 78.43^\circ \end{aligned}$$

$$\therefore v_2(t) = 16.26 \cos(1000t + 78.43^\circ) \text{ V} \quad (4 \text{ pts})$$

$$\vec{I}_2 = \frac{\vec{V}_2}{Z_L} = \frac{16.26 \angle 78.43^\circ}{6 \angle 90^\circ} = 2.71 \angle -11.57^\circ \text{ A}$$

$$\therefore i_2(t) = 2.71 \cos(1000t - 11.57^\circ) \text{ A} \quad (4 \text{ pts})$$

$$\begin{aligned} \vec{I}_3 &= \frac{\vec{V}_2}{Z_{R_2} + Z_C} = \frac{16.26 \angle 78.43^\circ}{8 - j4} = \frac{16.26 \angle 78.43^\circ}{8.944 \angle -26.57^\circ} \\ &= 1.818 \angle 105^\circ \text{ A} \end{aligned}$$

$$i_3(t) = 1.818 \cos(1000t + 105^\circ) \text{ A} \quad (4 \text{ pts})$$

Note that $\vec{I}_2 \neq \vec{I}_3$ could have been
obtained using current division.

5/9


Finally,

$$\begin{aligned}\vec{V}_3 &= \vec{I}_3 Z_c = 1.818 \angle 105^\circ (-j4) \\ &= 1.818 \angle 105^\circ (4 \angle -90^\circ)\end{aligned}$$

$$\vec{V}_3 = 7.27 \angle 15^\circ \text{ V}$$

$$\therefore v_3(t) = 7.27 \cos(1000t + 15^\circ) \text{ V} \quad (4 \text{ pts})$$

P3.

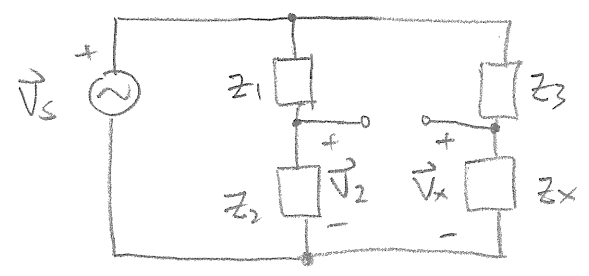

$Z_1 = 1 \text{ k}\Omega$

$Z_2 = 4.2 \text{ k}\Omega$

$f = 2 \text{ kHz}$

$\omega = 2\pi f = 4000\pi \text{ rad/s}^{-1}$

For a balanced bridge, the current through the ac meter is zero \rightarrow can replace the meter with an open circuit.

$$\vec{V}_2 = \vec{V}_s \frac{Z_2}{Z_1 + Z_2}$$
 the 1st branch (2pts)

And
$$\vec{V}_x = \vec{V}_s \frac{Z_x}{Z_x + Z_3}$$
 the 2nd branch (2pts)

Since
$$\vec{V}_2 = \vec{V}_x$$
 (for balanced bridge)

then
$$\frac{Z_2}{Z_1 + Z_2} = \frac{Z_x}{Z_x + Z_3}$$

$$Z_2 Z_x + Z_2 Z_3 = Z_x Z_1 + Z_x Z_2$$

$$Z_2 Z_3 = Z_x (Z_1 + Z_2 - Z_2)$$

$$\therefore Z_x = \frac{Z_2 Z_3}{Z_1} \quad \text{--- (1) (2pts)}$$

$$Z_3 = R_3 \parallel \frac{1}{j\omega C_3} = \frac{R_3}{R_3 + \frac{1}{j\omega C_3}}$$

$$Z_3 = \frac{R_3}{1 + j\omega R_3 C_3} \quad (2pts)$$

P3 (cont'd)

Given: $R_3 = 1.5 \text{ M}\Omega$
 $C_3 = 12 \text{ pF}$

Then

$$Z_3 = \frac{1.5 \times 10^6}{1 + j(4000\pi)(1.5 \times 10^6)(12 \times 10^{-12})} \Omega$$
$$= \frac{1.5 \times 10^6}{1 + j0.2262} = \frac{1.5 \times 10^6 \angle 0^\circ}{1.025 \angle 12.746^\circ}$$
$$= 1.463 \angle -12.746^\circ \text{ M}\Omega$$

$$Z_3 = 1.427 - j0.3228 \text{ M}\Omega \quad (2 \text{ pts})$$

sub into (1) we have

$$Z_x = \frac{(4.2 \times 10^3)}{(1 \times 10^3)} (1.463 \angle -12.746^\circ) \text{ M}\Omega$$

$$Z_x = 6.145 \angle -12.746^\circ \text{ M}\Omega$$

$$Z_x = 5.993 - j1.356 \text{ M}\Omega \quad (2 \text{ pts})$$

P.3 (a) For a series circuit implementation:

$$\text{Let } Z_x = R_x + jX_x = 5.993 - j1.356 \text{ M}\Omega$$

Since X_x is negative, we choose a capacitor

$$\therefore Z_x = R_x + \frac{j}{\omega C_x} = 5.993 - j1.356 \text{ M}\Omega \quad (2 \text{ pts})$$

$$\therefore \boxed{R_x = 5.993 \text{ M}\Omega}$$

↓ (2 pts)

P.3(a) cont'd

$$X_x = \frac{1}{\omega C_x} = 1.356 \text{ M}\Omega$$

$$\therefore C_x = \frac{1}{(1.356 \times 10^6)(4000\pi)}$$


$$\boxed{C_x = 58.69 \text{ pF}}$$

$$Z_x = \left\{ \begin{array}{l} R_x \\ Z_x \end{array} \right\} \quad (1 \text{ pt})$$

P3(b) For a parallel circuit implementation:

$$\text{Let } Z_x = (5.993 - j1.356) \text{ M}\Omega$$
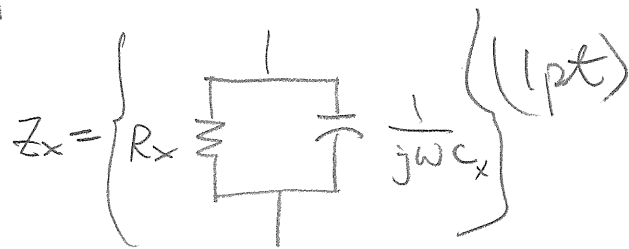
$$= R_x \parallel \frac{1}{j\omega C_x}$$



$$Z_x = \frac{R_x}{1 + j\omega R_x C_x} \quad (2 \text{ pts})$$

$$= \frac{R_x}{1 + j\omega R_x C_x} \cdot \frac{1 - j\omega R_x C_x}{1 - j\omega R_x C_x} = \frac{R_x (1 - j\omega R_x C_x)}{1 + \omega^2 R_x^2 C_x^2}$$

$$= \frac{R_x}{1 + \omega^2 R_x^2 C_x^2} - j \frac{\omega R_x^2 C_x}{1 + \omega^2 R_x^2 C_x^2} \quad (2 \text{ pts})$$

Comparing terms we have

$$\frac{R_x}{1 + \omega^2 R_x^2 C_x^2} = 5.993 \times 10^6 \quad \text{--- (2) (1 pt)}$$

and

$$\frac{\omega R_x^2 C_x}{1 + \omega^2 R_x^2 C_x^2} = 1.356 \times 10^6 \quad \text{--- (3) (1 pt)}$$



P3(b) (Cont'd)

9/9

Dividing (3) by (2) yields:

$$\frac{\text{Eq (3)}}{\text{Eq (2)}} = \frac{\omega R_x^2 C_x}{R_x} = \omega R_x C_x = \frac{1.356 \times 10^6}{5.993 \times 10^6}$$

$$\therefore (4000\pi) R_x C_x = 0.22626$$

$$R_x C_x = 1.80 \times 10^{-5}$$

$$\therefore R_x = \frac{1.80 \times 10^{-5}}{C_x} \quad \text{--- (4)}$$

Sub (4) into (2) yields:

$$\frac{1.80 \times 10^{-5}}{C_x} = 5.993 \times 10^6$$
$$1 + (4000\pi)^2 \left(\frac{1.80 \times 10^{-5}}{C_x} \right)^2 C_x^2$$

$$\frac{1.80 \times 10^{-5}}{C_x} \cdot \frac{1}{1.05} = 5.993 \times 10^6$$
$$C_x = \frac{1.80 \times 10^{-5}}{(1.05)(5.993 \times 10^6)}$$

$$\boxed{\therefore C_x = 2.86 \text{ pF}} \quad (2 \text{ pts})$$

Sub C_x into (4) yields:

$$R_x = \frac{1.80 \times 10^{-5}}{2.86 \times 10^{-12}} \Omega$$

$$\boxed{\therefore R_x = 6.30 \text{ M}\Omega}$$

(2 pts)