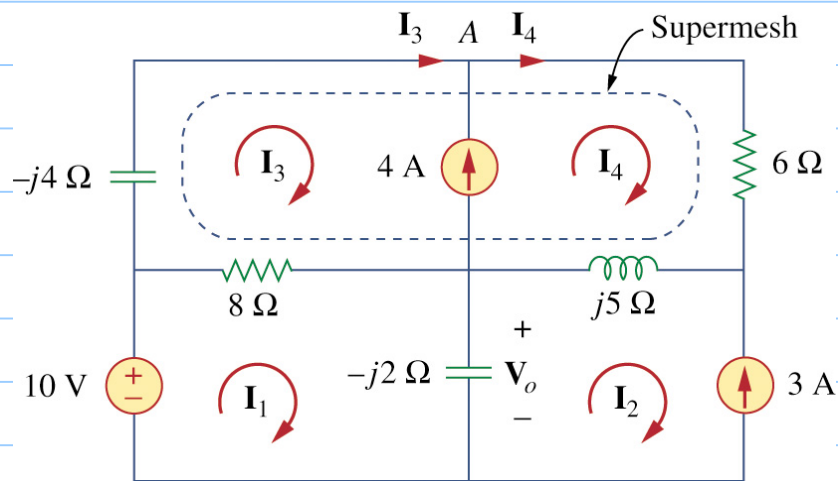


ECE202 (Fall 2007) HW#4 Solutions

(P.1) For the meshes (and supermesh) indicated:



For mesh 1, KVL gives

$$\textcircled{2} \quad -10 + (8 - j2)\vec{I}_1 - (-j2)\vec{I}_2 - 8\vec{I}_3 = 0 \quad (1)$$

For mesh 2,

$$\textcircled{2} \quad \vec{I}_2 = (-1)3\angle 0^\circ = -3 \text{ A} \quad (2)$$

Meshes 3 & 4 form a supermesh due to the shared current source between them.

For the supermesh:

$$\textcircled{2} \quad (8 - j4)\vec{I}_3 - 8\vec{I}_1 + (6 + j5)\vec{I}_4 - j5\vec{I}_2 = 0 \quad (3)$$

Also, applying KCL to the node above the top current source yields:

$$\textcircled{2} \quad \vec{I}_4 = \vec{I}_3 + 4 \quad (4)$$

(a) Solving by hand

Combining (1) and (2) yields

$$\textcircled{2} \quad (8 - j2)\vec{I}_1 - 8\vec{I}_3 = 10 + j6 \quad (5)$$

Also, combining (3) and (4) yields

$$\textcircled{2} \quad -8\vec{I}_1 + (14 + j)\vec{I}_3 = -24 - j35 \quad (6)$$

From equations (5) and (6) we now have the system of equations

$$\textcircled{2} \quad \begin{bmatrix} (8 - j2) & -8 \\ -8 & (14 + j) \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_3 \end{bmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix} \quad (7)$$

Equation (7) may be solved using Kramer's Rule, or other linear algebra techniques.

Forming the determinants

$$\Delta = \begin{vmatrix} 8-j2 & -8 \\ -8 & 14+j \end{vmatrix} = 112 + j8 - j28 + 2 - 64$$
$$= 50 - j20$$

$$\Delta_1 = \begin{vmatrix} 10+j6 & -8 \\ -24-j35 & 14+j \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280$$
$$= -58 - j186$$

The current \vec{I}_1 is obtain as:

$$\textcircled{2} \quad \vec{I}_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j186}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

The voltage, \vec{V}_0 , is

$$\vec{V}_0 = -j2(\vec{I}_1 - \vec{I}_2) = -j2(3.618 \angle 274.5^\circ)$$
$$= -7.234 - j6.568 \text{ V}$$

②

$$\vec{V}_0 = 9.756 \angle -137.68^\circ \text{ V}$$

or

$$\vec{V}_0 = 9.756 \angle 222.32^\circ \text{ V}$$

(P.1)(b) Using MATLAB.

Equations (1)-(4) form the system of equation

$$\textcircled{2} \begin{bmatrix} (8-j2) & j2 & -8 & 0 \\ 0 & 1 & 0 & 0 \\ -8 & -j5 & (8-j4) & (6+j5) \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \\ \vec{I}_3 \\ \vec{I}_4 \end{bmatrix} = \begin{bmatrix} 10 \\ -3 \\ 0 \\ 4 \end{bmatrix} \quad (8)$$

or $\underline{A} \underline{I} = \underline{b}$

\underline{I} can be obtained by multiplying both sides by the inverse of A

$$\textcircled{2} \quad \underline{A}^{-1} \underline{A} \underline{I} = \underline{A}^{-1} \underline{b} \quad (\text{note: order of multiplication is important!})$$
$$\therefore \underline{I} = \underline{A}^{-1} \underline{b}$$

Entering the matrix and vector into MATLAB and solving for \underline{I} (and \underline{V}_s):

```
>> A = [(8-j*2) (j*2) -8 0;  
0 1 0 0;  
-8 (-j*5) (8-j*4) (6+j*5);  
0 0 -1 1];  
>> b = [10 -3 0 4]';  
>> I = A\b
```

```
I =  
0.2828 - 3.6069i  
-3.0000 + 0.0000i  
-1.8690 - 4.4276i  
2.1310 - 4.4276i
```

```
>> Vo = -2 * j * (I(1) - I(2))
```

```
Vo =
```

```
-7.2138 - 6.5655i
```

```
>> abs(Vo)
```

```
ans =
```

```
9.7542
```

```
>> phase(Vo)*180/pi
```

```
ans =
```

```
-137.6936
```

③ w/ML Code


$$\therefore \vec{V}_o = 9.7542 \angle -137.69^\circ \text{ V}$$

(Same as in
part (a))

HW#4, P.2 [25 pts]

(a) [5 pts] $i(t) = 7.906 \cos(2t - 136.5^\circ)$ A

(b) [15 pts] Schematic Diagram

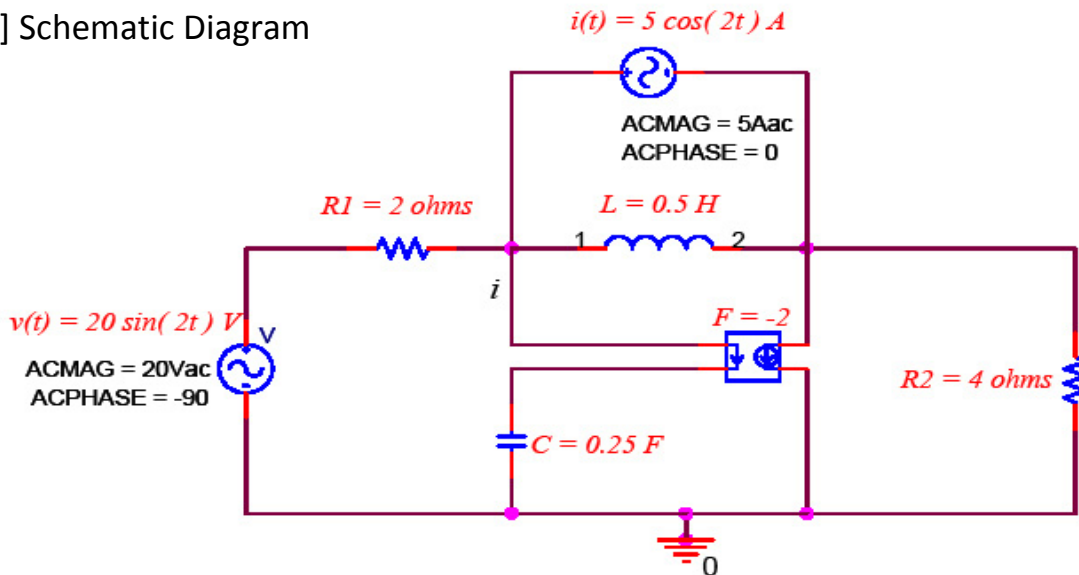

Title		
ECE202 (Spring 2007) Solution Key		
Size	Document Number	Rev
	Homework 4, Problem 2	1.0
Date:	Monday, October 01, 2007	Sheet 1 of 1

From simulation output file:

```
FREQ      IM(V_PRINT1)  IP(V_PRINT1)
3.183E-01  7.906E+00   -1.365E+02
```

(c) [5 pts] SCHEMATIC1.net:

```
* source HW4_P2
R_R1      N09488 N07835  2
R_R2      0 N08350  4
C_C       0 N00532  0.25
L_L       N07835 N08350  0.5
V_V       N09488 0 DC 0Vdc AC 20Vac -90
I_I       N07835 N08350 DC 0Adc AC 5Aac 0
V_PRINT1  N16146 N07835 0V

.PRINT     AC
+ IM(V_PRINT1)
+ IP(V_PRINT1)
X_F1      N16146 N00532 N08350 0 SCHEMATIC1_F1

.subckt   SCHEMATIC1_F1 1 2 3 4
F_F1      3 4 VF_F1 -2
VF_F1     1 2 0V
.ends     SCHEMATIC1_F1
```