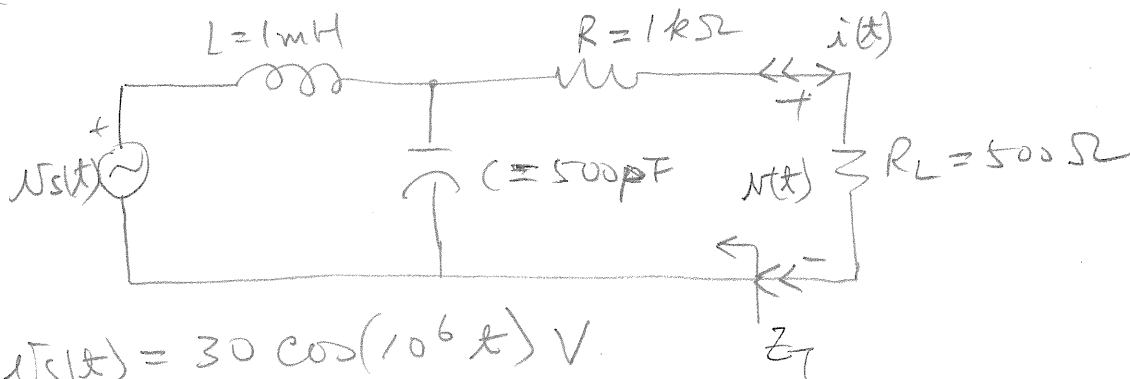


# ECE 202 Fall 2007 H.W #5 Solution Key

(P. 2) Solve P 8-59 in text.



$$v_s(t) = 30 \cos(10^6 t) \text{ V}$$

$$\therefore \omega = 10^6 \text{ rads}^{-1}$$

Obtain the Thevenin equivalent voltage source and impedance:

$$Z_T = 10^3 + \left( \frac{1}{j\omega(0.5 \times 10^{-9})} + \frac{1}{j\omega 10^{-3}} \right) \Omega$$

$$Z_T = 1 \times 10^3 + j 2 \times 10^3 = 1 + j2 \text{ k}\Omega$$

(2 pts)

For Thevenin voltage source, in phasor form

$$\vec{V}_T = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + j\omega L} \cdot \vec{V}_s$$

(2 pts)

$$= \frac{1}{j(10^6)(0.5 \times 10^{-9})} \cdot \frac{1}{j(10^6)(0.5 \times 10^{-9}) + j(10^6)(10^{-3})}$$

$$\vec{V}_T = 60 \text{ V}$$

(2 pts)

(P. 2) (P8-59(a))

For  $Z_L = 500 \Omega$ ,

$$\vec{I}_L = \frac{\vec{V}_T}{Z_T + 500}$$

(1 pt)

$$P_L = 0.5 |\vec{I}_L|^2 \cdot 500 \text{ W}$$

(2 pts)

$$\therefore \boxed{P_L = 0.144 \text{ W}} \quad (\underline{5 \text{ pts}})$$

(b)

$$P_{\text{max}} = \frac{|\vec{V}_T|^2}{8 \operatorname{Re}\{Z_T\}}$$

(1 pt)

$$= \frac{(60)^2}{8(1 \times 10^3)}$$


$$\boxed{P_{\text{max}} = 0.45 \text{ W}} \quad (\underline{5 \text{ pts}})$$

(c) For max power:  $Z_L = Z_T^*$  (1 pt)

$$\text{thus } \boxed{Z_L = 1 \times 10^3 - j2 \times 10^3 \Omega} \quad (\underline{5 \text{ pts}})$$

(2 pts)

(P.3) Solve P8-60 in text.

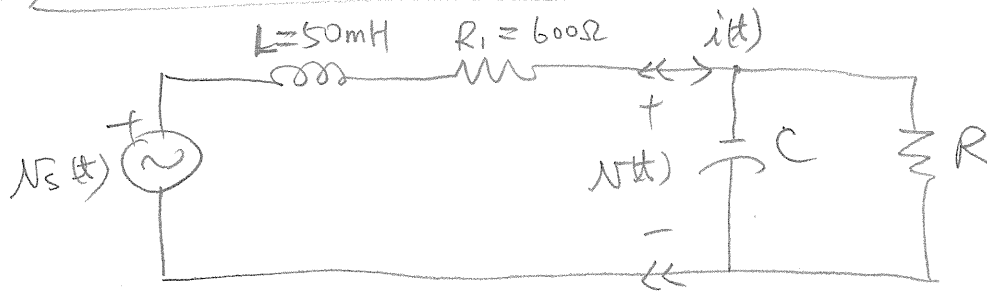

$$v_s(t) = 10 \cos(8000t) \text{ V}, \quad \omega = 8000 \text{ rad/s}$$

The Thévenin equivalent seen by the load is

(1 pt)  $\vec{V}_T = 10 \text{ V}$

$$Z_T = R_1 + j\omega L = 600 + j(8000)(50 \times 10^{-3}) \Omega$$

(2 pts)  $Z_T = 600 + j400 \Omega$

(2 pts) (a)  $P_{\max} = \frac{|\vec{V}_T|^2}{8 \operatorname{Re}\{Z_T\}} = \frac{(10)^2}{8(600)}$

$$P_{\max} = 2.083 \times 10^{-2} \text{ W} \quad (5 \text{ pts})$$

(b) For max average power, the load should be conjugate-matched to the Thévenin impedance:

(2 pts)  $Z_L = \frac{1}{\frac{1}{R} + j\omega C} = Z_T^* = 600 - j400 \Omega$

$$\therefore \frac{1}{\frac{1}{R} + j\omega C} = 600 - j400$$

(2 pts)  $\frac{1}{R} + j\omega C = \frac{1}{600 - j400} = 1.154 \times 10^{-3} + j7.69 \times 10^{-4}$

(P. 2) (cont'd)

comparing terms:

$$\frac{1}{R} = 1.154 \times 10^{-3}$$

(2 pts)  $\therefore$   $R = 866.581 \Omega$  (5 pts)

Also:  $j\omega C = j 7.69 \times 10^{-4}$

$$C = \frac{7.69 \times 10^{-4}}{8000}$$

(2 pts)  $\therefore$   $C = 96.15 \text{ nF}$  (5 pts)

(P.4)

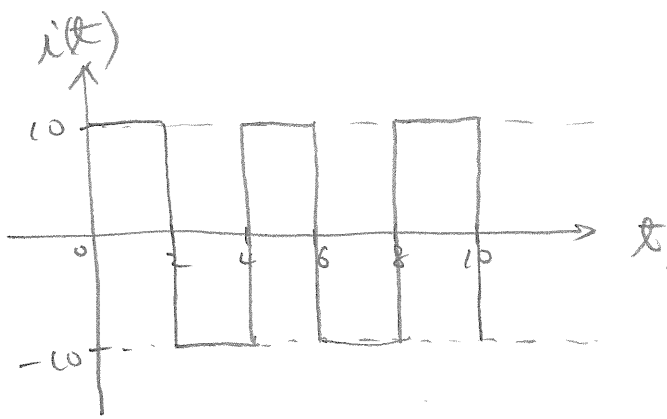


Fig. 1

(a) Find the rms value of  $i(t)$  in Fig. 1.

For one period,  $T = 4$ :  
$$i(t) = \begin{cases} I_m & 0 \leq t < 2 \\ -I_m & 2 \leq t < 4 \end{cases} \quad I_m = 10 \quad \text{over 1 period of } T = 4.$$

Square:  $i^2(t) = \begin{cases} I_m^2 & 0 \leq t < 2 \\ I_m^2 & 2 \leq t < 4 \end{cases} \quad \text{over 1 period } T.$   
(2 pts)

Mean: mean value =  $\frac{1}{T} \int_0^T i^2(t) dt$ .

(2 pts)

$$\begin{aligned} &= \frac{1}{T} \left\{ \int_0^{T/2} I_m^2 dt + \int_{T/2}^T I_m^2 dt \right\} \\ &= \frac{1}{T} \left\{ I_m^2 t \Big|_0^{T/2} + I_m^2 t \Big|_{T/2}^T \right\} \\ &= \frac{1}{T} \{ I_m^2 T \} \end{aligned}$$

(2 pts)  $\therefore$  Mean value =  $I_m^2$

Root:  $\sqrt{I_m^2} \Rightarrow \boxed{I_{rms} = I_m = 10 \text{ A}}$  (10 pts)

P.4 (b) The avg pwr dissipated in a  $2\text{-}\Omega$  resistor is:

(2pts)  $P = I_{\text{rms}}^2 R = (10)^2 \cdot 2$  (1pt)

(2pts)  $P = 200 \text{ W}$  (5pts)

P.4 (c) For a sinusoidal signal of the same amplitude and frequency (thus, period):

$$i(t) = I_m \cos \left[ 2\pi \left( \frac{1}{T} \right) t \right] \text{ A.}$$

$$i(t) = 10 \cos(0.5\pi t) \text{ A}$$

(2pts)  $I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 \text{ A.}$

Avg power dissipated in this case is

(2pts)  $P = I_{\text{rms}}^2 R = (7.07)^2 (2)$

(1pt)  $P = 100 \text{ W}$  (5pts)

Notes: The sinusoidal signal delivers only half the average power of that delivered by the rectangular waveform!!