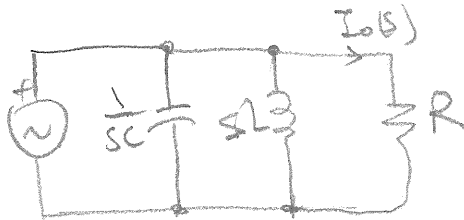


(P.2)  
(P.12-22)  
in  
text

$$C = 20 \mu\text{F} \quad Q = 10 \quad \omega_0 = 1 \text{ Mrads}^{-1}$$

Find  $R$ ,  $L$ ,  $\omega_{c1}$  &  $\omega_{c2}$ .

$$B = \frac{\omega_0}{Q} = \frac{1 \times 10^6}{10} = 100 \text{ krad/s}^{-1}$$

$$L = \frac{1}{\omega_0^2 \cdot C} = \frac{1}{(1 \times 10^6)^2 \cdot (20 \times 10^{-9})} = 50 \mu\text{H}$$

$$B = \omega_{c2} - \omega_{c1} = \frac{1}{RC} \quad (\text{eg 12-23 text})$$

$$R = \frac{1}{BC} = \frac{1}{(10)(20 \times 10^{-9})} = 500 \Omega$$

$$\therefore \omega_0^2 = \omega_{c1} \omega_{c2} = (10^6)^2$$

$$\uparrow$$

$$= 10^{12} \quad \text{--- ①}$$

$$\text{also } B = \omega_{c2} - \omega_{c1} = 100 \times 10^3$$

$$\omega_{c2} = \omega_{c1} + 100 \times 10^3 \quad \text{--- ②}$$

Sub ② into ①

$$\omega_{c1}^2 + 100 \times 10^3 \omega_{c1} - 10^{12} = 0$$

$$= -50 \times 10^3 \pm \frac{1}{2} \sqrt{(100 \times 10^3)^2 - 4(-10^{12})}$$

$$= -50 \times 10^3 \pm 6.325 \times 10^6$$

$$\omega_{c1} = 951.25 \text{ krad/s} \quad \text{or } -1.05 \text{ Mrads}^{-1}$$

unrealistic!


$$\text{OR } \omega_{c1} = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c1} = 951.25 \text{ krad/s}$$

$$\omega_{c2} = \omega_{c1} + 100 \times 10^3$$

$$\omega_{c2} = 1.051 \text{ Mrads}^{-1}$$

(P.3) [24]

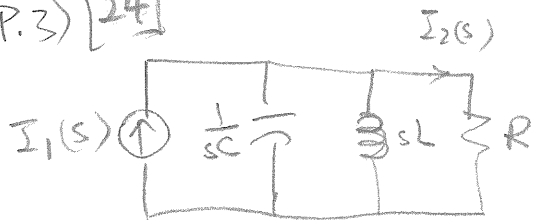

3(a) Find  $T(s) = \frac{I_2(s)}{I_1(s)}$

3

$$I_2(s) = I_1(s) \frac{\frac{1}{R}}{\frac{1}{R} + sC + \frac{1}{sL}}$$

current divider using admittances

$$\frac{I_2(s)}{I_1(s)} = \frac{s \frac{1}{R} C}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} \quad \text{①}$$

3 (-2 if coefficient of  $s^2$  term is not 1.)

$L = 50 \mu\text{H}$   
 $C = 20 \text{ nF}$   
 $R = 500 \Omega$

3(b) Parallel RLC circuit

10

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(50 \times 10^{-6})(20 \times 10^{-9})}} = 1 \text{ Mrads}^{-1} \quad \text{②}$$

$$B = \omega_{c2} - \omega_{c1} = \frac{1}{RC} = \frac{1}{(500)(20 \times 10^{-9})} = 100 \text{ Krads}^{-1} \quad \text{②}$$

$$Q = \frac{\omega_0}{B} = \frac{1 \times 10^6}{100 \times 10^3} = 10 \quad \text{②}$$

note:  $B = BW =$  bandwidth

$$\omega_{c2} - \omega_{c1} = B = 100 \text{ k}$$

$$\omega_{c2} = 100 \text{ k} + \omega_{c1}$$

$$\omega_0^2 = \omega_{c1} \cdot \omega_{c2} = \omega_{c1} (100 \text{ k} + \omega_{c1}) = (1 \times 10^6)^2$$

$$\omega_{c1}^2 + (100 \times 10^3) \omega_{c1} - 1 \times 10^{12} = 0$$

$$\omega_{c1} = 951.25 \text{ Krads}^{-1}$$

$$\text{or } \omega_{c1} = -1.0 \times 10^6 \text{ Mrads}^{-1}$$

unrealizable

$$\omega_{c2} = \omega_{c1} + 100 \times 10^3$$

if  $\omega_{c1} = 951.25 \times 10^3 \text{ rad/s}$

then  $\omega_{c2} = 1.051 \times 10^6 \text{ rad/s}$

OR  $\omega_{c1} \cdot \omega_{c2} = \omega_0^2 = 1 \times 10^{12} \quad \frac{3}{6}$

$$\omega_{c2} = \frac{1 \times 10^{12}}{951.25 \times 10^3}$$

$$\omega_{c2} = 1.051 \times 10^6 \text{ rad/s}$$

OR 
$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$
  
$$= 9.512 \times 10^5 \text{ rad/s}$$

$\therefore \omega_{c1} = 951.2 \text{ k rad/s} \quad (2)$   
 $\omega_{c2} = 1.051 \text{ M rad/s} \quad (2)$

3(c) net list file (3)

(11) Magnitude plot (1)

$\omega_{c1}$  (1)

$\omega_{c2}$  (1)

Phase plot (1)

$\omega_{c1}$  (1)

$\omega_{c2}$  (1)

$H(s)$  is a band pass filter (2)


$$\omega \ll \omega_0 \quad |H(j\omega)| \rightarrow -\infty \text{ dB} = 0$$

$$\omega \gg \omega_0 \quad |H(j\omega)| \rightarrow -\infty \text{ dB} = 0$$


$$\omega = \omega_0$$

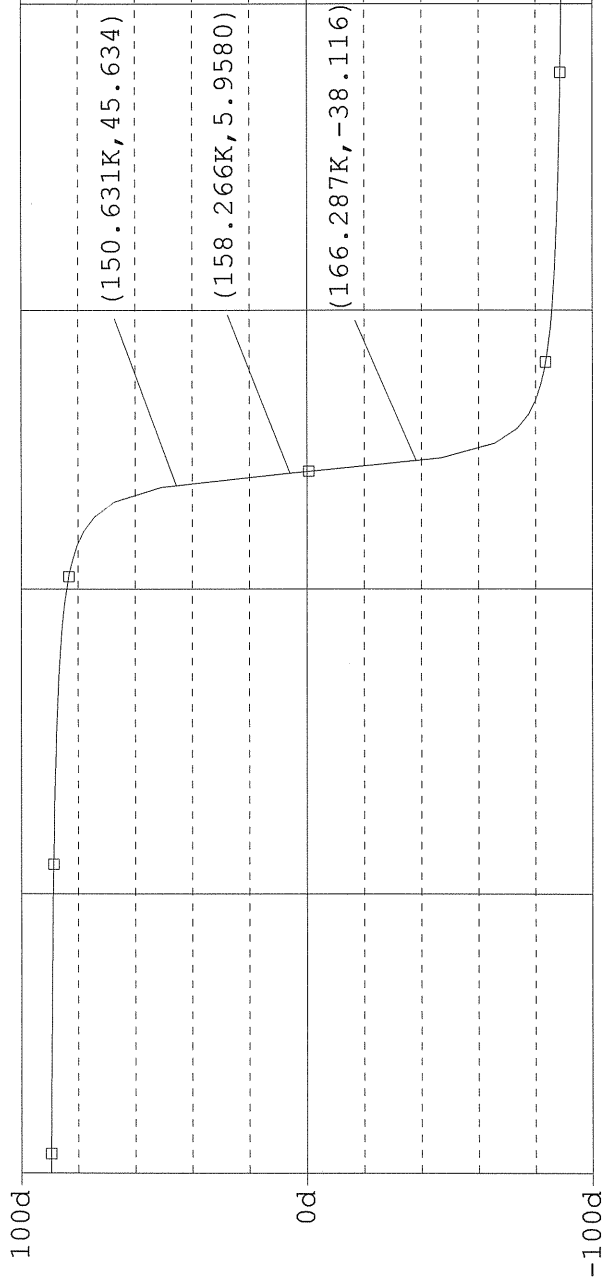(A) HW8\_P3.dat (active)

```
* source HW8_P3
I1 10 DC 0Ac AC 1Aac
C1 01 20n
R1 01 500
L1 01 50uH
.probe
.ac dec 20 10000 100000000
.end
```



□ P(I(R1)/I(I1))

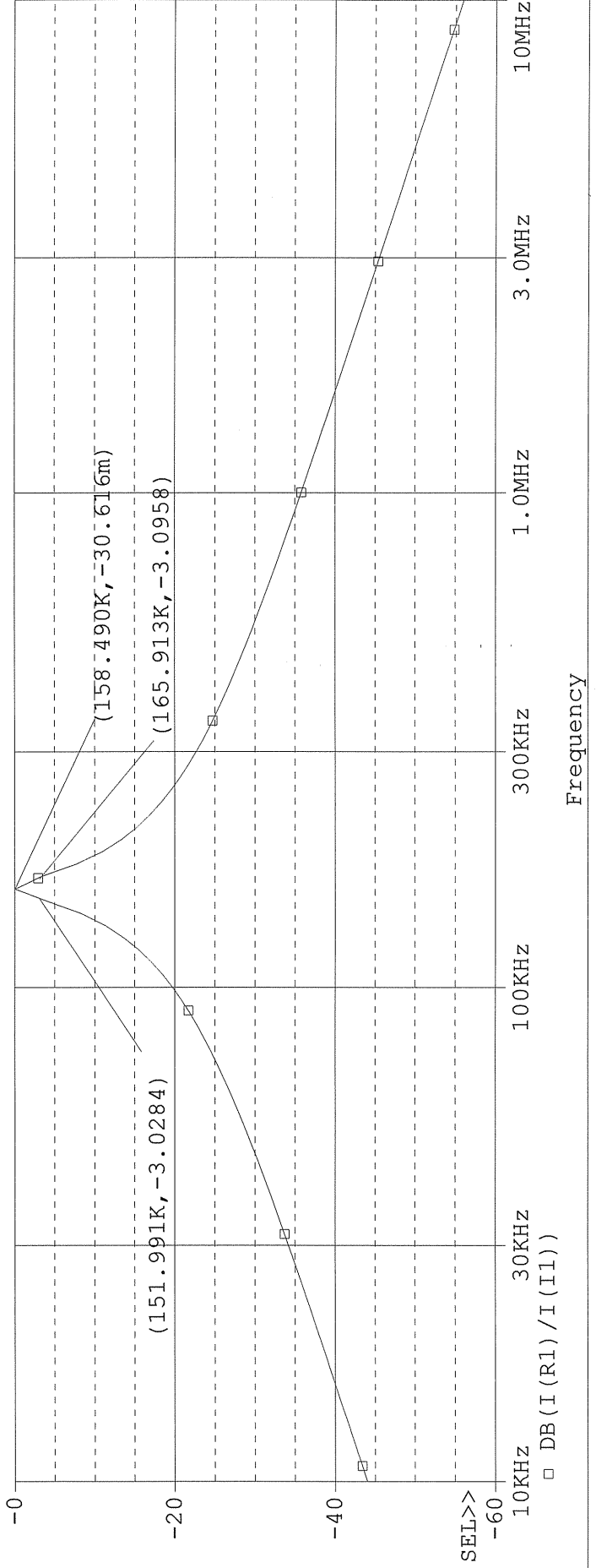

SEL>>

□ DB(I(R1)/I(I1))

Frequency

(P.4) (P12-24 in text)

(I) Series RLC circuit :

$$B = \frac{R}{L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

(Eqn 12-17 in text) (Eqn 12-15 in text)

- |        |                  |   |
|--------|------------------|---|
| (I)(a) | Replace R by 2R  | doubles B w/out $\Delta$ ing $\omega_0$ |
| (b)    | Replace C by C/4 | doubles $\omega_0$ w/out $\Delta$ ing B |


(II) Parallel RLC circuit

$$B = \frac{1}{RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

(Eqn 12-23 in text) (Eqn 12-21 in text)

- |         |                            |                                       |
|---------|----------------------------|---------------------------------------|
| (II)(a) | Replace R by 0.5R (or R/2) |                                       |
| (b)     | Replace L by L/4           | doubles $\omega_0$ w/o $\Delta$ ing B |

(P.5)  
10

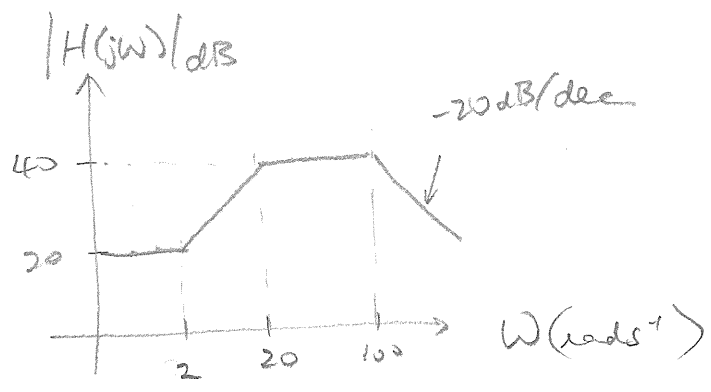

$20 = 20 \log_{10} k \rightarrow k = 10. \quad (2)$

A zero caused a slope of  $+20$  dB/dec @  $\omega = 2$  rad/s<sup>-1</sup>  
 $\Rightarrow (1 + j\frac{\omega}{2}) \quad (2)$

A pole caused a slope of  $-20$  dB/dec @  $\omega = 20$  rad/s<sup>-1</sup>  
 $\Rightarrow (\frac{1}{1 + j\frac{\omega}{20}}) \quad (2)$

A pole caused a slope of  $-20$  dB/dec @  $\omega = 100$  rad/s<sup>-1</sup>  
 $\Rightarrow (\frac{1}{1 + j\frac{\omega}{100}}) \quad (2)$

Hence:

$$H(j\omega) = \frac{10 (1 + j\frac{\omega}{2})}{(1 + j\frac{\omega}{20})(1 + j\frac{\omega}{100})}$$

let  $j\omega = s$

$$H(s) = \frac{10 (1 + \frac{s}{2})}{(1 + \frac{s}{20})(1 + \frac{s}{100})} = \frac{10s (2+s) 2000}{(20+s)(100+s)}$$

$$H(s) = \frac{10000 (s+2)}{s^2 + 120s + 2000} \quad (2)$$

(-5 if coefficient of  $s^2$  not equal 1)