
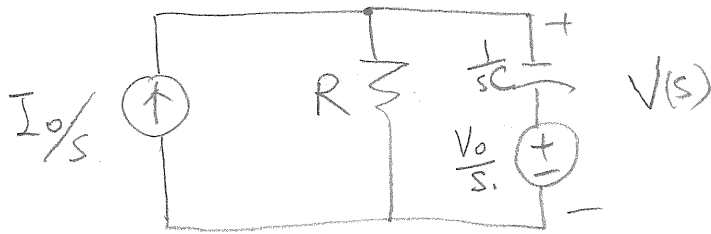


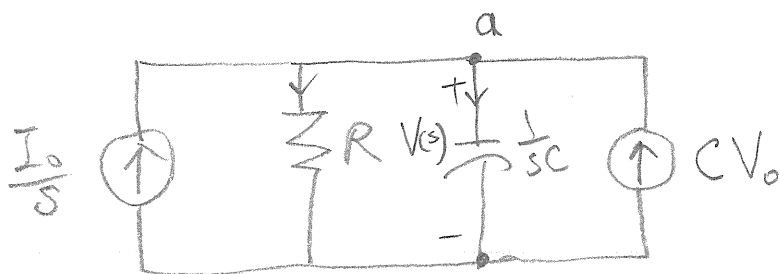(P.1) For the capacitor,  $V(0^-) = V_0$ ,  
 [13] The circuit diagram becomes



With a source transformation, the circuit becomes



Applying KCL to node a yields

$$\frac{I_0}{s} - \frac{V(s)}{R} - \frac{V(s)}{1/sC} + CV_0 = 0$$

$$\therefore \frac{I_0}{s} + CV_0 = \frac{V(s)}{R} + V(s) sC = \left( sC + \frac{1}{R} \right) V(s)$$

$$V(s) = \frac{I_0}{s \left( sC + \frac{1}{R} \right)} + \frac{CV_0}{\left( sC + \frac{1}{R} \right)}$$

$$= \frac{V_0}{s + \frac{1}{RC}} + \frac{I_0/C}{s \left( s + \frac{1}{RC} \right)}$$

$$= \frac{V_0}{s + \frac{1}{RC}} + \frac{k_1}{s} + \frac{k_2}{s + \frac{1}{RC}}$$

$$k_1 = \frac{I_0/c}{0 + \frac{1}{RC}} = I_0 R$$


$$k_2 = (s + \frac{1}{RC}) \frac{I_0/c}{s(s + \frac{1}{RC})} \Big|_{s = -\frac{1}{RC}} = \frac{I_0/c}{-\frac{1}{RC}} = -I_0 R$$

$$\begin{aligned} \therefore V(s) &= \frac{V_0}{s + \frac{1}{RC}} + \frac{I_0 R}{s} - \frac{I_0 R}{s + \frac{1}{RC}} \\ &= (V_0 - I_0 R) \frac{1}{s + \frac{1}{RC}} + I_0 R \frac{1}{s} \end{aligned}$$


$$\therefore v(t) = \left[ (V_0 - I_0 R) e^{-\frac{t}{RC}} + I_0 R \right] u(t) \quad V$$

$$\tau = RC$$

(P.1) Alternate Approach

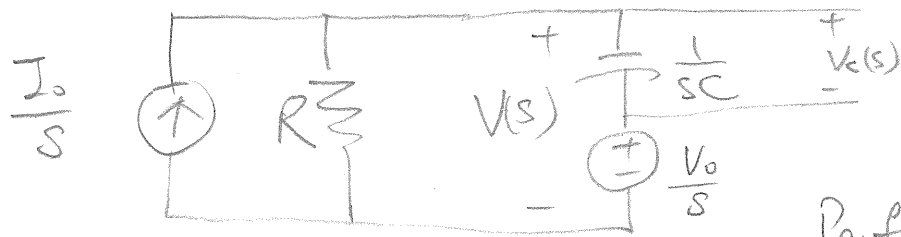

Perform a source transformation ...

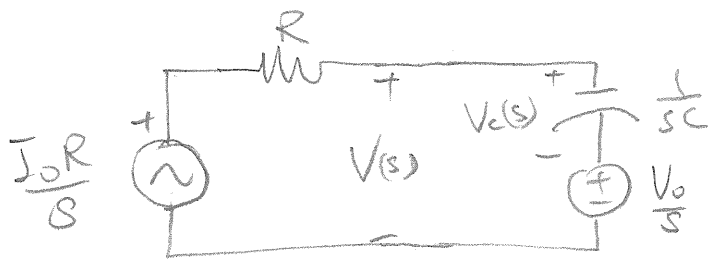

$$V_{c1}(s) = \frac{I_0 R}{s} \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{I_0 R}{s} \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$V_{c2}(s) = -\frac{V_0}{s} \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = -\frac{V_0}{s} \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$V_c(s) = \frac{(I_0 R - V_0) \frac{1}{RC}}{s(s + \frac{1}{RC})} = \frac{k_1}{s} + \frac{k_2}{s + \frac{1}{RC}}$$

$$k_1 = I_0 R - V_0$$

$$k_2 = \frac{(I_0 R - V_0) \frac{1}{RC}}{-\frac{1}{RC}} = -(I_0 R - V_0)$$

$$\therefore V_c(s) = -(V_0 - I_0 R) \frac{1}{s} + (V_0 - I_0 R) \frac{1}{s + \frac{1}{RC}}$$

$$V(s) = (V_0 - I_0 R) \frac{1}{s + \frac{1}{RC}} + I_0 R \frac{1}{s} = V_c(s) + \frac{V_0}{s}$$

$$\therefore \boxed{v(t) = \left[ (V_0 - I_0 R) e^{-\frac{t}{RC}} + I_0 R \right] u(t) \text{ V}}$$

$$\boxed{\text{time constant } \tau = RC}$$


(P.2) [50]

(2pts for each label)

4/10

(a) [14]

$$V_1(s) = \frac{10}{s}$$

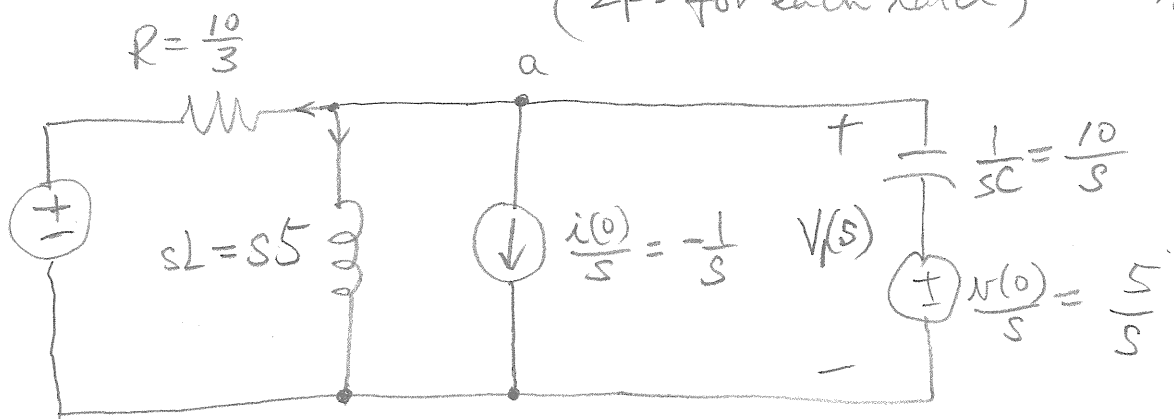

(b) [11]

Apply KCL at node a yields:

$$\frac{V_1(s) - \frac{10}{s}}{\frac{10}{3}} + \frac{V_1(s)}{s5} - \frac{1}{s} + \frac{V_1(s) - \frac{5}{s}}{10/s} = 0.$$

$$(0.3)V_1(s) - \frac{3}{s} + \frac{V_1(s)}{s5} - \frac{1}{s} + \frac{sV_1(s)}{10} - \frac{1}{2} = 0.$$

$$V_1(s) \left[ 0.3 + \frac{1}{s} 0.2 + 0.1s \right] = \frac{3}{s} + \frac{1}{s} + 0.5$$

$$\frac{0.1}{s} V_1(s) \left[ 3s + 2 + s^2 \right] = \frac{4}{s} + 0.5.$$

$$V_1(s) \left[ s^2 + 3s + 2 \right] = 40 + 5s$$

$$\therefore V_1(s) = \frac{5s + 40}{s^2 + 3s + 2} = \frac{5s + 40}{(s+2)(s+1)}$$

$$= \frac{k_1}{s+1} + \frac{k_2}{s+2}$$

$$k_1 = \frac{35}{1} = 35$$

$$k_2 = \frac{30}{-1} = -30$$


$$\therefore V_1(s) = \frac{35}{s+1} - \frac{30}{s+2}$$

thus

$$(b) \mathcal{W}_1(t) = \left[ 35e^{-t} - 30e^{-2t} \right] u(t) \text{ V}$$

P. 2 (c)  
[5]

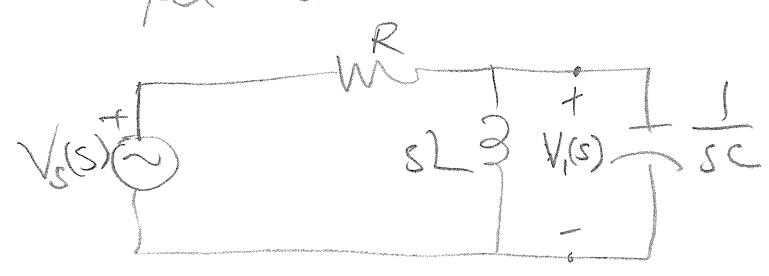To obtain the network function,  
set all ICs to 0.



$$V_1(s) = V_s(s) \frac{sL // \frac{1}{sC}}{sL // \frac{1}{sC} + R}$$

note:

$$sL // \frac{1}{sC} = \frac{sL \frac{1}{sC}}{sL + \frac{1}{sC}} = \frac{sL}{s^2LC + 1}$$

$$T_1(s) = \frac{V_1(s)}{V_s(s)} = \frac{\frac{sL}{s^2LC + 1}}{\frac{sL}{s^2LC + 1} + R} = \frac{sL}{sL + Rs^2LC + R}$$

$$= \frac{sL}{s^2RLC + sL + R}$$

$$= \frac{s \frac{1}{RC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}}$$

note:

$$\frac{1}{RC} = \frac{1}{\left(\frac{10}{3}\right)(0.1)} = 3$$

and

$$\frac{1}{LC} = \frac{1}{5(0.1)} = 2$$

$$(c) T_1(s) = \frac{3s}{s^2 + 3s + 2}$$

$$H(s) = 1 \cdot T_1(s) = \frac{k_1}{s+2} + \frac{k_2}{s+1}$$

P.2(d)

[10]

$$k_1 = \frac{3s}{s+1} \Big|_{s=-2} = \frac{-6}{-1} = 6$$

$$k_2 = \frac{3s}{s+2} \Big|_{s=-1} = \frac{-3}{1} = -3$$

$$\therefore H_1(s) = \frac{6}{s+2} - \frac{3}{s+1}$$

$$(d) \quad h_1(t) = \left[ \underset{2}{6} e^{-\underset{2}{2t}} - \underset{2}{3} e^{-\underset{2}{t}} \right] \underset{2}{u(t)}$$

P.2(e) Step response

[10]

To obtain the step response,  $g(t)$ , we use the relationship:

$$G(s) = \frac{H_1(s)}{s} = \frac{3}{s^2 + 3s + 2} = \frac{k_1}{s+2} + \frac{k_2}{s+1}$$


$$k_1 = \frac{3}{s+1} \Big|_{s=-2} = -3$$

$$k_2 = \frac{3}{s+2} \Big|_{s=-1} = 3$$


$$\therefore G(s) = \frac{-3}{s+2} + \frac{3}{s+1}$$

$$(e) \quad g(t) = \left[ \underset{2}{-3} e^{-\underset{2}{2t}} + \underset{2}{3} e^{-\underset{2}{t}} \right] \underset{2}{u(t)}$$

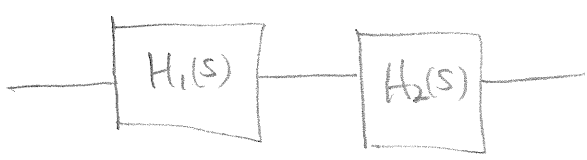P.3  
[18]  $h_1(t) = e^{-2t}$   
 $h_2(t) = 4e^{-4t}$



The cascaded system is

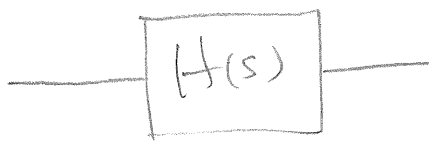

$H(s) = H_1(s) \cdot H_2(s)$

which has the time-domain relation

$h(t) = h_1(t) * h_2(t)$

(i) The time-domain integral is  $h(t) = \int_0^t h_1(t-\tau) h_2(\tau) d\tau$

[10]  $h(t) = \int_0^t e^{-2(t-\tau)} \cdot 4e^{-4\tau} d\tau$  (2)

$= \int_0^t 4e^{-2t} e^{-2\tau} d\tau$

$= 4e^{-2t} \int_0^t e^{-2\tau} d\tau$

$= (4e^{-2t}) \left(-\frac{1}{2}\right) e^{-2\tau} \Big|_0^t$

$= -2e^{-2t} [e^{-2t} - 1]$

$\therefore h(t) = \left( \underset{2}{2} e^{-2t} - \underset{2}{2} e^{-4t} \right) u(t)$

P. 3 (ii)  
[8]

$$H(s) = H_1(s) \cdot H_2(s)$$

$$H_1(s) = \mathcal{L}\{h_1(t)\} = \frac{1}{s+2}$$

$$H_2(s) = \mathcal{L}\{h_2(t)\} = \frac{4}{s+4}$$

$$\therefore H(s) = \frac{1}{s+2} \cdot \frac{4}{s+4}$$

$$= \frac{k_1}{s+2} + \frac{k_2}{s+4}$$


$$k_1 = \frac{4}{s+4} \Big|_{s=-2} = 2$$

$$k_2 = \frac{4}{s+2} \Big|_{s=-4} = -2$$

$$\therefore H(s) = 2 \frac{1}{s+2} - \frac{2}{s+4}$$

$$\therefore \boxed{h(t) = \left( \underset{2}{2} e^{-2t} - \underset{2}{2} e^{-4t} \right) u(t)}$$

P.4  
[19]

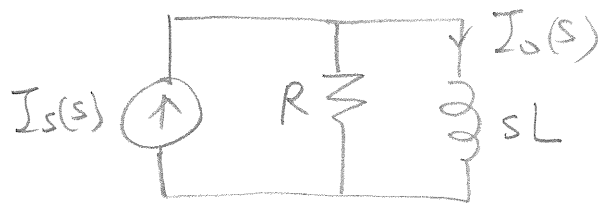

$R = 1 \Omega$   
 $L = 1 H$

To use the convolution integral, we need the impulse response,  $h(t)$ , of the circuit.


$h(t)$  may be obtained as  $\mathcal{L}^{-1}\{H(s)\}$ .

The transfer function,  $H(s)$ , of the circuit is

$$H(s) = \frac{I_o(s)}{I_s(s)} = \frac{R}{R + sL} = \frac{1}{s + 1}$$

$$\therefore h(t) = e^{-t} u(t)$$

The input signal is

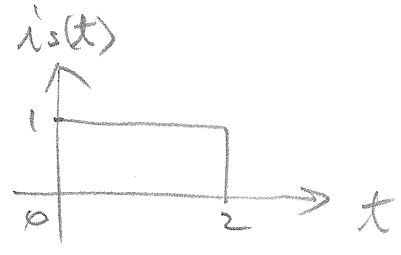

$$i_s(t) = u(t) - u(t-2)$$

Thus, the output is

$$\begin{aligned} i_o(t) &= h(t) * i_s(t) \\ &= \int_0^t i_s(\tau) h(t-\tau) d\tau \\ &= \int_0^t [u(\tau) - u(\tau-2)] e^{-(t-\tau)} d\tau \end{aligned}$$

P. 4 (contd)

Since  $u(\tau-2) = 0$  for  $0 < \tau < 2$ ,  
 the integrand involving  $u(\tau)$  is nonzero  
 $\forall \tau > 0$ .

The integrand involving  $u(\tau-2)$  is nonzero  
 only for  $t > 2$   
 Thus, the integration / convolution will be  
 performed in 2 parts, with

$$i_0(t) = i_1(t) + i_2(t)$$

$$\begin{aligned} i_1(t) &= \int_0^t (1) e^{-(t-\tau)} d\tau \\ &= e^{-t} \int_0^t (1) e^{\tau} d\tau \\ &= e^{-t} e^{\tau} \Big|_0^t = e^{-t} [e^t - 1] \end{aligned}$$

$$i_1(t) = 1 - e^{-t} \quad t \geq 0$$

And

$$\begin{aligned} i_2(t) &= \int_2^t (1) e^{-(t-\tau)} d\tau = e^{-t} \int_2^t e^{\tau} d\tau \\ &= e^{-t} [e^t - e^2] \\ &= 1 - e^2 e^{-t} = 1 - e^{-t+2} \quad \text{for } t \geq 2 \end{aligned}$$

$$\therefore i_0(t) = \underbrace{(1 - e^{-t})}_{1, 2, 2} \underbrace{[u(t)]}_{2} - \underbrace{(1 - e^{-(t-2)})}_{2, 2, 2} \underbrace{u(t-2)}_{2} \underbrace{A}_{2}$$

$$\text{OR } i_0(t) = \begin{cases} 1 - e^{-t} & A & 0 \leq t \leq 2 \\ (e^2 - 1)e^{-t} & A & t > 2 \end{cases} \begin{matrix} 2, 2, 1, 2, 2 \\ 2, 2, 2, 1, 2 \end{matrix} \Downarrow$$

Supplemental

100%

Are the two forms of solution really equal to each other?

$$i_o(t) = (1 - e^{-t})u(t) - [1 - e^{-(t-2)}]u(t-2) \quad \text{--- ①}$$

$$i_o(t) = \begin{cases} 0 & t < 0 \\ 1 - e^{-t} & 0 \leq t \leq 2 \\ (e^2 - 1)e^{-t} & 2 < t \end{cases} \quad \text{--- ②}$$

Ⓐ For  $t < 0$ , ① yields zero ✓

Ⓑ For  $0 \leq t \leq 2$ :  
the 2nd term in ① is zero due to  $u(t-2)$ .

The output is due to contribution from the  $1e^t$  term in ①:

$$i_o(t) = (1 - e^{-t}) \cdot 1 - [1 - e^{-(t-2)}] \cdot 0$$
$$i_o(t) = 1 - e^{-t} \quad 0 \leq t \leq 2 \quad \checkmark$$

Ⓒ For  $t > 2$ :  
Both terms in ① contribute to the answer:

$$i_o(t) = (1 - e^{-t}) \cdot 1 - (1 - e^{-(t-2)}) \cdot 1 \quad \text{for } t > 2$$
$$= -e^{-t} + e^{-t} e^2$$

$$i_o(t) = e^{-t}(e^2 - 1) \quad t > 2 \quad \checkmark$$

∴ Yes, the two forms, ① & ②, are equal!