

## Electronics Primer

---

- ohms law
  - Kirchoff's current node rule
  
  - define resistor
  - define capacitor
  
  - high/low pass RC filters
  - $s = j\omega$  notation,  $\omega = 2\pi f$
  - filter transfer functions
- 

## Amplifiers and Analog Signal Processing

---

- Most bioelectric signals are small
    - voltages in micro-volts range
    - currents in pA and nA range common
  
  - Small signals require amplification and filtering
    - op-amp, resistors and capacitors
    - integrated circuit and surface-mount technology
  
  - Most modern signal processing tasks (filtering) are performed on a digital signal processor.
    - little change in amplification/filtering requirements over last 40 years
    - but new interest in putting DSP algorithms into analog circuits
      - due to demand for low power portable/implantable instruments
-

## Ideal Op-Amp

- Operational amplifier (op-amp) is a high-DC-gain differential amplifier
- Design circuits assuming op-amps are ideal
  - then verify/modify using simulations/prototyping
- Ideal op-amp model
  - "open loop" gain:  $A = \infty$
  - differential input resistance:  $R_d = \infty$
  - output resistance:  $R_o = 0$ 
    - input current = 0
  - output voltage:
    - $v_o = 0$  when  $v_1 - v_2 = 0$


*ideal op-amp*

$$A = \infty$$

$$v_o = 0$$

$$R_d = \infty$$

$$R_o = 0$$

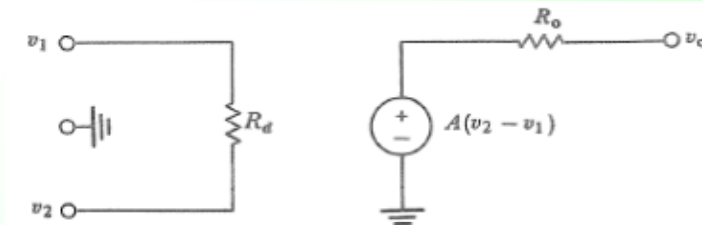


*ideal op-amp small signal model*

## Op-Amp Properties

- Properties
  - open-loop gain: ideally infinite: practical values 20k-200k
    - high open-loop gain  $\rightarrow$  virtual short between + and - inputs
  - input impedance: ideally infinite: CMOS opamps are close to ideal
  - output impedance: ideally zero: practical values 20-100 $\Omega$
  - zero output offset: ideally zero: practical value  $< 1\text{mV}$
  - gain-bandwidth product (GB): practical values  $\sim\text{MHz}$ 
    - frequency where open-loop gain drops to 1 V/V
- Commercial opamps provide many different properties
  - low noise
  - low input current
  - low power
  - high bandwidth
  - low/high supply voltage
  - special purpose: comparator, instrumentation amplifier

# Basic Op-Amp Principles

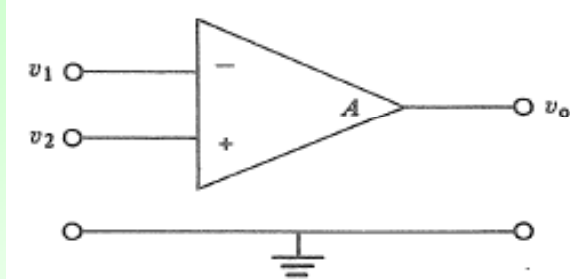


typical op-amp schematic symbol

$v_o, v_1, v_2$  referenced to ground

- Open loop gain:  $v_o = A (v_2 - v_1)$ 
  - since  $A$  is very large,  $v_1 - v_2$  must be very small
- When the op-amp output is in its linear range
  - two input terminals are at (essentially) the same voltage
  - i.e., "virtual ground" between op-amp inputs
    - rely on this for DC/bias calculations
- Single vs. Dual Supply Voltage
  - most modern ICs use single supply
    - "ground" in a dual supply becomes  $V_{DD}/2$  in single supply
      - mid way between  $V_{DD}$  and Ground

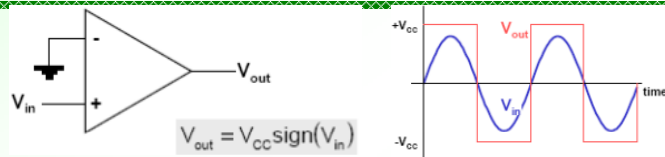
# Basic Opamp Configuration

- Voltage Comparator
  - digitize input
  - assumes very high DC gain
  - $V_{cc}$  = supply voltage




$$V_{out} = V_{CC} \text{sign}(V_{in})$$

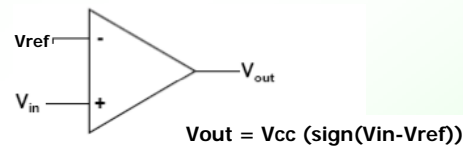- Negative Feedback
  - output tied back into negative input terminal
  - generally avoid positive feedback



$$V_{out} = V_{CC} (\text{sign}(V_{in} - V_{ref}))$$

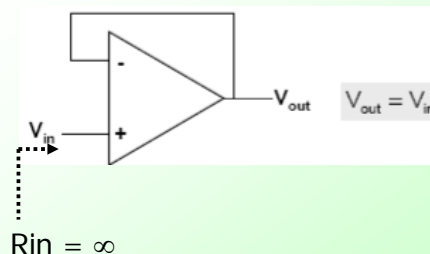- Voltage Follower
  - buffer
  - prevents input signal from being loaded down by a low-resistance load




$$V_{out} = V_{in}$$


$$R_{in} = \infty$$
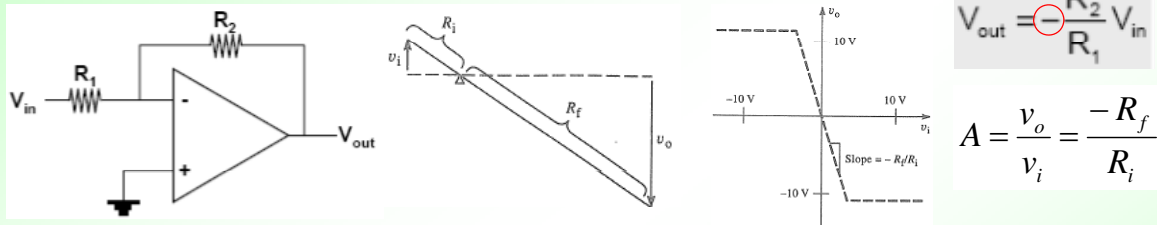
# Inverting/Non-Inverting Configurations

- Inverting Amplifier (uses negative feedback)




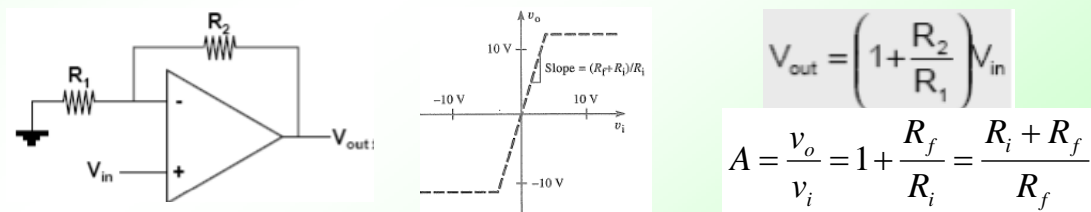- Non-Inverting Amplifier (also uses negative feedback)


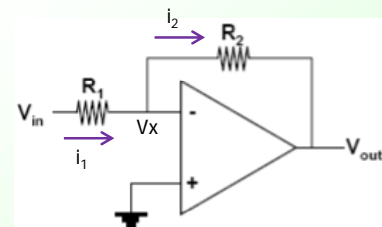
# Transfer Function Derivation


- Ideal op-amp conditions (simplify derivation)
  - virtual short at inputs (voltage at + same as at -)
  - no current into input terminals
- Inverting amplifier gain transfer function
  - write equations of operation from schematic using Ohms law
    - $V_x - V_{in} = R_1 * i_1$
    - $V_{out} - V_x = R_2 * i_2$
  - apply ideal op-amp conditions
    - virtual short  $\rightarrow V_x = 0$
    - no input current  $\rightarrow i_1 = i_2 = i$
  - thus
    - $-V_{in} = R_1 * i \rightarrow i = -V_{in}/R_1$
    - $V_{out} = R_2 * i \rightarrow i = V_{out}/R_2$
  - and setting  $i = i...$ 
    - $\rightarrow -V_{in}/R_1 = V_{out}/R_2 \rightarrow V_{out} = -V_{in} (R_2/R_1)$



$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

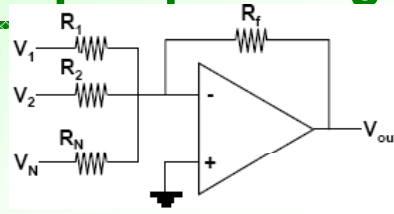
## More Opamp Configurations

- Summing Amp
  - weighted sum of multiple inputs
  - inverting or non???
- Differential Amp
  - match  $R_1$ s and  $R_2$ s
  - inverting or non???




$$V_{out} = - \left( V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_N \frac{R_f}{R_N} \right)$$
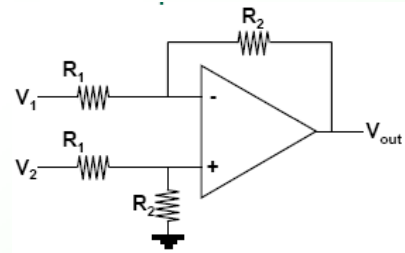
$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


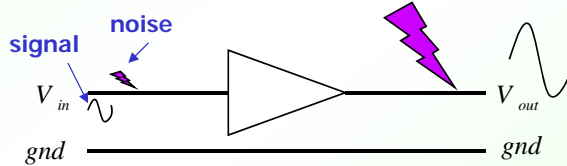
### Single-Ended Amplifier Representation



$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}}$$


### Noise Amplification

- even small interference at input gets amplified at output

## Differential vs. Common Mode Signal


- Define
  - $x^+$  = input at + terminal
  - $x^-$  = input at - terminal
  - $c$  = common mode signal on both inputs

- Differential inputs

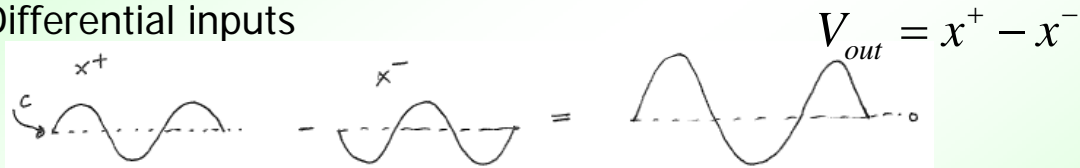

- Add common mode input

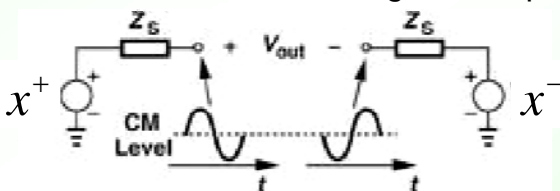- $c$  rejected by differential amplifier (not amplified)
- $c$  must be small enough to keep op-amp biased in linear operation




$$V_{out} = (x^+ + c) - (x^- + c)$$


$$c = \frac{x^+ + x^-}{2}$$
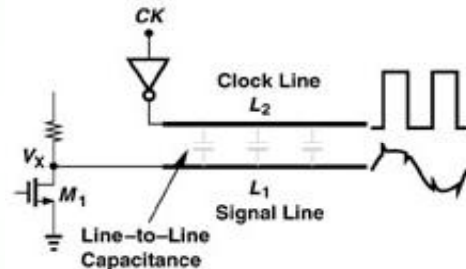
## Noise in Differential Amplifiers

- Global interference (e.g., supply voltage variations)
  - assumed to be located far away from amp. input terminals
    - same interference on both the terminals
  - appear as common mode disturbance.
  - example: clock noise




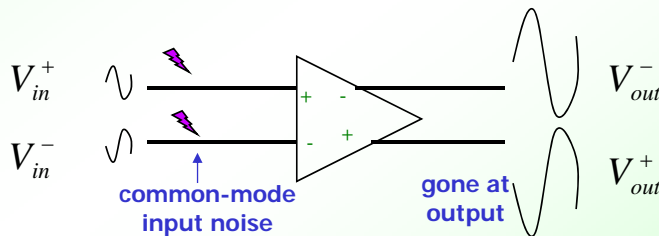- Differential amplifiers
  - amplify only the difference
  - reject the interference (common-mode)




## Desirable Properties of Amplifiers

- High differential gain,  $A_v$

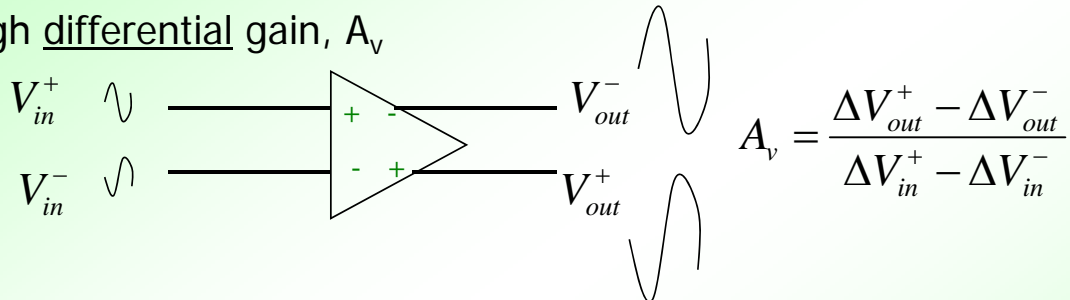

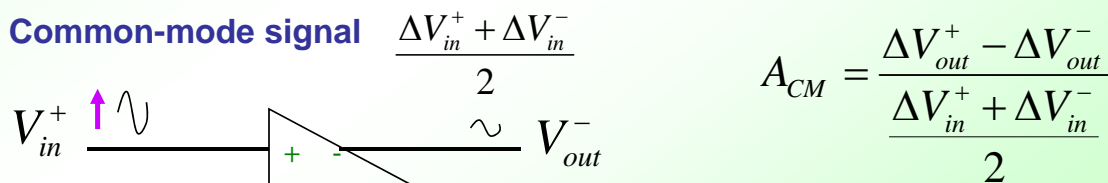
- Low common mode gain,  $A_{cm}$   
= high "common mode rejection"



common mode rejection ratio:  $CMRR = \frac{A_v}{A_{cm}}$
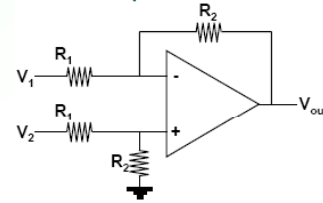
# 3-Op-Amp Instrumentation Amplifier


- Differential amplifiers
  - low common mode gain = Great!
  - lower than ideal input resistance – Bad!
- 3-op-amp structure
  - keeps low common mode gain
  - provides very high input resistance
    - why?
  - call “instrumentation amp”
    - will discuss in detail later



**total differential gain**


$$G_d = \frac{2R_2 + R_1}{R_1} \left( \frac{R_4}{R_3} \right)$$

$$A_{com} = 1$$

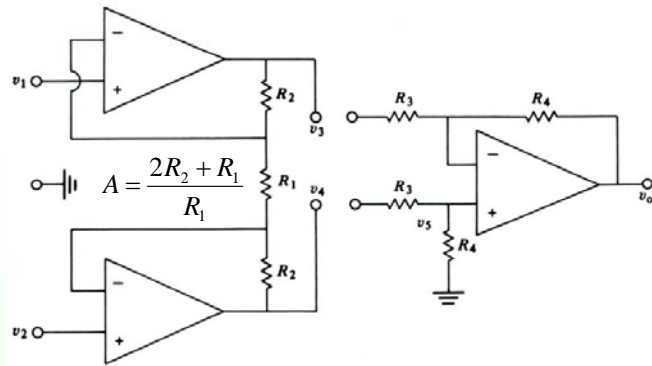

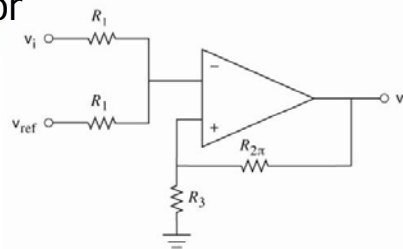
# Comparator

- Compare an input voltage  $v_i$  to a reference voltage  $v_{ref}$
- Output digital value (hi/low)
  - low if  $v_i > v_{ref}$  why low and not hi?
  - high if  $v_i < v_{ref}$
- Output voltage = supply voltage
- Op-amp comparator



(a)

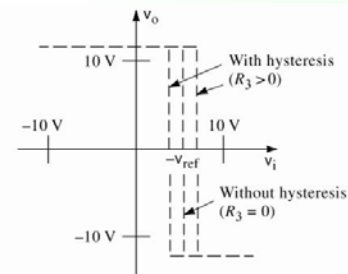

(b)


- Add hysteresis to improve noise immunity
  - hysteresis = rising transition point different that falling transition point
  - R3 controls hysteresis

## Logarithmic Amplifiers

- Uses non-linear current-voltage relationship of BJT in feedback path

$$V_{BE} = k \log\left(\frac{I_C}{I_S}\right)$$

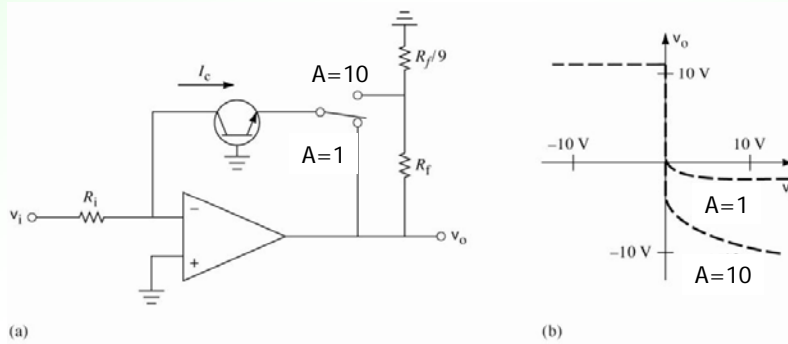
- Useful for computing logarithms and anti-logs
  - for compressing and multiplying/dividing signals



## Integrating/Differentiating Configurations


- Integrating Amp

$$v = \frac{1}{C} \int_0^t i dt$$

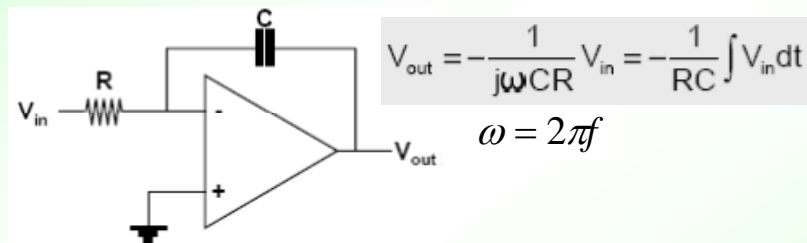

- Differentiating Amp


$$i = C \frac{dv}{dt}$$

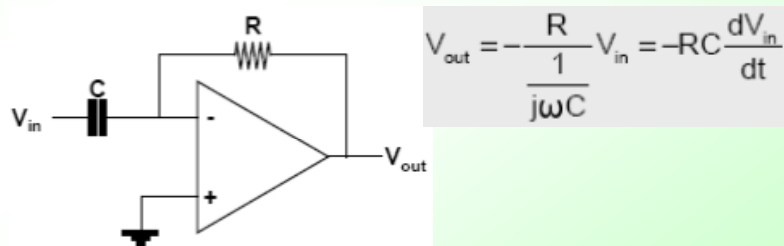




# Converting Configuration

- Current-to-Voltage

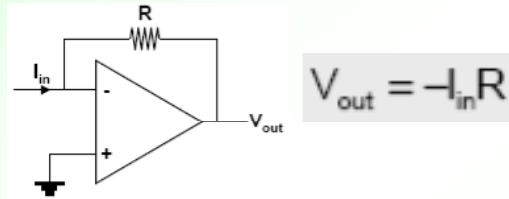


- Voltage-to-Current

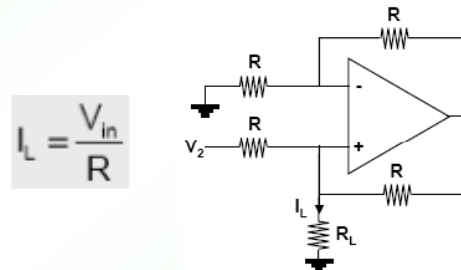

# Active Filters


- Passive low pass filter

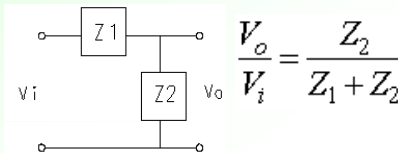

If Z1 is a resistor (R) and Z2 is a capacitor (1/sC) then

$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sCR}$$

- Active low pass filter

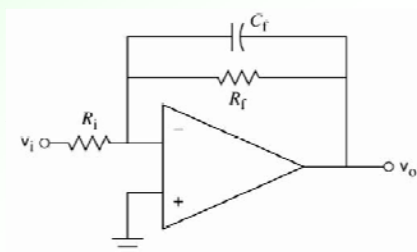

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{Z_f}{Z_i} = -\frac{(R_f / j\omega C_f)}{[(1 / j\omega C_f) + R_f]}$$

-3dB frequency

$$\omega_0 = \frac{1}{R_f C_f}$$


$$= -\frac{R_f}{(1 + j\omega R_f C_f) R_i} = -\frac{R_f}{R_i} \frac{1}{1 + s/\omega_0} \quad \omega = 2\pi f$$

$$\frac{V_o}{V_i} = \frac{H_o \omega_0}{s + \omega_0}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{1}{1 + j\omega R_f C_f}$$

# Active Filters



- Active high pass filter

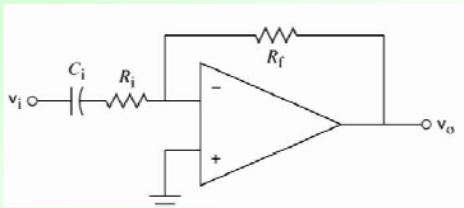

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{j\omega R_i C_i}{1 + j\omega R_i C_i}$$


$$\frac{V_o}{V_i} = H_0 \frac{s}{s + \omega_0} \quad \omega_0 = 1/R_i C_i$$

First-order High Pass Butterworth Filter

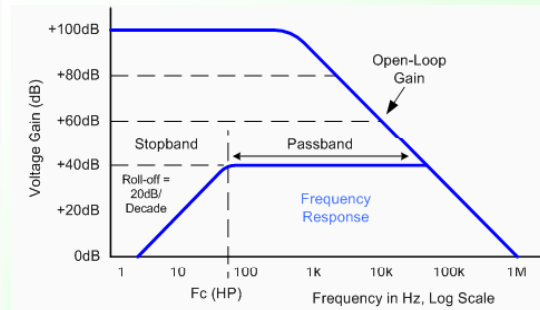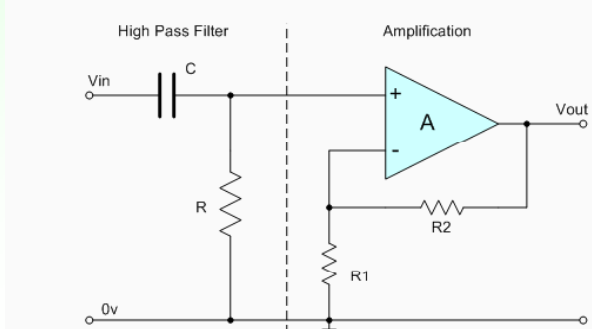


# Active Filters

## Band Pass Filter

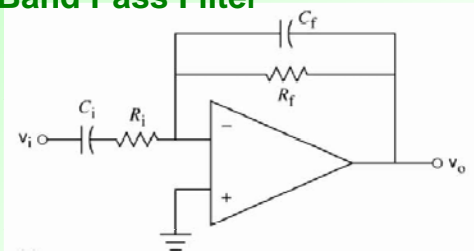


$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{j\omega R_f C_i}{(1 + j\omega R_f C_f)(1 + j\omega R_i C_i)}$$


## 2-stage Band Pass Filter

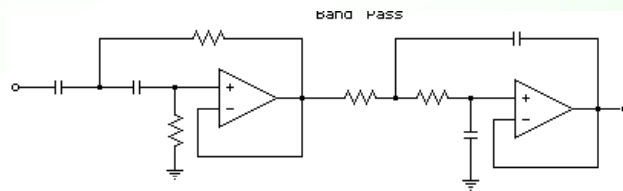
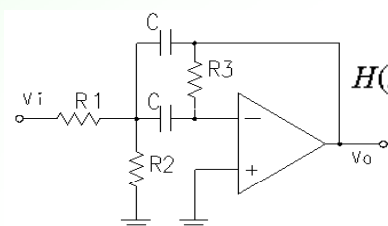
## High Q (narrow frequency) Band Pass Filter


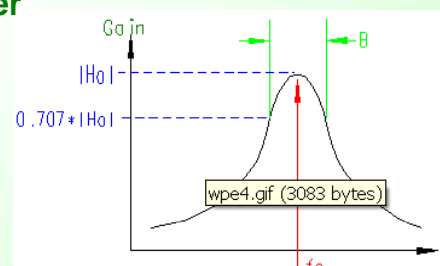
$$H(s) = \frac{V_o}{V_i} = \frac{H_0 \beta s}{s^2 + \beta s + \omega_0^2}$$



## Non-ideal Characteristics

- Offset voltage
  - output not zero when the inputs to the amplifiers are equal
    - could be in order of millivolts
  - cancel offset voltage by adding an external “nulling” potentiometer
- Temperature Drift
  - offset voltage can drift by 0.1 microvolts over one degree variation
- Finite (lower than infinite) input impedance
  - can cause errors at input
- High output impedance
  - limits load driving capabilities
- Noise
  - Thermal noise or high-frequency noise
  - Flicker noise: low-frequency noise

