

# Amplifiers and Analog Signal Processing

---

- Most bioelectric signals are small
  - voltages in micro-volts range
  - currents in pA and nA range common
- Small signals require amplification and filtering
  - op-amp, resistors and capacitors
  - integrated circuit and surface-mount technology
- Most modern signal processing tasks (filtering) are performed on a digital signal processor.
  - little change in amplification/filtering requirements over last 40 years
  - but new interest in putting DSP algorithms into analog circuits
    - due to demand for low power portable/implantable instruments

# Ideal Op-Amp

- Operational amplifier (op-amp) is a high-DC-gain differential amplifier
- Design circuits assuming op-amps are ideal
  - then verify/modify using simulations/prototyping
- Ideal op-amp model
  - “open loop” gain:  $A = \infty$
  - differential input resistance:  $R_d = \infty$
  - output resistance:  $R_o = 0$ 
    - input current = 0
  - output voltage:
    - $v_o = 0$  when  $v_1 - v_2 = 0$



*ideal op-amp*

$$A = \infty$$

$$v_o = 0$$

$$R_d = \infty$$

$$R_o = 0$$

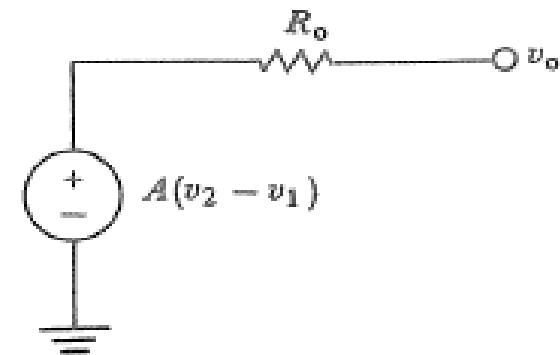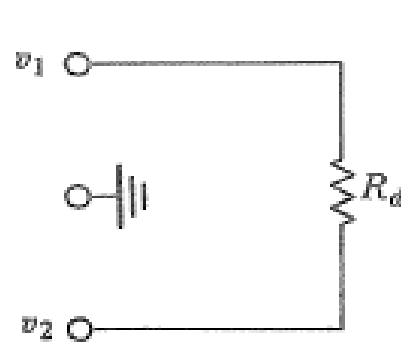

*ideal op-amp small signal model*

# Op-Amp Properties


## • Properties

- open-loop gain: ideally infinite: practical values 20k-200k
  - high open-loop gain  $\rightarrow$  virtual short between + and - inputs
- input impedance: ideally infinite: CMOS opamps are close to ideal
- output impedance: ideally zero: practical values 20-100 $\Omega$
- zero output offset: ideally zero: practical value  $< 1\text{mV}$
- gain-bandwidth product (GB): practical values  $\sim$  MHz
  - frequency where open-loop gain drops to 1 V/V

## • Commercial opamps provide many different properties

- low noise
- low input current
- low power
- high bandwidth
- low/high supply voltage
- special purpose: comparator, instrumentation amplifier

# Basic Op-Amp Principles

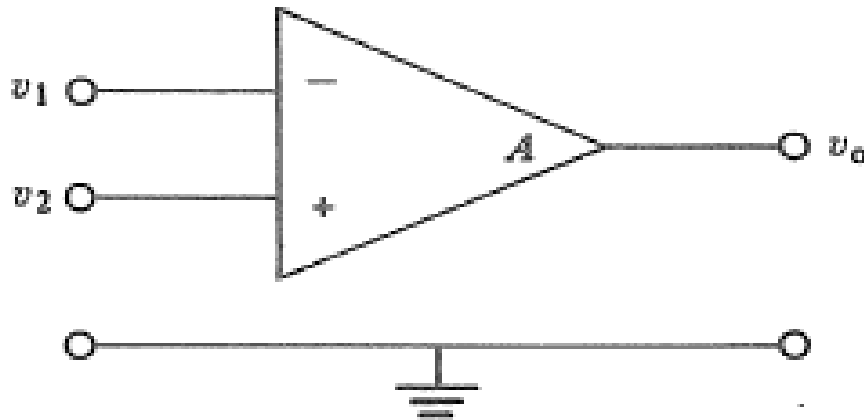


*typical op-amp schematic symbol*

$v_o, v_1, v_2$  referenced to ground


- Open loop gain:  $v_o = A (v_1 - v_2)$ 
  - since  $A$  is very large,  $v_1 - v_2$  must be very small
- When the op-amp output is in its linear range
  - two input terminals are at (essentially) the same voltage
  - i.e., “virtual ground” between op-amp inputs
    - rely on this for DC/bias calculations
- Single vs. Dual Supply Voltage
  - most modern ICs use single supply
    - “ground” in a dual supply becomes  $V_{DD}/2$  in single supply
      - mid way between  $V_{DD}$  and Ground
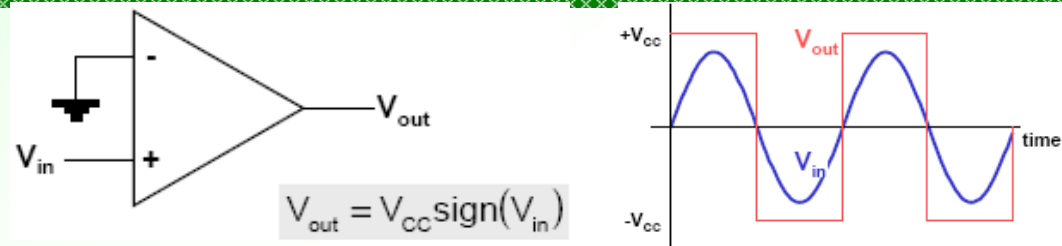
# Basic Opamp Configuration


- Voltage Comparator
  - digitize input
  - assumes very high DC gain
  - $V_{cc}$  = supply voltage



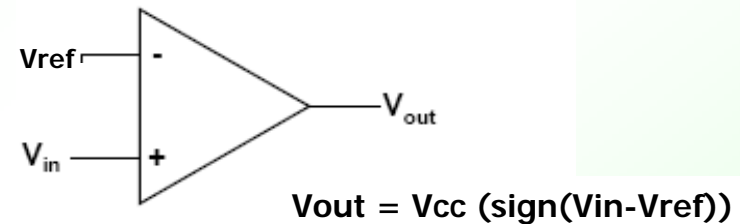- Negative Feedback
  - output tied back into negative input terminal
  - generally avoid positive feedback






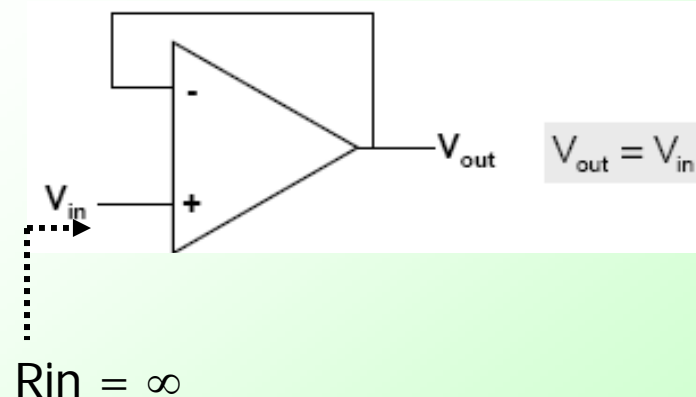- Voltage Follower
  - buffer
  - prevents input signal from being loaded down by a low-resistance load


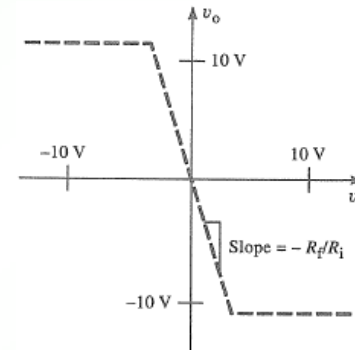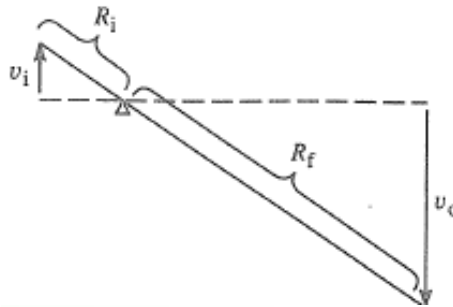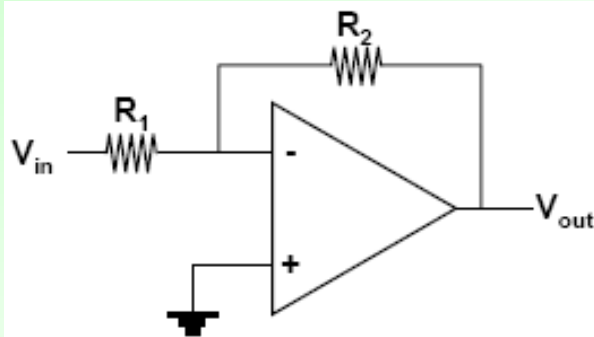
# Inverting/Non-Inverting Configurations



- Inverting Amplifier (uses negative feedback)



$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$$A = \frac{v_o}{v_i} = \frac{-R_f}{R_i}$$

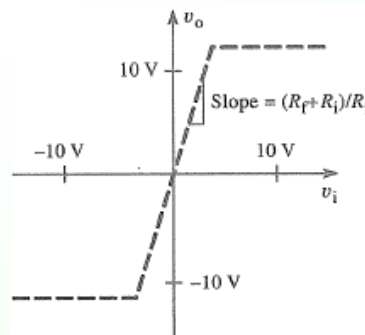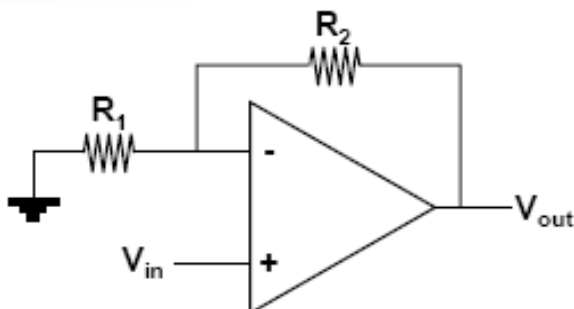- Non-Inverting Amplifier (also uses negative feedback)




$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$A = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_i} = \frac{R_i + R_f}{R_i}$$

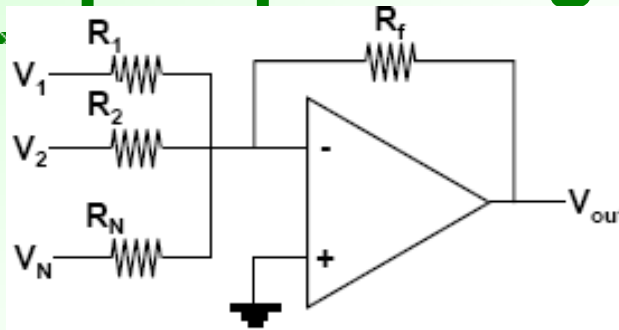
# More Opamp Configurations

- Summing Amp
  - weighted sum of multiple inputs
  - **inverting or non??**
- Differential Amp
  - match  $R_1$ s and  $R_2$ s
  - **inverting or non??**




$$V_{out} = - \left( V_1 \frac{R_f}{R_1} + V_2 \frac{R_f}{R_2} + \dots + V_N \frac{R_f}{R_N} \right)$$
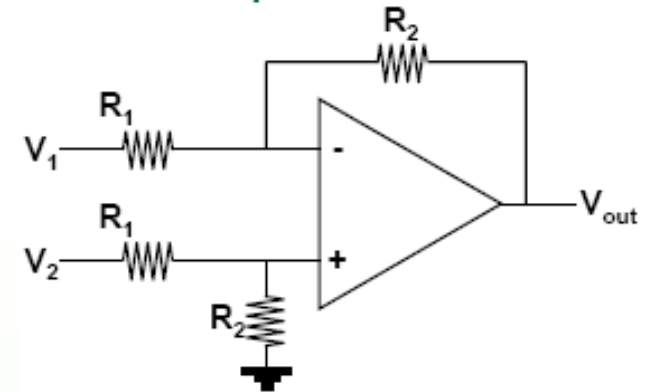
$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$



## Single-Ended Amplifier Representation

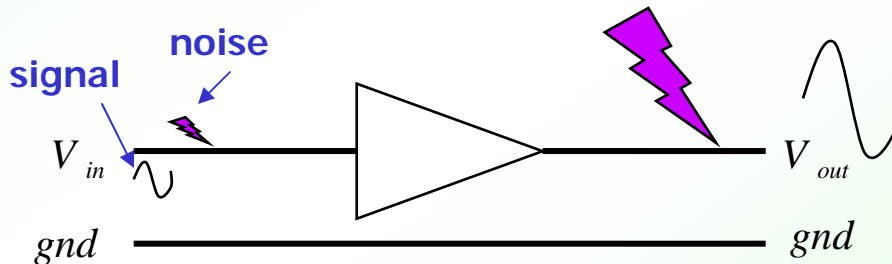


$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}}$$

## Noise Amplification


- even small interference at input gets amplified at output
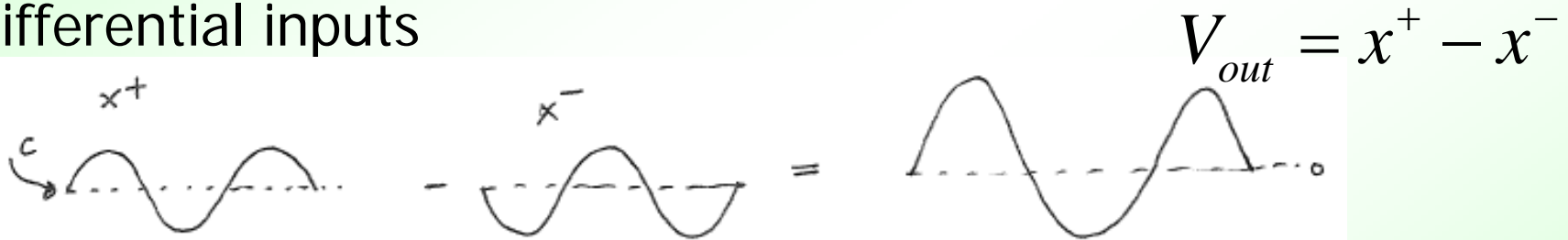
# Differential vs. Common Mode Signal

- Define
  - $x^+$  = input at + terminal
  - $x^-$  = input at - terminal
  - $c$  = common mode signal on both inputs
- Differential inputs



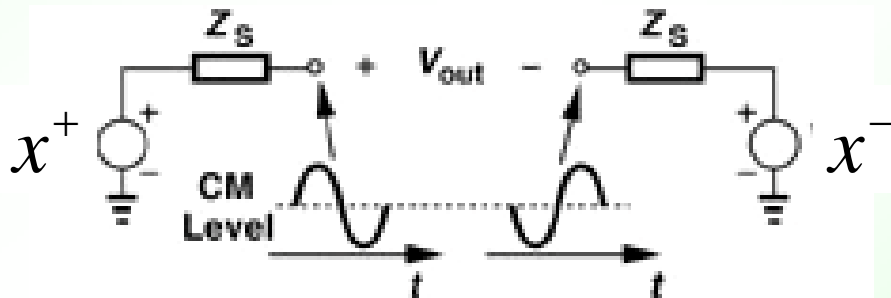- Add common mode input
  - $c$  rejected by differential amplifier (not amplified)
  - $c$  must be small enough to keep op-amp biased in linear operation





$$V_{out} = (x^+ + c) - (x^- + c)$$

$$c = \frac{x^+ + x^-}{2}$$

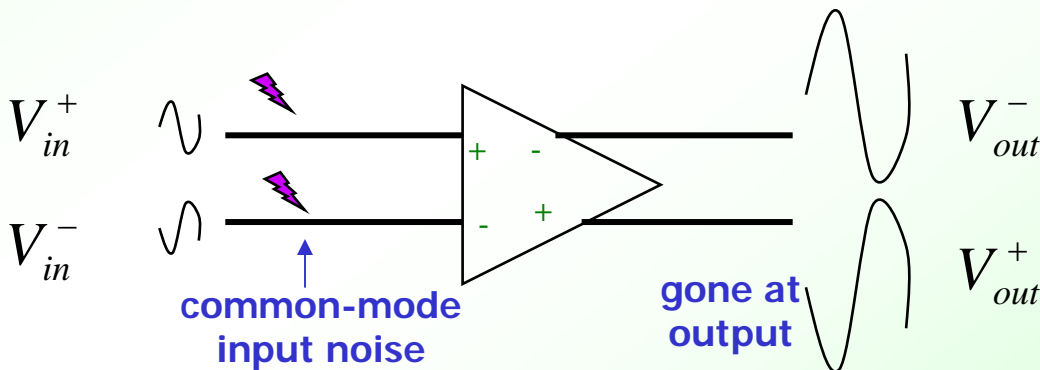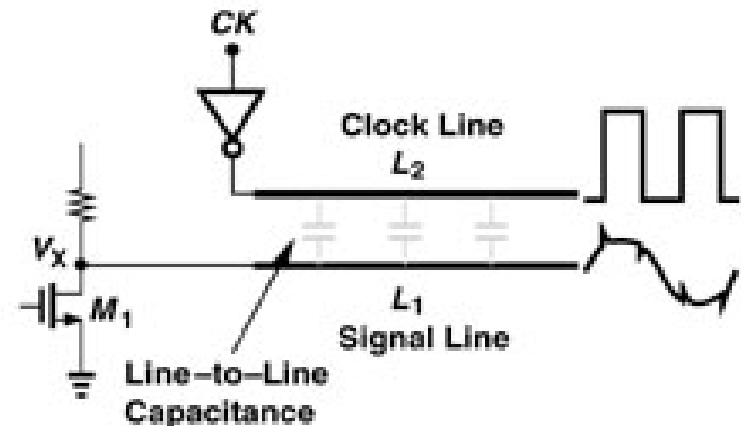
# Noise in Differential Amplifiers

- Global interference (e.g., supply voltage variations)
  - assumed to be located far away from amp. input terminals
    - same interference on both the terminals
  - appear as common mode disturbance.
  - example: clock noise
- Differential amplifiers
  - amplify only the difference
  - reject the interference (common-mode)



# Desirable Properties of Amplifiers


- High differential gain,  $A_v$

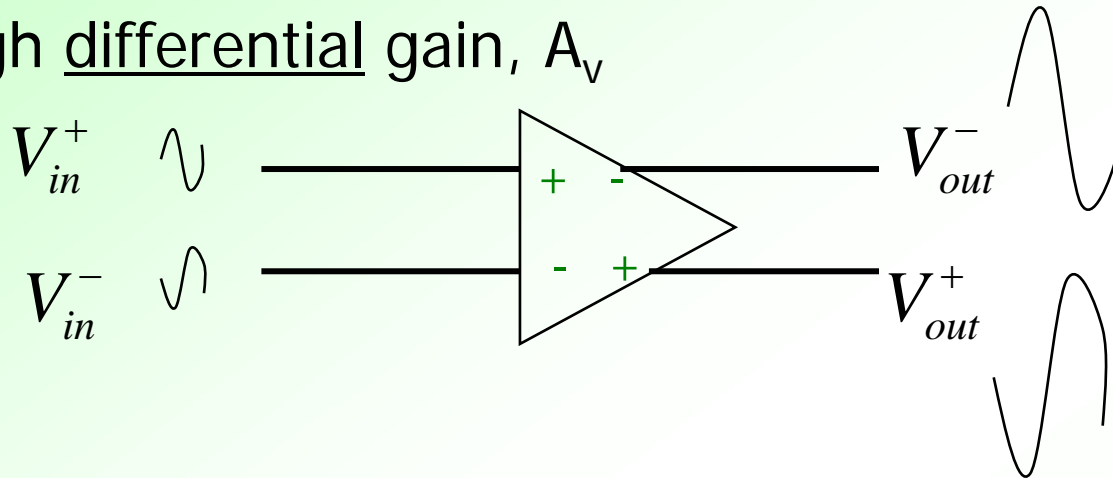

$$A_v = \frac{\Delta V_{out}^+ - \Delta V_{out}^-}{\Delta V_{in}^+ - \Delta V_{in}^-}$$

- Low common mode gain,  $A_{cm}$   
= high "common mode rejection"

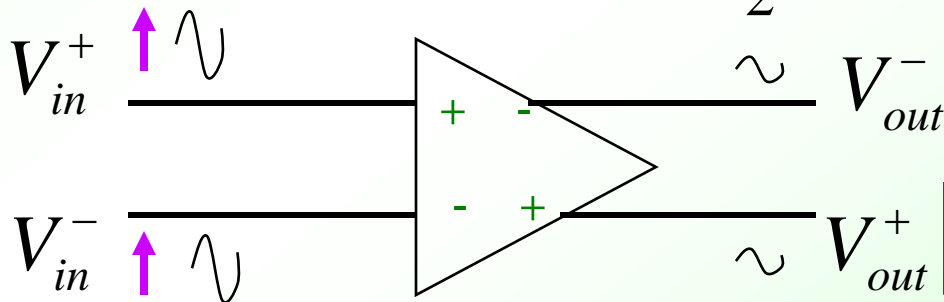**Common-mode signal**  $\frac{\Delta V_{in}^+ + \Delta V_{in}^-}{2}$




$$A_{CM} = \frac{\Delta V_{out}^+ - \Delta V_{out}^-}{\frac{\Delta V_{in}^+ + \Delta V_{in}^-}{2}}$$

common mode rejection ratio:  $CMRR = \frac{A_v}{A_{cm}}$
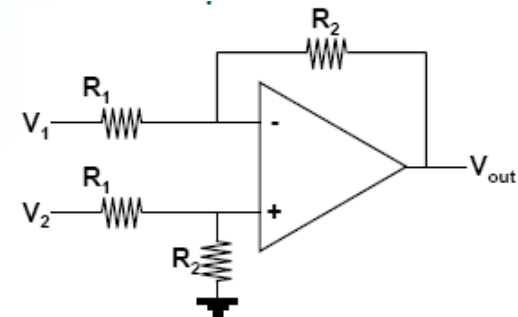
# 3-Op-Amp Instrumentation Amplifier


- Differential amplifiers
  - low common mode gain = Great!
  - lower than ideal input resistance – Bad!
- 3-op-amp structure
  - keeps low common mode gain
  - provides very high input resistance
    - why?
  - call “instrumentation amp”
    - will discuss in detail later




**total differential gain**

$$G_d = \frac{2R_2 + R_1}{R_1} \left( \frac{R_4}{R_3} \right)$$

$$A_{com} = 1$$

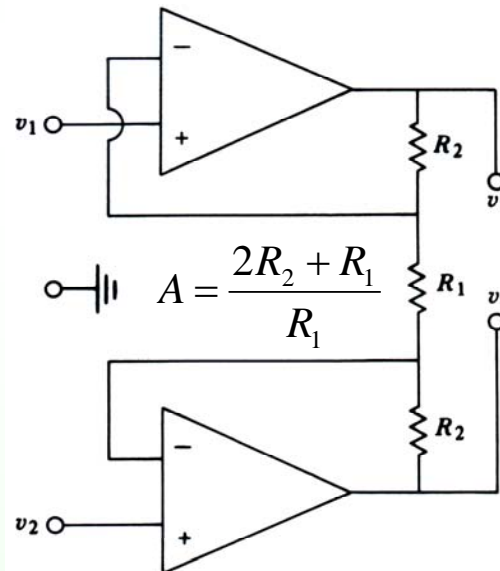


$$A = \frac{2R_2 + R_1}{R_1}$$

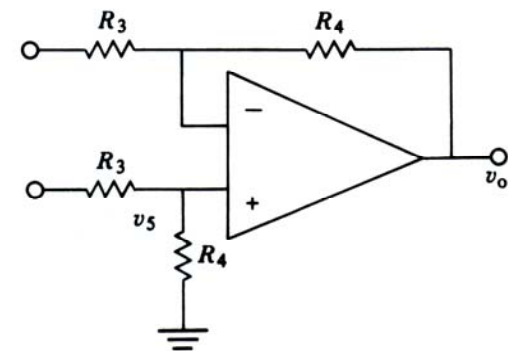

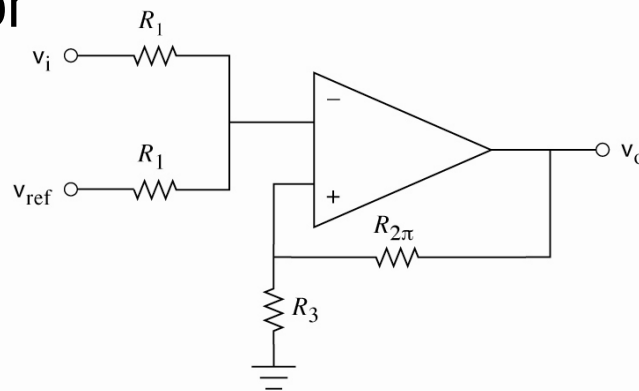
# Comparator

- Compare an input voltage  $v_i$  to a reference voltage  $v_{ref}$
- Output digital value (hi/low)
  - low if  $v_i > v_{ref}$  **why low and not hi?**
  - high if  $v_i < v_{ref}$
- Output voltage = supply voltage
- Op-amp comparator



(a)

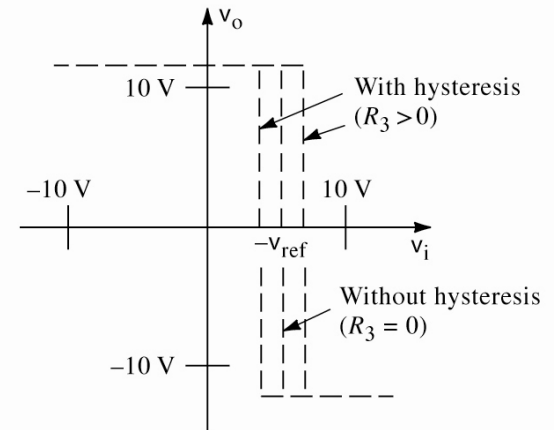

(b)


- Add hysteresis to improve noise immunity
  - hysteresis = rising transition point different than falling transition point
  - $R_3$  controls hysteresis

# Logarithmic Amplifiers


- Uses non-linear current-voltage relationship of BJT in feedback path

$$V_{BE} = k \log\left(\frac{I_C}{I_S}\right)$$

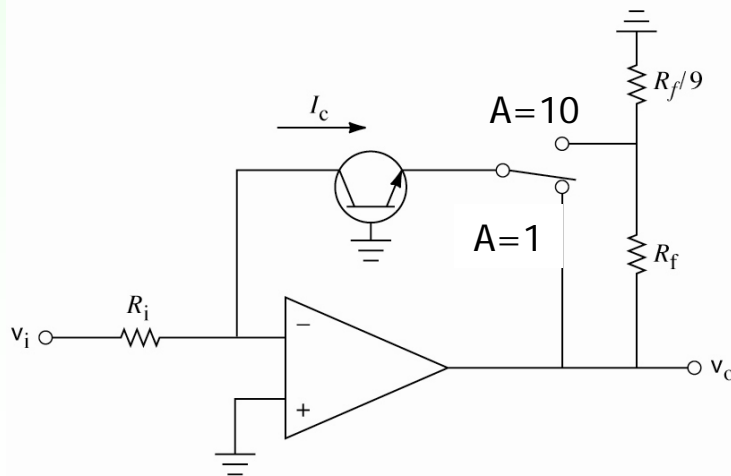- Useful for computing logarithms and anti-logs
  - for compressing and multiplying/dividing signals



(a)

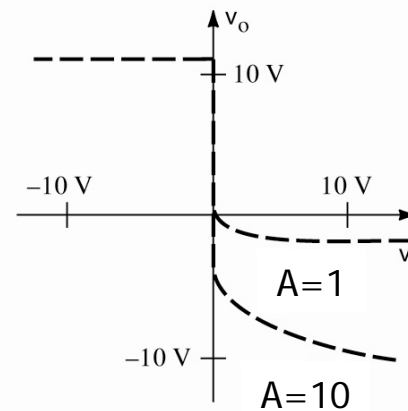


(b)

# Integrating/Differentiating Configurations

- Integrating Amp

$$v = \frac{1}{C} \int_0^t i dt$$

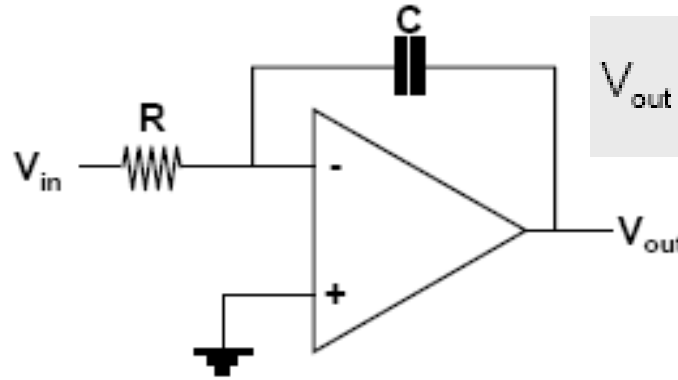


$$V_{out} = -\frac{1}{j\omega CR} V_{in} = -\frac{1}{RC} \int V_{in} dt$$

$$\omega = 2\pi f$$

- Differentiating Amp


$$i = C \frac{dv}{dt}$$

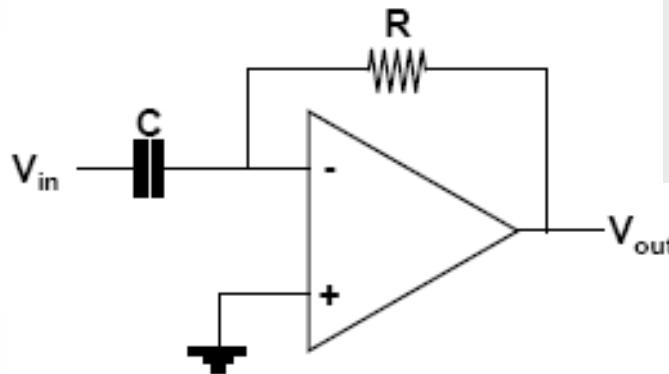

$$V_{out} = -\frac{R}{\frac{1}{j\omega C}} V_{in} = -RC \frac{dV_{in}}{dt}$$

# Converting Configuration


- Current-to-Voltage

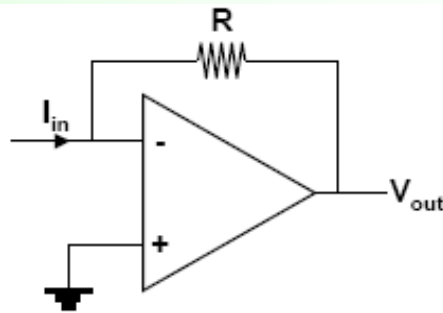

$$V_{out} = -I_{in}R$$


- Voltage-to-Current

$$I_L = \frac{V_{in}}{R}$$

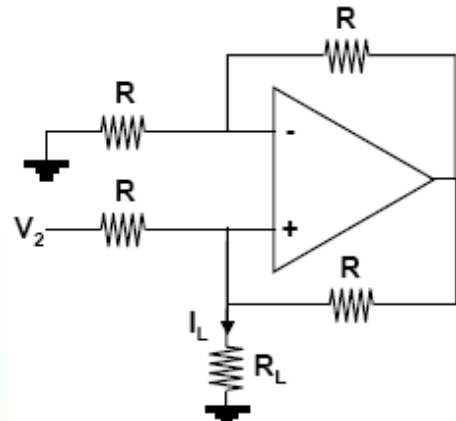

# Active Filters

- Passive low pass filter

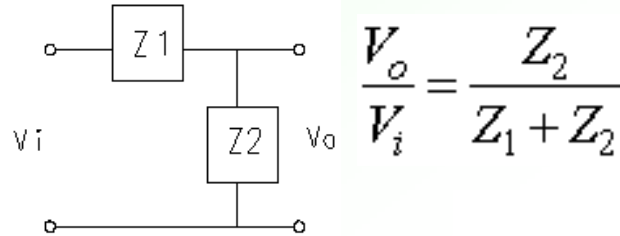


$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$

If Z1 is a resistor (R) and Z2 is a capacitor (1/sC) then

$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sCR}$$

- Active low pass filter

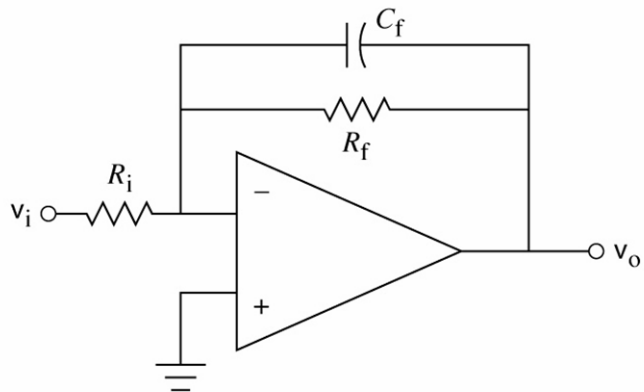

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{Z_f}{Z_i} = -\frac{(R_f / j\omega C_f)}{[(1 / j\omega C_f) + R_f]}$$

$$\omega_0 = 1 / R_f C_f$$


$$= -\frac{R_f}{(1 + j\omega R_f C_f) R_i} = -\frac{R_f}{R_i} \frac{1}{1 + s / \omega_0}$$

$$\frac{V_o}{V_i} = \frac{H_o \omega_0}{s + \omega_0}$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{1}{1 + j\omega R_f C_f}$$

# Active Filters



- Active high pass filter

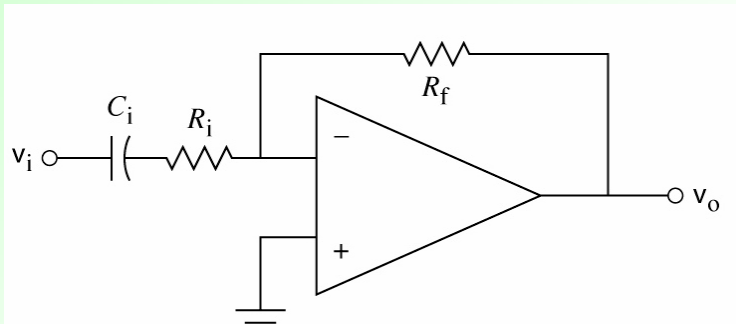

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{j\omega R_i C_i}{1 + j\omega R_i C_i}$$


$$\frac{V_o}{V_i} = H_0 \frac{s}{s + \omega_0} \quad \omega_0 = \frac{1}{R_i C_i}$$
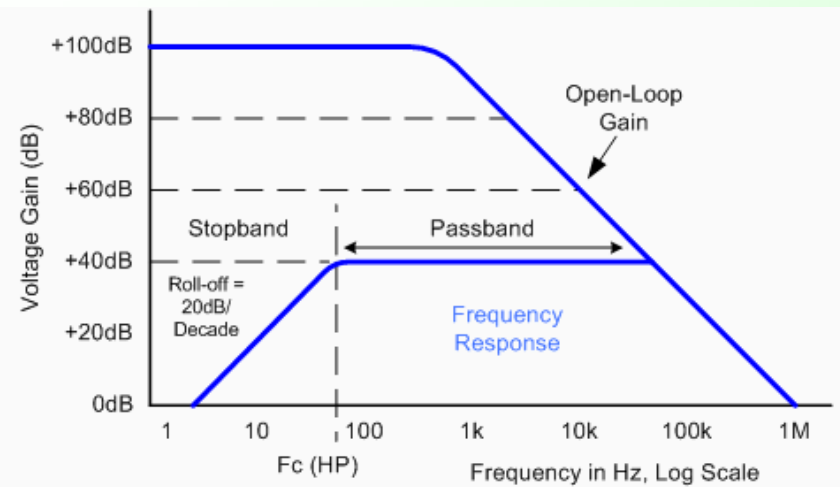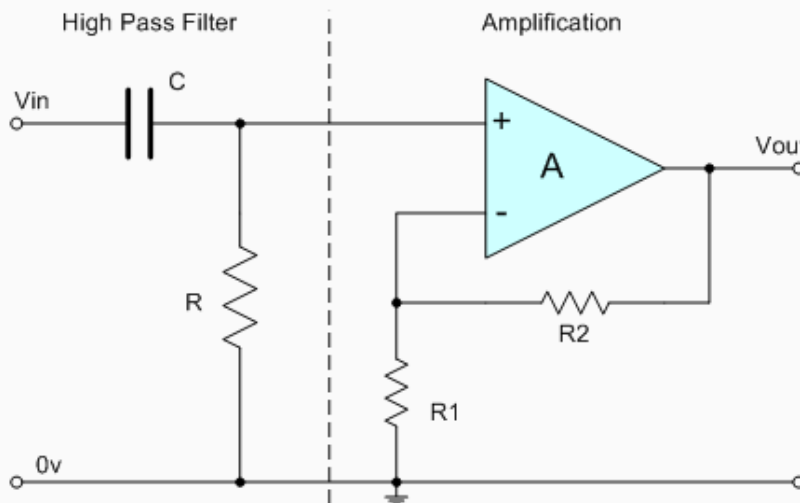
## First-order High Pass Butterworth Filter




# Active Filters

## Band Pass Filter

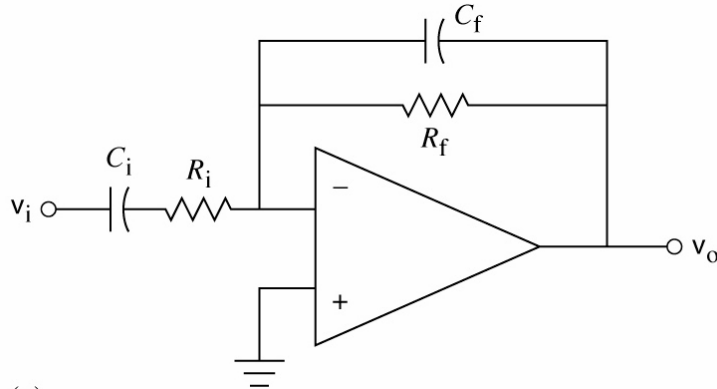


$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i} \frac{j\omega R_f C_i}{(1 + j\omega R_f C_f)(1 + j\omega R_i C_i)}$$


## 2-stage Band Pass Filter

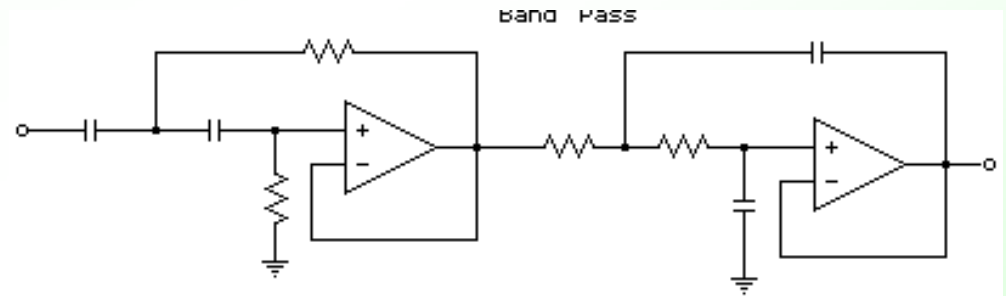
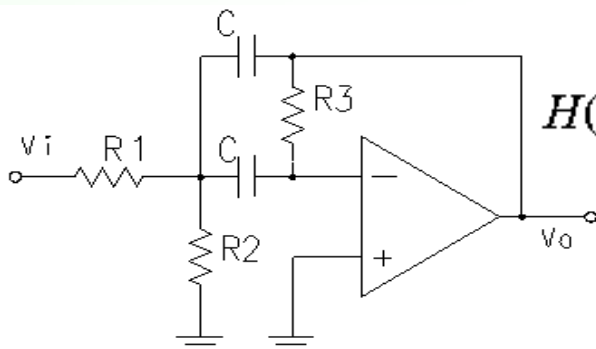
## High Q (narrow frequency) Band Pass Filter


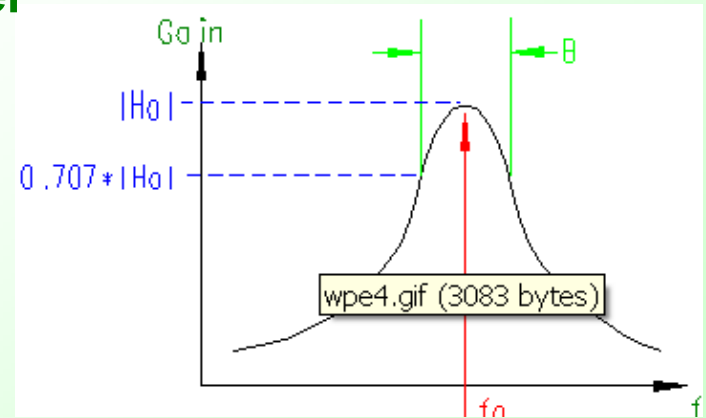
$$H(s) = \frac{V_o}{V_i} = \frac{H_o \beta s}{s^2 + \beta s + \omega_o^2}$$



# Non-ideal Characteristics

- Offset voltage
  - output not zero when the inputs to the amplifiers are equal
    - could be in order of millivolts
  - cancel offset voltage by adding an external “nulling” potentiometer
- Temperature Drift
  - offset voltage can drift by 0.1 microvolts over one degree variation
- Finite (lower than infinite) input impedance
  - can cause errors at input
- High output impedance
  - limits load driving capabilities
- Noise
  - Thermal noise or high-frequency noise
  - Flicker noise: low-frequency noise

