
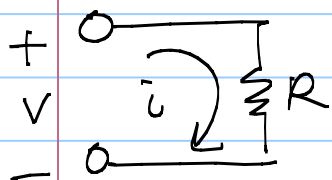


Electric Circuits

Resistor

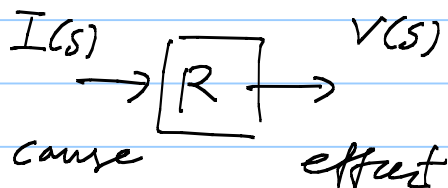


$$v = iR$$



$$: V(s) = RI(s)$$

Capacitor

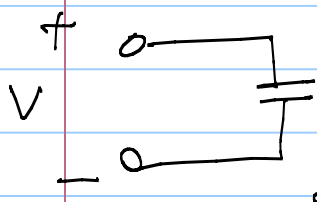


$$\begin{cases} q = CV \\ i = C \frac{dv}{dt} \end{cases}$$


$$V = \frac{1}{C} \int_0^t i dt + V_0$$

$$V(s) = \frac{1}{Cs} I(s)$$

$$V_0 = 0$$

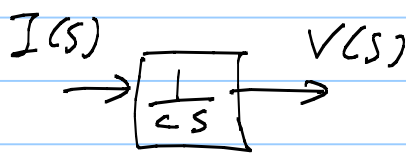


Inductor

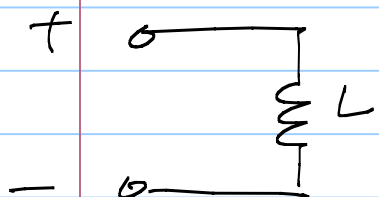

$$V = L \frac{di}{dt}$$


$$V(s) = sL I(s)$$

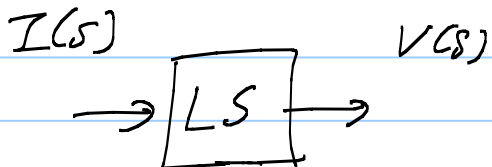



Impedance

Take Z of elements

$$V(s) = Z(s) I(s)$$

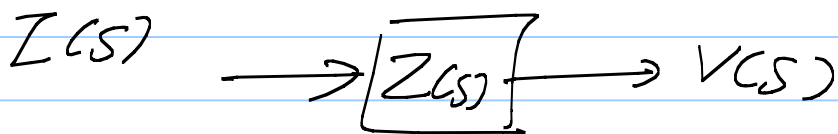

| | time domain | s-domain |
|---|-----------------------------|--|
| R | $v = iR$ | $V(s) = \textcircled{R} I(s)$ |
| L | $v = L \frac{di}{dt}$ | $V(s) = \textcircled{sL} I(s)$ |
| C | $v = \frac{1}{C} \int i dt$ | $V(s) = \textcircled{\frac{1}{Cs}} I(s)$ |

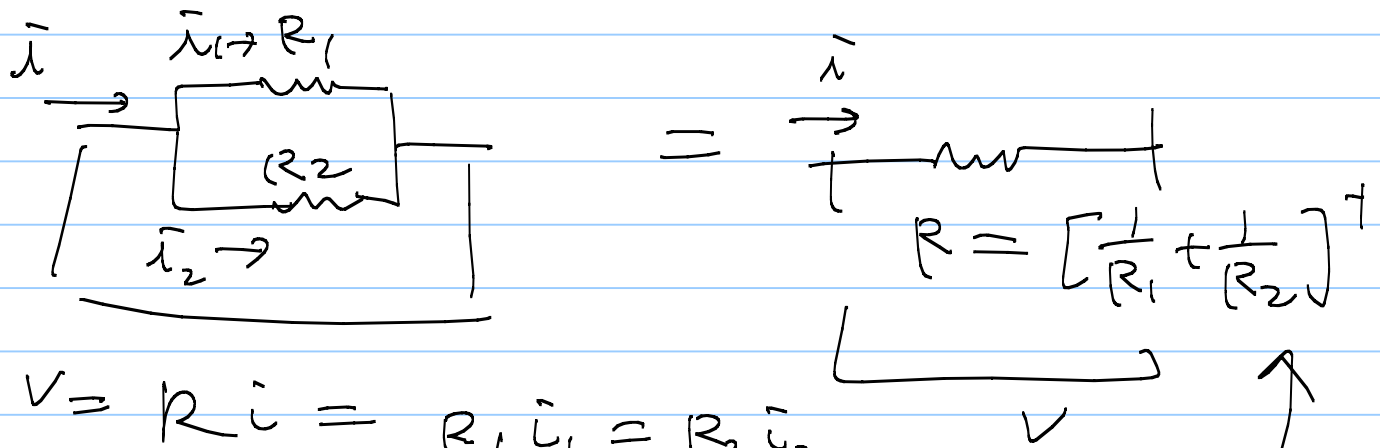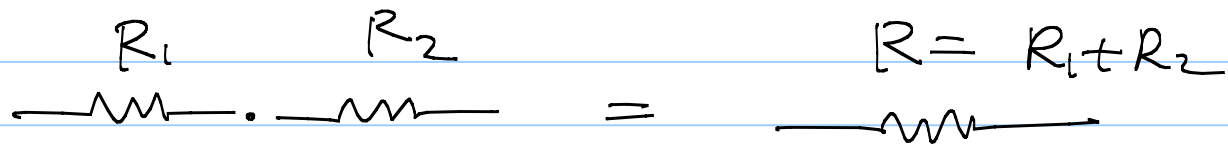


$$v = R \bar{i} = R_1 \bar{i}_1 = R_2 \bar{i}_2$$

$$\bar{i}_1 = \frac{v}{R_1} \quad \bar{i}_2 = \frac{v}{R_2}$$

$$\begin{aligned}
 v &= R \bar{i} = R (\bar{i}_1 + \bar{i}_2) \\
 &= R v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)
 \end{aligned}$$

Low-pass filter

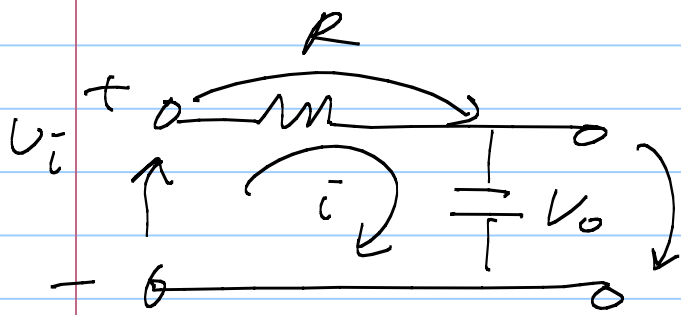

KCL Voltage Law

$$V_i - iR - V_o = 0$$

$$V_o = \frac{1}{C} \int_0^t i dt$$


$$i = C \frac{dV_o}{dt}$$

$$V_i - \left(RC \cdot \frac{dV_o}{dt} \right) - V_o = 0$$

\mathcal{L}

$$\overline{V_i}(s) - RC s \overline{V_o} - \overline{V_o}(s) = 0$$

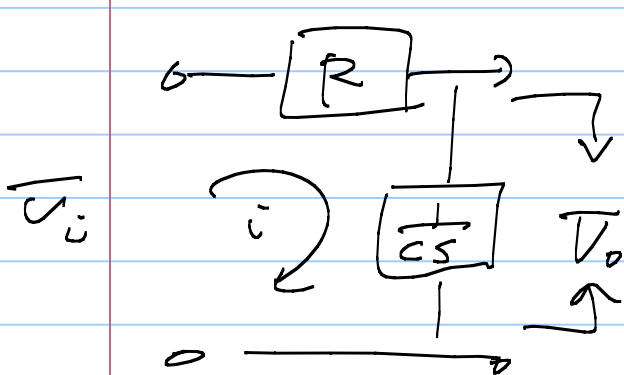
$$\frac{\overline{V_o}(s)}{\overline{V_i}(s)} = \frac{1}{(RCs + 1)}$$



$$\overline{V_o}(s) = \left[\frac{1}{Cs} \right] I(s)$$

$$\overline{V_i}(s) = \left(R + \frac{1}{Cs} \right) I(s)$$
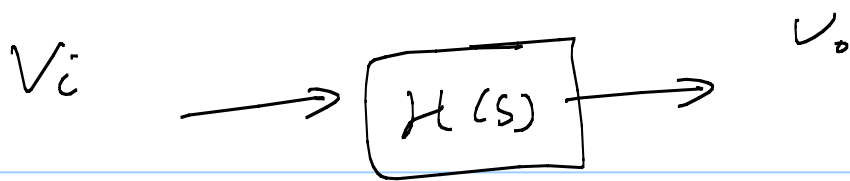
$$\frac{\overline{V_o}(s)}{\overline{V_i}(s)} = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{1}{RCs + 1}$$




Take $v_i = e^{j\omega t} = \cos \omega t + j \sin \omega t$

$$v_o = H(j\omega) e^{j\omega t}$$

$$= \frac{1}{RS(j\omega) + 1} e^{j\omega t}$$
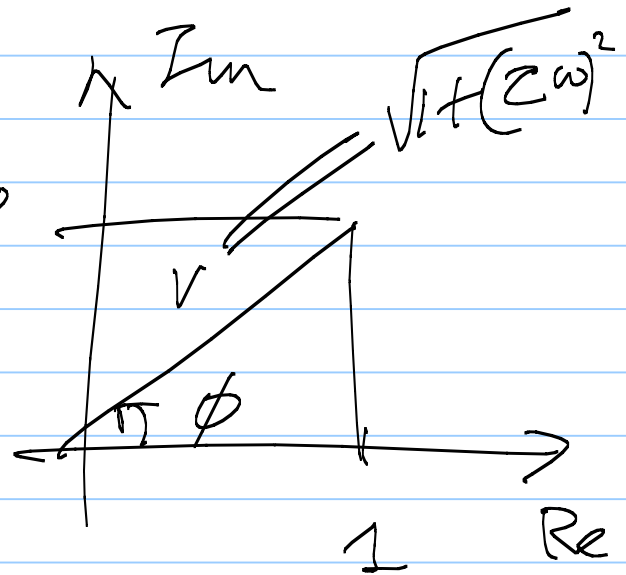
$$\Rightarrow \frac{1}{R Z j\omega + 1}$$




$$\Rightarrow \frac{1}{\sqrt{1 + (Z\omega)^2}} e^{j\phi}$$

$$= \frac{e^{-j\phi}}{\sqrt{1 + (Z\omega)^2}} e^{j\omega t}$$


$$= \frac{1}{\sqrt{1 + Z^2 \omega^2}} \left(e^{j(\omega t - \phi)} = \cos(\omega t - \phi) + j \sin(\omega t - \phi) \right)$$

High-pass - filter

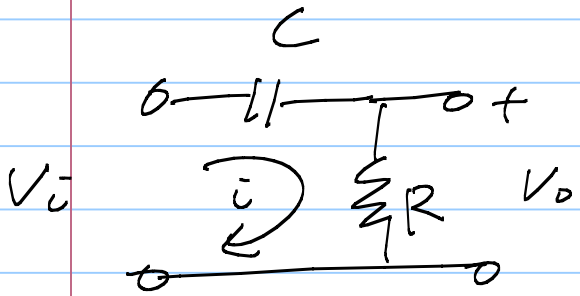

$$V_o = R I(s)$$
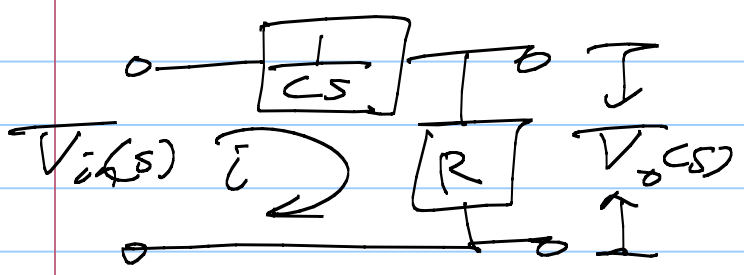
$$V_i = \left(\frac{1}{Cs} + R \right) I(s)$$



$\frac{1}{Cs}$ Voltageren


$$\frac{V_o}{V_i} = \frac{R}{\frac{1}{Cs} + R} = \frac{RCS}{RCS + 1}$$

$H(s)$

$$v_i = e^{j\omega t} = \cos \omega t + j \sin \omega t$$


$$v_o = H(j\omega) e^{j\omega t}$$
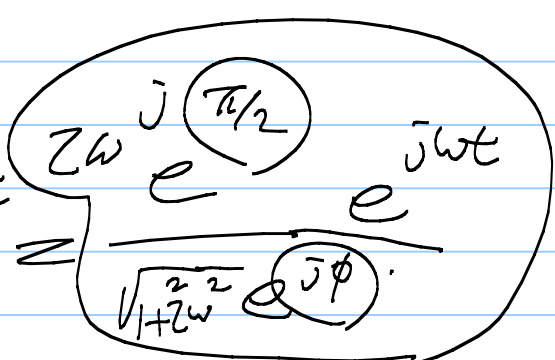
$$= \frac{RCj\omega}{RCj\omega + 1} e^{j\omega t}$$



$$Z = RC$$
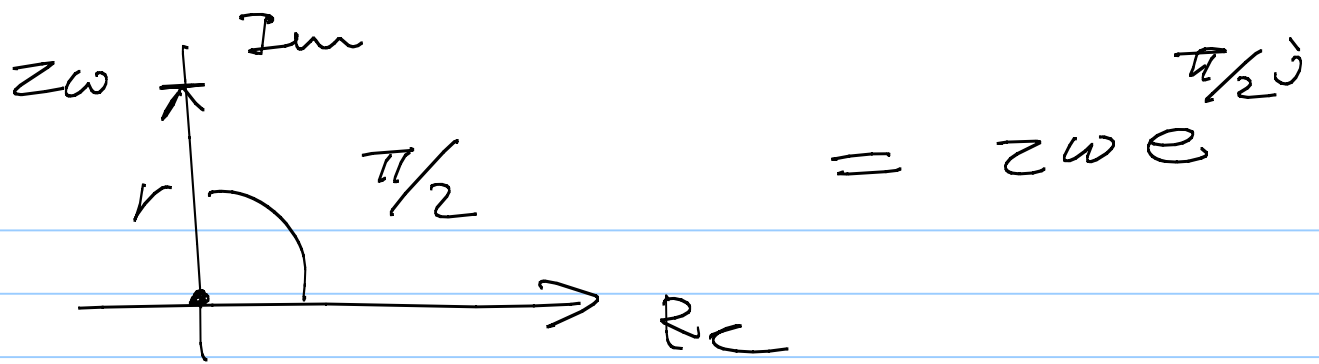
$$= \frac{Z\omega}{\sqrt{1+Z^2\omega^2}} e^{j(\pi/2 - \phi)}$$



$$v_o = \frac{z\omega}{\sqrt{1+z^2\omega^2}} e^{j(\omega t + \pi/2 - \phi)}$$

$$= \frac{z\omega e^{j\pi/2}}{\sqrt{1+z^2\omega^2}} e^{j\omega t}$$

$$= \frac{z\omega}{\sqrt{1+z^2\omega^2}} \left[\cos(\omega t + \pi/2 - \phi) + j \sin(\omega t + \pi/2 - \phi) \right]$$