

$$G(s) = \frac{V_2(s)}{V_1(s)} = ?$$

③

Loop 1:  $-V_1 = R_1 i_1 + R_2 (i_1 - i_2)$

Loop 2:  $-V_1 = R_1 i_1 + (R_3 + Ls) i_2$


$$\Rightarrow \begin{bmatrix} R_1 + R_2 & -R_2 \\ R_1 & R_3 + Ls \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -V_1 \\ -V_1 \end{bmatrix} \Rightarrow i_2 = \frac{\begin{vmatrix} R_1 + R_2 & -V_1 \\ R_1 & -V_1 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ R_1 & R_3 + Ls \end{vmatrix}} =$$

applying Cramer's rule

$$= \frac{-R_2 V_1}{L_1 (R_1 + R_2) s + R_1 R_3 + R_2 R_3 + R_1 R_2} \Rightarrow -V_1 = \frac{L_1 (R_1 + R_2) s + R_1 R_3 + R_2 R_3 + R_1 R_2}{R_2} i_2$$

$$V_2 = -R_3 i_2$$
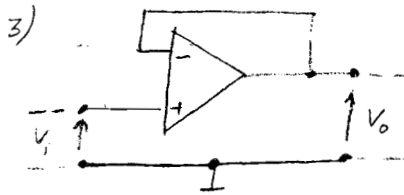
$$\Rightarrow G(s) = \frac{V_2(s)}{-V_1(s)} = \frac{R_3 \cdot R_2}{L_1 (R_1 + R_2) s + R_1 R_3 + R_2 R_3 + R_1 R_2}$$




$$G(s) = \frac{V_o(s)}{V_i(s)} = ?$$

①

$$V_+ = V_i, V_+ = V_- \text{ (for op-amp), } \Rightarrow$$

$$\Rightarrow V_- = V_i, V_o = V_- \Rightarrow V_o = V_i \Rightarrow$$
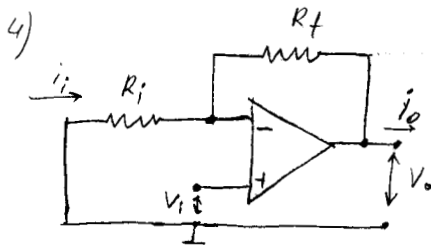
$$G(s) = \frac{V_o}{V_i} = \frac{V_i}{V_i} = 1$$



$$G(s) = \frac{V_o}{V_i} = ?$$

①

$$V_+ = V_i$$

$$V_o = V_- = i_o R_f, V_- = -R_i \cdot i_i \Rightarrow$$

$$V_o = -R_i i_i = -R_f i_o$$

$$\text{for op-amp } i_o = i_i, V_+ = V_- \Rightarrow G(s) = \frac{V_o}{V_i} = \frac{-R_i i_i - R_f i_i}{-R_i i_i} = 1 + \frac{R_f}{R_i}$$