

Name: Solutions

Student ID: _____

ECE 202 EXAM 3

April 13, 2007

- No textbooks, notes or HW solutions.
- Calculators are allowed.
- Exam is 50 minutes.
- To maximize your score on this exam, read the questions carefully and write legibly. For those problems that allow partial credit, show your work clearly.
- Good luck.

1. [25] Answer the following questions briefly.

- a) For a circuit with impulse response $h(t) = e^{-2t}u(t)$, find the output to the input $x(t) = u(t)$ using the convolution integral.

$$y(t) = \int_0^t e^{-2(t-\tau)} d\tau = e^{-2t} \int_0^t e^{2\tau} d\tau$$
$$= e^{-2t} \left. \frac{e^{2\tau}}{2} \right|_0^t = e^{-2t} \left[\frac{e^{2t}}{2} - \frac{1}{2} \right] = \left[\frac{1}{2} - \frac{1}{2} e^{-2t} \right] u(t)$$

- b) For a RLC bandpass circuit, which element would you adjust (and by how much) to double the bandwidth without changing the center frequency?

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
$$BW = \frac{\omega_0}{Q_0} \rightarrow \text{double BW} \rightarrow \text{half } Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Double R

- c) For a circuit with transfer function, $T(s) = \frac{2000(s+200)}{(s+1000)(s-400)}$, determine whether the circuit is stable or not. Explain why.

poles at -1000 and 400

Not stable since not all of the poles are in the LHP.

- d) A voltage source of $v(t) = 10 \cos(100t)$ is applied to a lowpass filter with a transfer function $T(s) = \frac{100}{s+10}$. Predict the output voltage $v_o(t)$.

Hint: Use Bode diagrams to estimate the gain and the phase at the input frequency.

$$\frac{100}{j\omega + 10} = \frac{100}{10} \frac{1}{1 + j\frac{\omega}{10}} = (10) \left(\frac{1}{1 + j\frac{\omega}{10}} \right)$$

$20 \log_{10} 10 = 20 \text{ dB}$
 gain at $\omega = 100 \rightarrow 0 \text{ dB} = 1 \cdot |T(j\omega)|$
 phase at $\omega = 100 \rightarrow -90^\circ$
 $v_o(t) = 10 \cos(100t - 90^\circ)$

- e) The first three terms in the Fourier series expansion of a periodic signal is

$f(t) = \frac{8}{\pi^2} \cos(100\pi t) + \frac{8}{9\pi^2} \cos(300\pi t) + \frac{8}{25\pi^2} \cos(500\pi t) + \dots$ Determine the fundamental frequency in Hz.


$$100\pi = 2\pi f_0$$

$f_0 = 50 \text{ Hz}$

2. [25] Given the following inverting amplifier:

a) [12] Find the transfer function, $T(s)$.

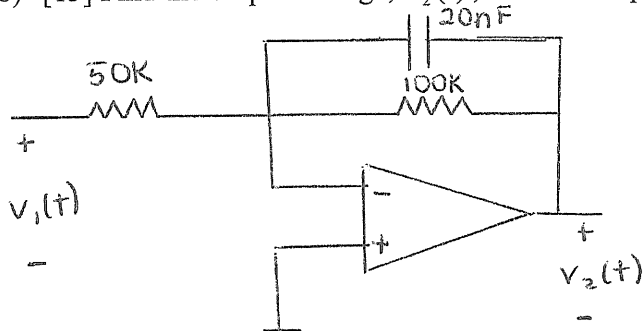b) [13] Find the output voltage, $v_2(t)$, when the input is $v_1(t) = u(t)$.



$$a) T(s) = -\frac{Z_2}{Z_1} = -\frac{(100K \parallel \frac{1}{s20 \times 10^{-9}})}{50K}$$

$$= -\frac{\frac{100 \times 10^3}{s20 \times 10^{-9}}}{\frac{100 \times 10^3 + 20 \times 10^{-9}}{s}} = -\frac{100 \times 10^3}{50 \times 10^3} \frac{s}{1 + s2 \times 10^{-3}}$$

$$= -\frac{2}{1 + s2 \times 10^{-3}}$$

$$= -\frac{1000}{s + 500}$$

$$b) v_2(s) = \left(\frac{1}{s}\right) \left(\frac{-1000}{s+500}\right) = \frac{k_1}{s} + \frac{k_2}{s+500}$$

$$k_1 = -2$$

$$k_2 = 2$$


$$v_2(t) = -2u(t) + 2e^{-500t}u(t)$$

3. [25] Given the network function $T(s) = \frac{1000s}{(s+10)(s+100)}$, construct the Bode plot for $|T(j\omega)|$ and $\angle T(j\omega)$ with respect to frequency. The magnitude plot should be in terms of dBs and the phase plot in terms of degrees. Label your axis carefully. Determine whether this is a lowpass, highpass, bandpass or bandstop filter.


$$T(j\omega) = \frac{1000 j \omega}{(j\omega + 10)(j\omega + 100)}$$

$$= \frac{1000}{(10)(100)} j\omega \left(\frac{1}{1 + \frac{j\omega}{10}} \right) \left(\frac{1}{1 + \frac{j\omega}{100}} \right)$$

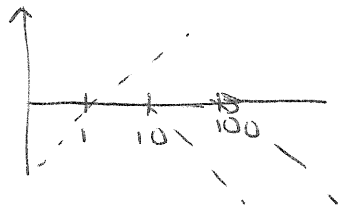
$$= \underbrace{(1)}_{\text{I}} \underbrace{(j\omega)}_{\text{II}} \underbrace{\left(\frac{1}{1 + \frac{j\omega}{10}} \right)}_{\text{V}} \underbrace{\left(\frac{1}{1 + \frac{j\omega}{100}} \right)}_{\text{VI}}$$




⇒

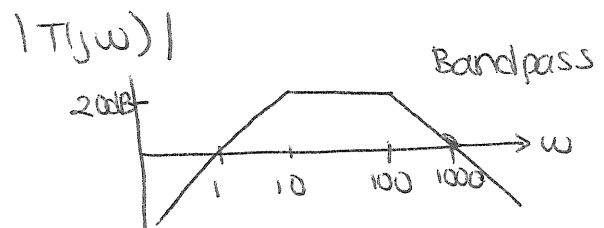


$$\angle T(j\omega)$$

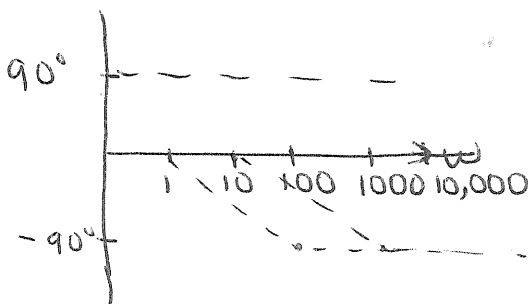

$$\angle T(j\omega)$$

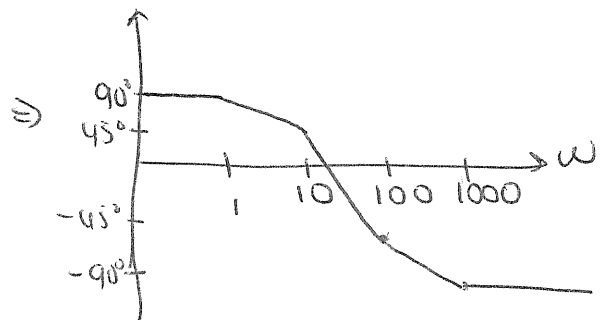

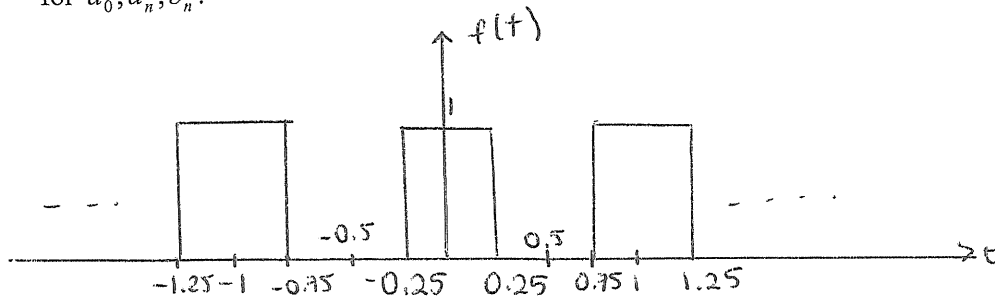4. [25] For the following rectangular wave with amplitude 1 V and period 1 sec:
- [5] Determine whether the signal has odd symmetry or even symmetry.
 - [20] Determine the Fourier series coefficients for this signal, i.e. find expressions for a_0, a_n, b_n .



a) Even symmetry.

b) $b_n = 0$ since even symmetric

$$a_0 = \int_{-0.25}^{0.75} 1 dt = 0.5 //$$

$$f_0 = \frac{1}{T_0} = 1 \text{ Hz}$$

$$a_n = 2 \int_{-0.25}^{0.25} \cos(2\pi n f_0 t) dt = \frac{2 \sin(2\pi n f_0 t)}{2\pi n f_0} \Big|_{-0.25}^{0.25}$$

$$= 2 \left[\frac{\overset{-\sin(0.5\pi n)}{\sin(0.5\pi n)} - \sin(-0.5\pi n)}{2\pi n} \right] = 2 \left[\frac{2 \sin(0.5\pi n)}{2\pi n} \right]$$

$$a_n = \frac{2 \sin(0.5\pi n)}{\pi n}$$