

ECE 435
Homework Set #1
Fall 2002

Kempel

Due: 9/11/02

All homework must be completed NEATLY!!! (If I can't read it, I can't grade it!)

1. A 4-port network has the following scattering matrix

$$\begin{bmatrix} 0.1\angle 90^\circ & 0.6\angle -45^\circ & 0.6\angle 45^\circ & 0 \\ 0.6\angle -45^\circ & 0 & 0 & 0.6\angle 45^\circ \\ 0.6\angle -45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.6\angle 45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix}$$

- (a) Is this network lossless?
(b) Is this network reciprocal?
(c) What is the reflection coefficient at port 1 if a short circuit is placed at the terminal plane of port 3 and all other ports are match loaded?
2. The scattering matrix for a two-port network is given below, what are the equivalent impedance parameters if the characteristic impedance is 50Ω ?

$$\begin{bmatrix} 0.3 + j0.7 & j0.6 \\ j0.6 & 0.3 - j0.7 \end{bmatrix}$$

3. Consider two 2-port networks, $[S^A]$ and $[S^B]$, show that the over-all S_{21} of the cascade network is given by $S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$.
4. For a lossless 2-port network: (a) if the network is reciprocal, show $|S_{21}|^2 = 1 - |S_{11}|^2$ and (b) if the network is nonreciprocal, show that it is impossible to have unidirectional transmission (e.g. $S_{12} = 0$ and $S_{21} \neq 0$).