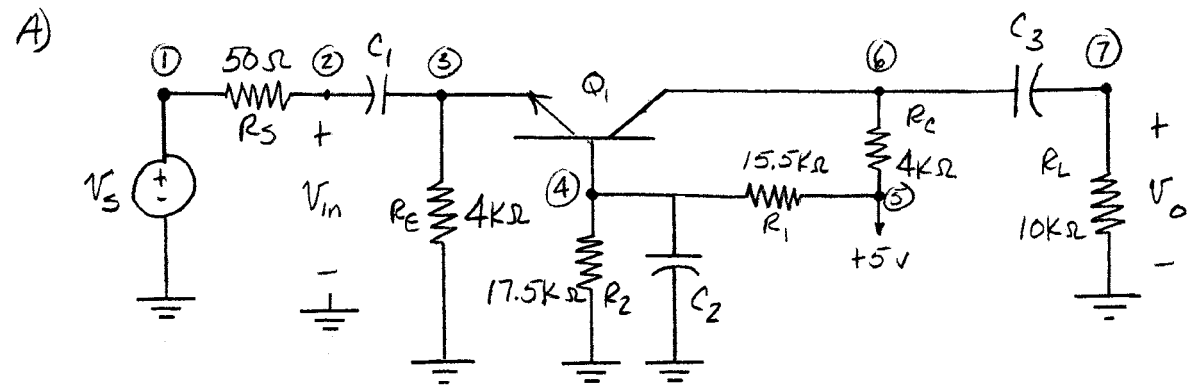


ECE 302 - HW #11 - SOLUTION - 30 PTS



Common-Base Amplifier

```

VCC 5 0 5
R1 5 4 15.5K
R2 4 0 17.5K
RC 5 6 4K
RE 3 0 4K
RS 1 2 50
RL 7 0 10K
C1 2 3 47U
C2 6 7 47U
CE 4 0 47U
VS 1 0 AC 1M
Q1 6 4 3 Q2N3904
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03
+ Bf=416.4 Ne=1.259 Ise=6.734f Ikf=66.78m Xtb=1.5
+ Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1 Cjc=3.638p Mjc=.3085
+ Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10
.AC DEC 25 1 100MEG
.OP
.PROBE
.END


```

- .OP


**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q1
MODEL	Q2N3904
IB	4.03E-06
IC	4.89E-04
VBE	6.47E-01
VBC	-4.26E-01
VCE	1.07E+00
BETADC	1.21E+02
GM	1.88E-02
RPI	7.51E+03
RX	1.00E+01
RO	1.52E+05
CBE	1.20E-11
CBC	3.17E-12
CJS	0.00E+00
BETAAC	1.41E+02
CBX/CBX2	0.00E+00
FT/FT2	1.96E+08

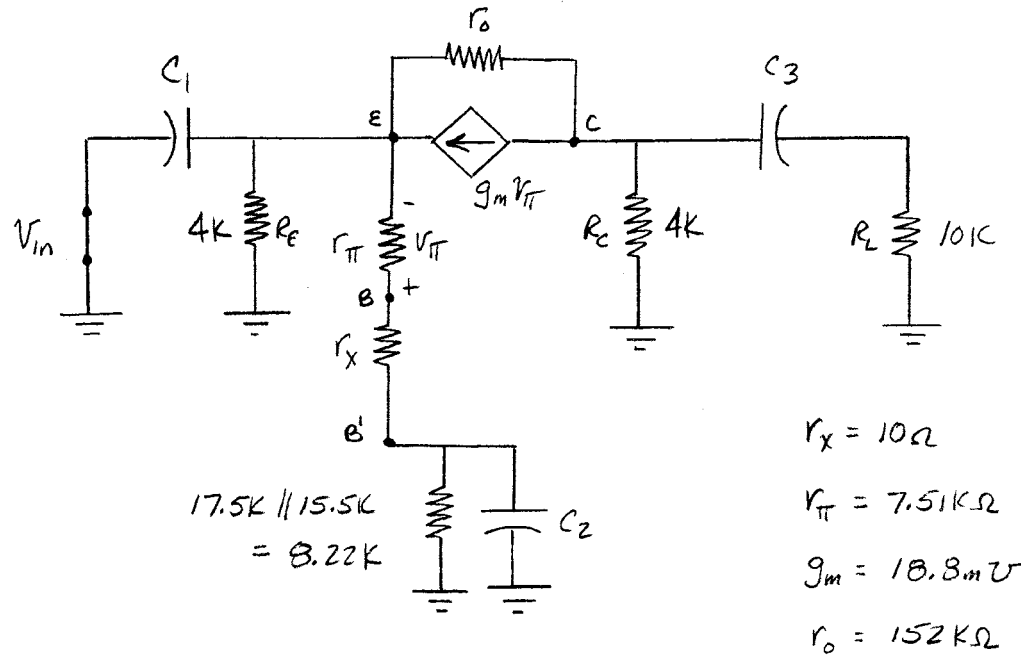B) Low FREQ. MODEL WITH V_{in} SHORTED (IGNORE R_E)




1) \uparrow_{SC_1} (SHORT C_2, C_3)

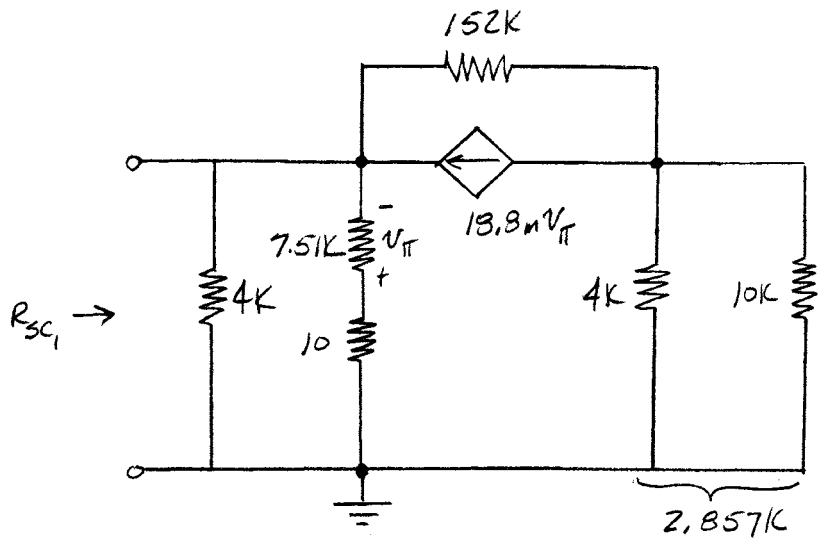


- DOING A SOURCE TRANSFORMATION
 $V = (18.8 m V_{\pi}) 152K = 2.8576 K V_{\pi}$
 $R_{EQ} = 152K + 2.857K = 154.857K$
- TRANSFORMING AGAIN
 $i = (2.8576K V_{\pi}) / 154.857K = 18.453 m V_{\pi}$

- RESULTING CIRCUIT

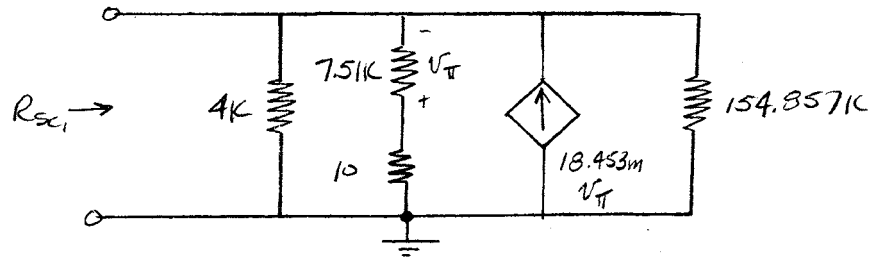

$$4k \parallel 154.857k = 3.9k$$

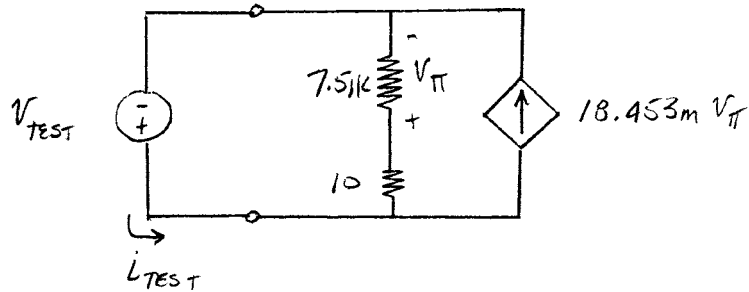

$$\begin{aligned} I_{TEST} &= 18.453m V_{\pi} + \frac{V_{\pi}}{7.51k} \\ &= 18.586m V_{\pi} \end{aligned}$$

$$V_{\pi} = V_{TEST} \frac{7.51k}{7.51k + 10} = 0.9987 V_{TEST}$$



$$\therefore I_{TEST} = 18.586m (0.9987) V_{TEST}$$

$$\frac{V_{TEST}}{I_{TEST}} = \frac{1}{18.586m (0.9987)} = 53.87 \Omega$$

$$\therefore R_{SC1} = 3.9k \parallel 53.87 = 53.1 \Omega$$

$$\uparrow_{SC1} = (53.1) C_1$$


2) \uparrow_{SC2} (SHORT C_1, C_3)

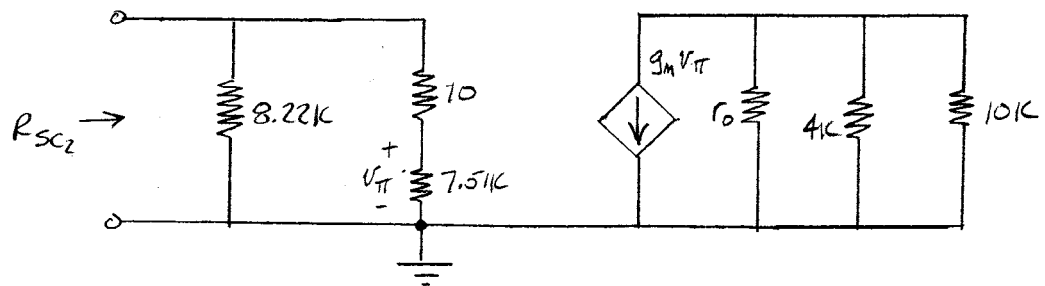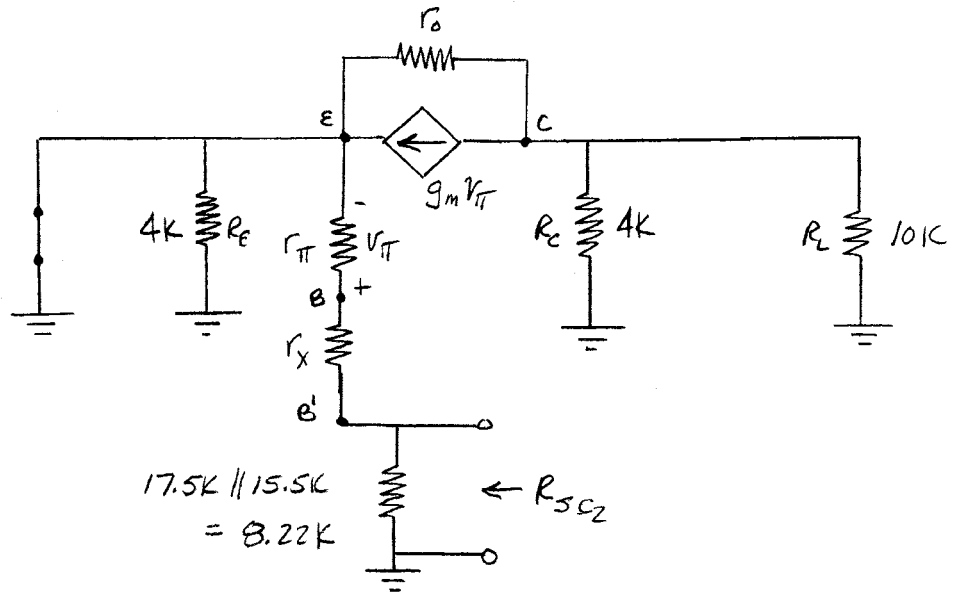


$$R_{SC2} = 8.22k \parallel 7.52k = 3.927k \Omega$$

$$\uparrow_{SC2} = (3.927k) C_2$$

3) \uparrow_{SC3} (SHORT C_1, C_2)

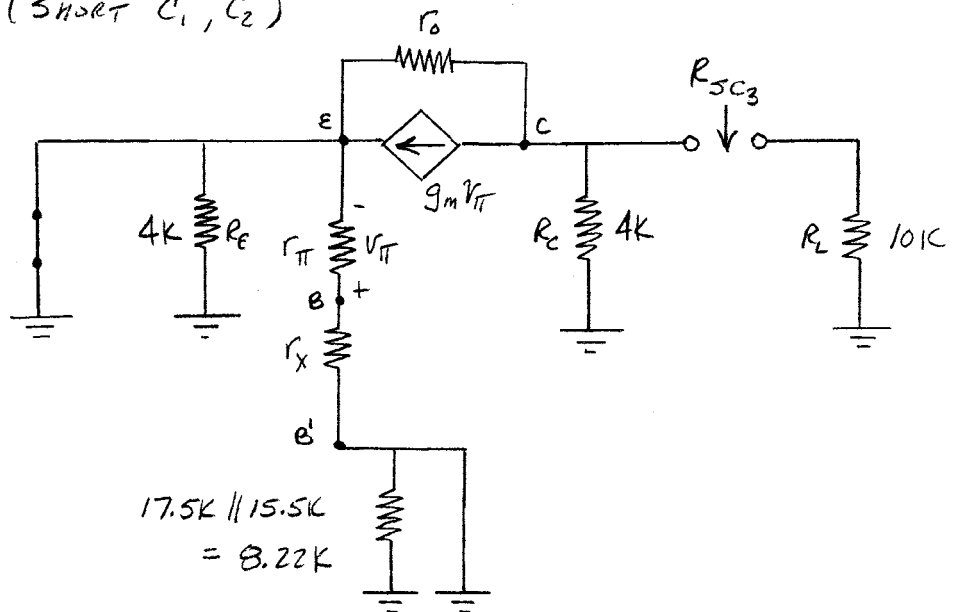

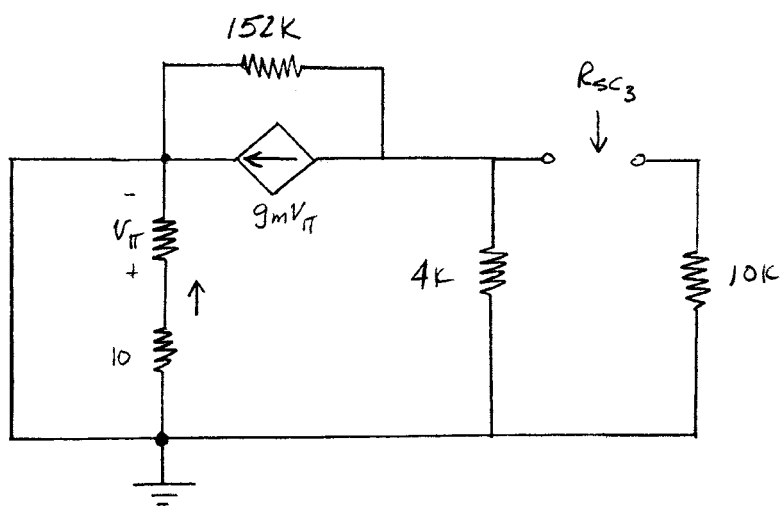

SINCE $10 \left(\frac{V_{\pi}}{R_{\pi}} \right) + V_{\pi} = 0$ THEN $V_{\pi} = 0$

$\therefore R_{sc3} = 152K \parallel 4K + 10K = 13.897K \Omega$

$\uparrow_{sc3} = (13.897K) C_3$

4)
$$W_L = \frac{1}{53.1 C_1} + \frac{1}{(3.927K) C_2} + \frac{1}{(13.897K) C_3}$$

$$= 2\pi (20) = 125.66$$


- WE COULD LET $\frac{1}{\uparrow_{sc1}} = \frac{1}{\uparrow_{sc2}} = \frac{1}{\uparrow_{sc3}} = \frac{125.66}{3}$

THEN $C_1 = 450 \mu F, C_2 = 6.08 \mu F, C_3 = 1.72 \mu F$

OR WE COULD LOWER C_1 (SEE 510.5) WITH LETTING


$\frac{1}{\uparrow_{sc1}} = 0.9 W_L = 113.09 \Rightarrow C_1 = \frac{1}{(53.1)(113.09)} =$	$166.5 \mu F$
$\frac{1}{\uparrow_{sc2}} = 0.05 W_L = 6.283 \Rightarrow C_2 = \frac{1}{(3.927K)(6.283)} =$	$40.5 \mu F$
$\frac{1}{\uparrow_{sc3}} = 0.05 W_L = 6.283 \Rightarrow C_3 = \frac{1}{(13.897K)(6.283)} =$	$11.5 \mu F$

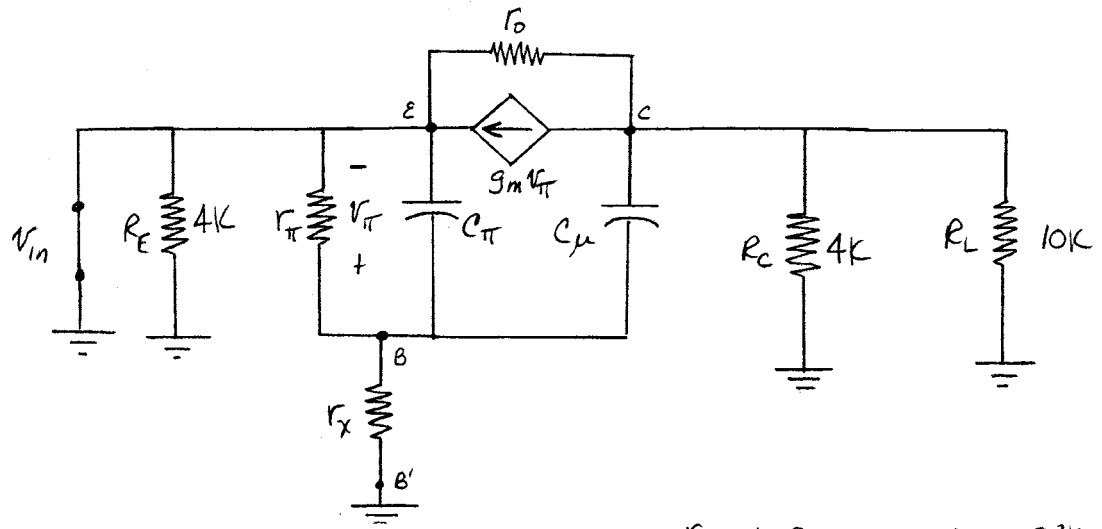C) HIGH FREQ. MODEL WITH V_{in} SHORTED (IGNORE R_c)



- $r_x = 10\Omega$
- $r_{\pi} = 7.51K\Omega$
- $g_m = 13.8mV$
- $r_o = 152K$
- $C_{\pi} = 12pF$
- $C_{\mu} = 3.17pF$


1) \uparrow_{OC_1} (OPEN C_{μ})

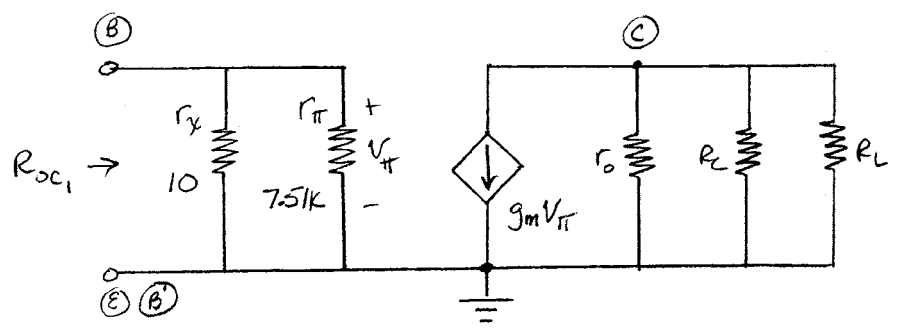

$$R_{oc_1} = 10 \parallel 7.51K = 9.987\Omega$$

$$\begin{aligned} \uparrow_{OC_1} &= C_{\pi} R_{oc_1} = (12p)(9.987) \\ &= 119.84 pSEC \end{aligned}$$

2) \uparrow_{OC2} (OPEN C_{π})

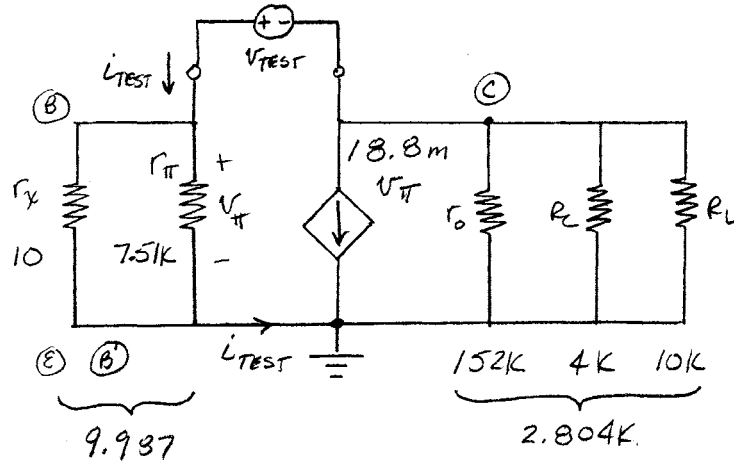

$$V_{TEST} = I_{TEST} (9.987) + 2.804k (I_{TEST} + 18.8m V_{\pi})$$

$$V_{\pi} = I_{TEST} (9.987)$$

$$\begin{aligned} \frac{V_{TEST}}{I_{TEST}} &= R_{OC2} = 9.987 + 2.804k (1 + 18.8m \cdot 9.987) \\ &= 3.34k\Omega \end{aligned}$$

$$\uparrow_{OC2} = C_{\mu} R_{OC2} = (3.17p) (3.34k) = 10.59 n SEC$$

$$\begin{aligned} 3) \quad \omega_H &= \frac{1}{\uparrow_{OC1} + \uparrow_{OC2}} = \frac{1}{119.84p + 10.59n} \\ &= 93.38 M/RAD/SEC \end{aligned}$$

$$f_H = \omega_H / 2\pi$$

$$= \boxed{14.86 MHz}$$


D)

```

CB Amplifier
VCC 5 0 5
R1 5 4 15.5K
R2 4 0 17.5K
RC 5 6 4K
RE 3 0 4K
RS 1 2 50
RL 7 0 10K
C1 2 3 166.5U
C2 6 7 40.5U
CE 4 0 11.5U
VS 1 0 AC 1M
Q1 6 4 3 Q2N3904
.model Q2N3904 NPN(Is=6.734f Xti=3 Eg=1.11 Vaf=74.03
+ Bf=416.4 Ne=1.259 Ise=6.734f Ikf=66.78m Xtb=1.5
+ Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1 Cjc=3.638p Mjc=.3085
+ Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10
.AC DEC 25 1 100MEG
.OP
.PROBE
.END
    
```

CB Amplifier

Temperature: 27.0

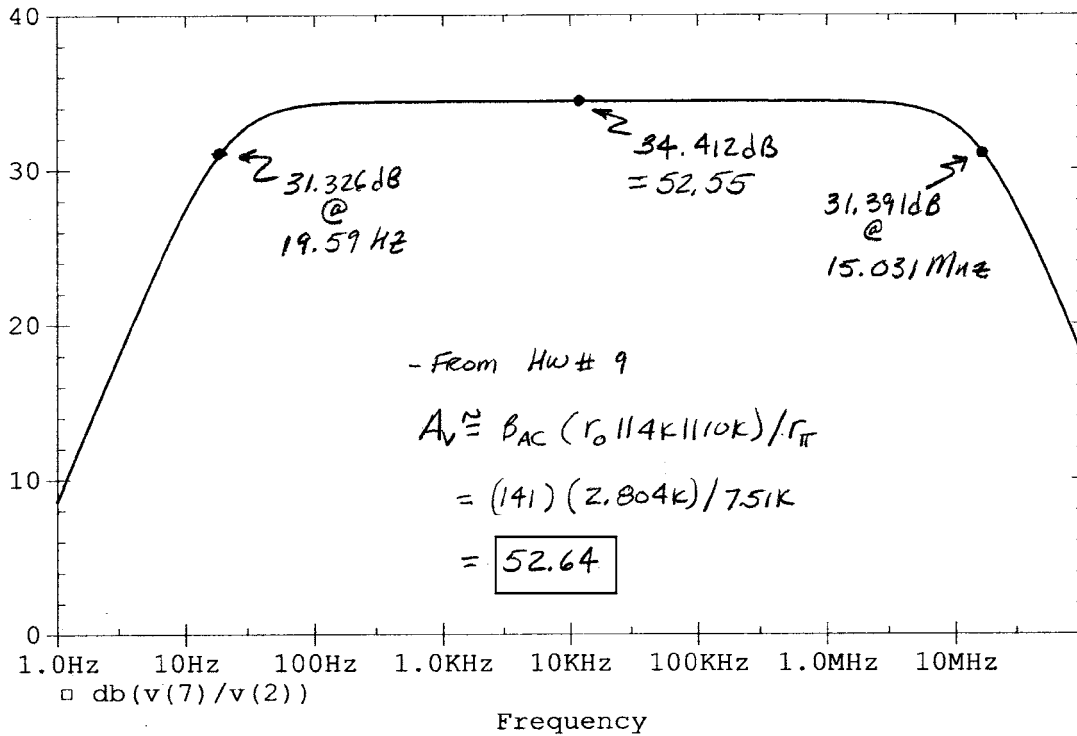

	<u>PSPICE</u>	<u>ESTIMATED</u>	<u>% DIFF</u>
A_v	52.55	52.64	0.171%
f_L	19.59 kHz	20 kHz	2.01%
f_H	15.031 MHz	14.86 MHz	-1.14%