

ECE 302 - HW#9 - SOLUTION - 30 POINTS

A) From TABLE "ON - CHARACTERISTICS" on p.2 for $I_C = 10\text{mA}$ AND $V_{CE} = 1\text{V}$

$$100 \leq \beta_F \leq 300$$

- From FIG. 15 on p6, $\beta_F = 1$ AT $I_C = 10\text{mA}$, $V_{CE} = 1\text{V}$
AND β_F FOR 0.5mA IS BETWEEN 0.6 AND 0.7
ON A LOG SCALE.

- THE 0.5mA CURVE IS 3.2cm OUT OF 3.9cm.
ON A 1-10 LOG SCALE THIS IS $10^{3.2/3.9} = 6.61$.
SO ON A 0.1 - 1. SCALE THIS IS 0.661

$$\therefore 100(0.661) \leq \beta_F \leq 300(0.661)$$


$$66.1 \leq \beta_F < 198.3$$

B) SINCE $V_{CE} = 1$ AND $V_{CC} = 5$, LET $V_{RC} = V_{RE} = 2\text{V}$
THEN $R_C \cong R_E = 2/0.5\text{m} = 4\text{K}\Omega$. $I_{B(\text{MAX})} = I_C / \beta_{F(\text{MIN})}$
 $= 0.5\text{m} / 66.1 = 7.56\mu\text{A}$. LET $I_{R_1} \cong I_{R_2} = 20(7.56\mu)$
 $= 151.3\mu\text{A}$. THEN (SEE CH 3 p40)

$$R_2 = \frac{V_B}{I_{R_2}} = \frac{2 + 0.65}{151.3\mu} = 17.5\text{K}\Omega$$


$$R_1 = \frac{V_{CC} - V_B}{I_{R_1}} = \frac{5 - 2.65}{151.3\mu} = 15.5\text{K}\Omega$$

c) Common - BASE AMPLIFIER

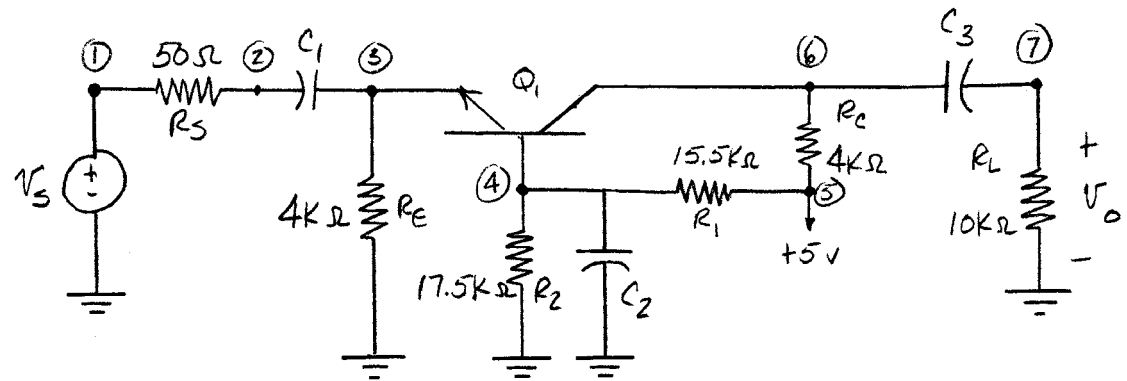

FOR Q_1 : $V_{BE(on)} = 0.65V$, $\beta_F = \frac{66.1 + 198.3}{2} = 132.2$, $\alpha_F = 1$

- STEP 1 : DC OPERATING POINT

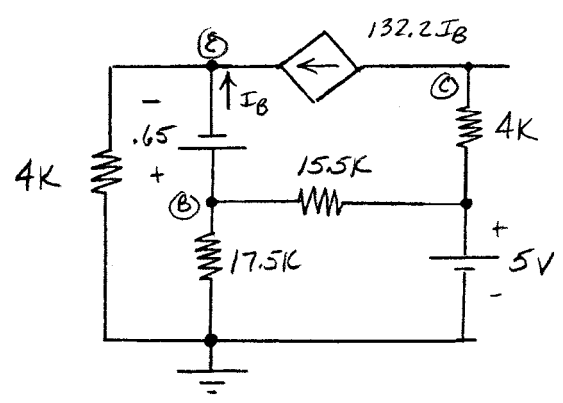


$$V_{Th} = 5 \frac{17.5K}{15.5K + 17.5K}$$

$$= 2.65V$$

$$R_{Th} = 15.5K || 17.5K$$

$$= 8.22K$$

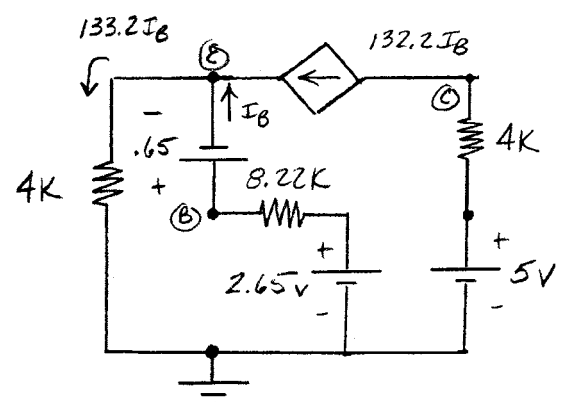

$$2.65 = 8.22K I_B + 0.65 + 4K(133.2 I_B)$$

$$\therefore I_B = \frac{2.65 - 0.65}{8.22K + 4K(133.2)} = 3.7 \mu A \quad \checkmark$$

$$I_C = 132.2 (3.7 \mu) = 488.7 \mu A$$

$$V_{CE} = 5 - (488.7 \mu) 4K - (133.2)(3.7 \mu) 4K = 1.07V \quad \checkmark$$


- ASSUMPTION CHECKS,

- STEP 2 : AC MODEL

$$r_{\pi} = \frac{\pi F V_T}{I_B} = \frac{26m}{3.7 \mu} = 7.03K \Omega$$

$$\beta_F = 132.2$$

- STEP 3 : AC MID-BAND ANALYSIS

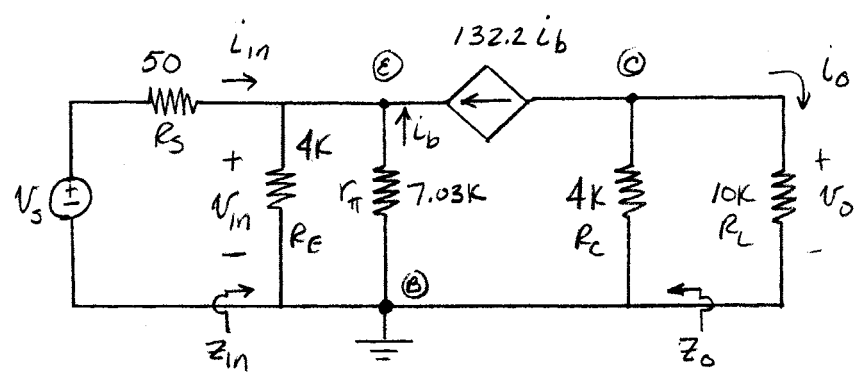

1) A_V

$$V_o = -132.2 I_b (4K \parallel 10K) = -377.7 I_b$$

$$I_b = -V_{in} / 7.03K$$

$$V_o = -377.7 \left(\frac{-V_{in}}{7.03K} \right) = 53.7 V_{in}$$

$$A_V = \frac{V_o}{V_{in}} = \boxed{53.7}$$

2) Z_{in}

$$i_{in} = \frac{v_{in}}{4k} - i_b - 132.2i_b = \frac{v_{in}}{4k} + 133.2 \frac{v_{in}}{7.03k}$$

$$= v_{in} \left[\frac{1}{4k} + \frac{133.2}{7.03k} \right]$$

$$\frac{v_{in}}{i_{in}} = Z_{in} = \frac{1}{\frac{1}{4k} + \frac{133.2}{7.03k}} = 4k \parallel \frac{7.03k}{133.2}$$

$$= 4k \parallel 52.8\Omega = \boxed{52.1\Omega}$$

3) A_I

$$A_I = A_V \frac{Z_{in}}{R_L} = 53.7 \frac{52.1}{10k} = .2798 = \boxed{279.8m}$$

4) G

$$G = A_V A_I = (53.7)(0.2798) = \boxed{15.02}$$

5) Z_o (SEE CH5, p21)

$$Z_o = R_c = \boxed{4k\Omega}$$