

NAME SOLUTION

ECE 831

EXAM III

Nov. 19, '08

<u>PROBLEM</u>	<u>POINTS</u>	<u>SCORE</u>
1	25	_____
2	25	_____
3	25	_____
4	25	_____
	<u>100</u>	<u>_____</u>

1) GIVEN $\rightarrow = Hs + \frac{K_0}{s} + \sum \frac{(2K_i)s}{s^2 + \omega_i^2}$

$$Z_{LC}(s) = \frac{48s^4 + 20s^2 + 1}{3s(8s^2 + 1)} = \frac{48s^4 + 20s^2 + 1}{24s(s^2 + 1/8)}$$

FIND A 1ST FOSTER LC ONE PORT. SKETCH YOUR CIRCUIT. LABEL ELEMENT VALUES


$$H = \frac{Z_{LC}}{s} \Big|_{s \rightarrow \infty} = \frac{48s^4}{24s^4} = \frac{48}{24} = 2$$

$$K_0 = s Z_{LC} \Big|_{s \rightarrow 0} = \frac{1}{24(1/8)} = \frac{1}{3}$$

$$\begin{aligned} 2K_i &= \frac{s^2 + 1/8}{s} \frac{48s^4 + 20s^2 + 1}{24s(s^2 + 1/8)} \Big|_{s^2 = -1/8} \\ &= \frac{48(\frac{1}{64}) + 20(-\frac{1}{8}) + 1}{24(-1/8)} = \frac{48 - 20(8) + 64}{24(-8)} \\ &= \frac{-48}{-24(8)} = \frac{2}{8} = \frac{1}{4} \end{aligned}$$

$$Z_i = \frac{\frac{1}{4}s}{s^2 + 1/8} = \frac{1}{\frac{4}{3}s^2 + \frac{4}{3}\frac{1}{8}} = \frac{1}{4s + \frac{1}{2s}}$$
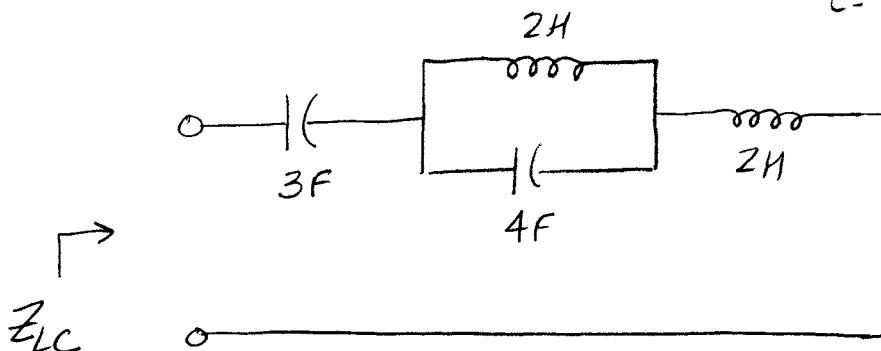
$$C = \frac{1}{2K_i} \quad \frac{2K_i}{\omega_i^2} = L$$




-3PT/ERROR

2) GIVEN


$$Z_{RC}(s) = \frac{24s + 7}{24s^2 + 15s + 1}$$

FIND A 1ST ORDER RC ONE PORT. SKETCH YOUR CIRCUIT. LABEL ELEMENT VALUES

$$\begin{array}{r}
 0 \Rightarrow R_1 = 0 \Omega \\
 24s^2 + 15s + 1 \overline{) 24s + 7} \quad 5 \Rightarrow C_2 = 1F \\
 \underline{24s + 7} \quad 24s^2 + 15s + 1 \\
 \quad \quad \quad \underline{24s^2 + 7s} \quad 3 \Rightarrow R_3 = 3\Omega \\
 \quad \quad \quad \quad \quad \quad \quad \quad 8s + 1 \overline{) 24s + 7} \\
 \quad \quad \quad \quad \quad \quad \quad \quad \underline{24s + 3} \quad 2s \Rightarrow C_4 = 2F \\
 \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad 4 \overline{) 8s + 1} \\
 \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \underline{8s} \quad 4 \Rightarrow R_5 = 4\Omega \\
 \quad 1 \overline{) 4}
 \end{array}$$

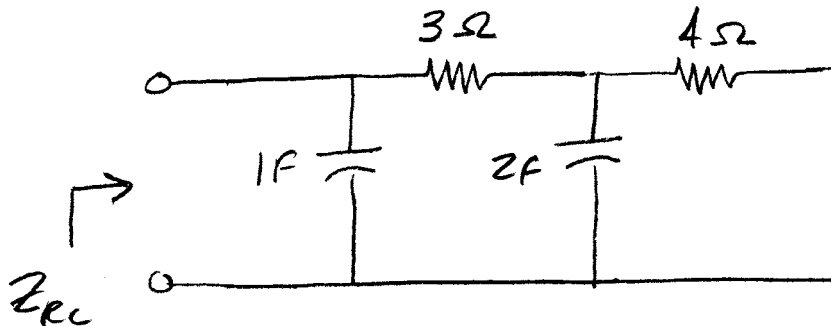

- 4 pt / Error

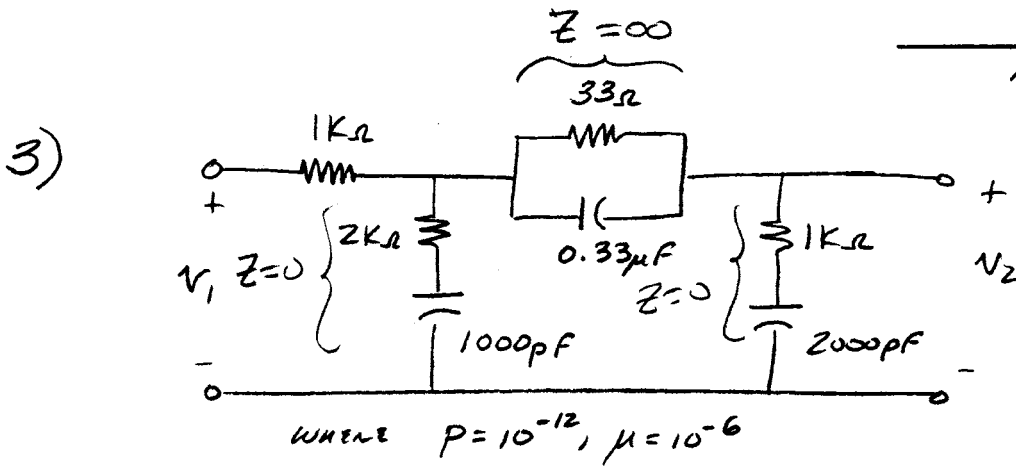


6) A) FIND THE TRANSMISSION ZEROS OF $\frac{V_2}{V_1}$. MARK THE LOCATION ON THE GRAPH BELOW


$$\frac{1}{s \cdot 1000p} = -2K \Rightarrow s = -\frac{1}{(1n)(2K)} = -500K \text{ RAD/SEC}$$

$$\frac{1}{s \cdot .33\mu} = -33 \Rightarrow s = -\frac{1}{(.33\mu)33} = -91.8K \text{ RAD/SEC}$$
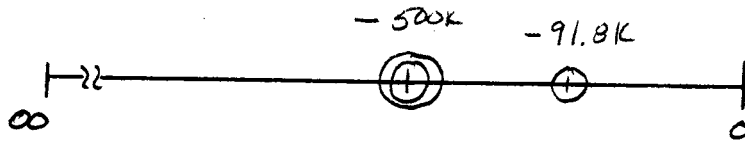
$$\frac{1}{s \cdot 2000p} = -1K \Rightarrow s = -\frac{1}{(2n)(1K)} = -500K \text{ RAD/SEC}$$




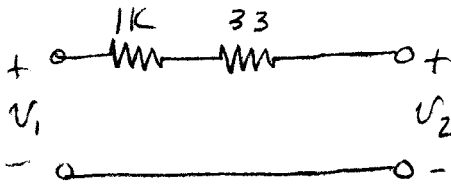B) WHAT IS $\frac{V_2}{V_1}$ AT $s=0$? OPEN C'S



$$\left. \frac{V_2}{V_1} \right|_{s=0} = \underline{\underline{1}} \quad (10)$$

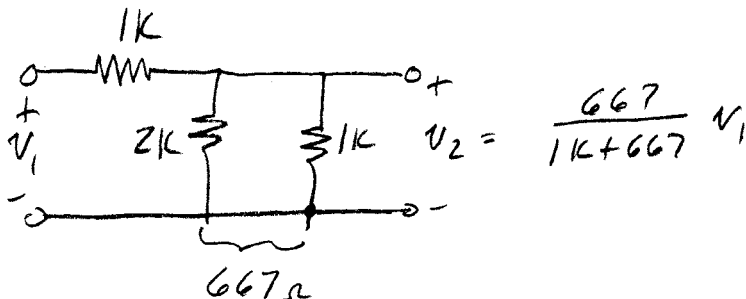C) WHAT IS $\frac{V_2}{V_1}$ AT $s=\infty$ SHORT C'S




$$\left. \frac{V_2}{V_1} \right|_{s=\infty} = \underline{\underline{0.4}} \quad (9)$$

4) GIVEN

$$G_{12} = \frac{V_2}{V_1} = K \frac{3s^2 + 1}{3s^2 + 3s + 1} = \frac{K \frac{3s^2 + 1}{3s}}{\frac{3s^2 + 1}{3s} + 1} = \frac{-y_{21}}{y_{22} + Y_2}$$

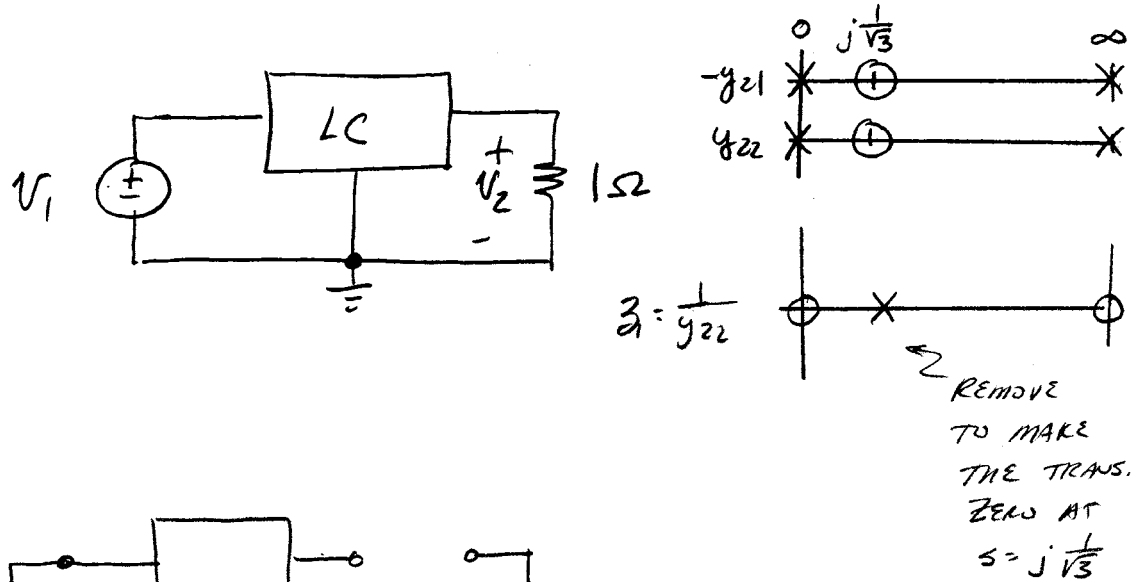A) SYNTHESIZE THE LC CIRCUIT USING OUR 2-PORT TECHNIQUE
 SKETCH YOUR FINAL CIRCUIT WITH ELEMENT VALUES.




$$Z_1 = \frac{1}{y_{22}} = \frac{3s}{3s^2 + 1} = \frac{1}{\frac{3s^2}{3s} + \frac{1}{3s}}$$

$$= \frac{1}{1s + \frac{1}{3s}}$$

\uparrow \uparrow
 $C=1F$ $L=3H$


4) ADDITIONAL WORK SPACE

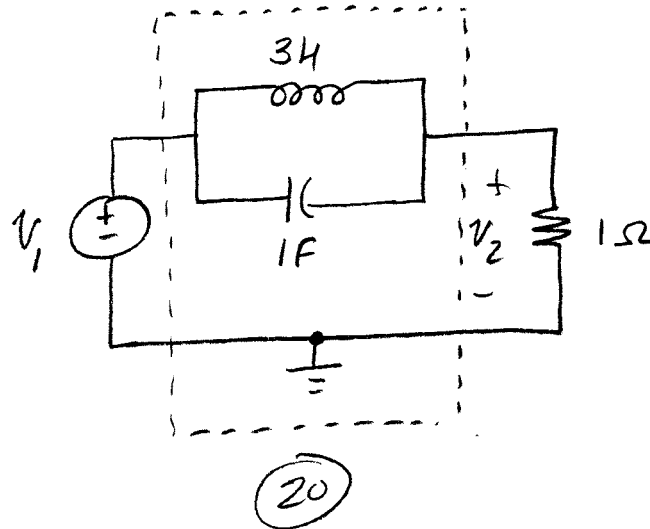

B) DETERMINE THE VALUE OF K

$$\frac{V_2}{V_1} = K \frac{3s^2 + 1}{3s^2 + 3s + 1} \Big|_{s=0} = K \frac{1}{1}$$

CIRCUIT AT $s=0$

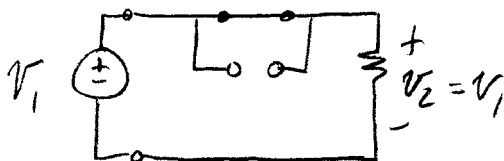

$K = \underline{\quad 1 \quad}$ (5)