



Memory Basics

- **RAM: Random Access Memory**
 - historically defined as memory array with individual bit access
 - refers to memory with **both Read and Write capabilities**
- **ROM: Read Only Memory**
 - no capabilities for "online" memory Write operations
 - Write typically requires high voltages or erasing by UV light
- **Volatility of Memory**
 - volatile memory loses data over time or when power is removed
 - RAM is volatile
 - non-volatile memory stores data even when power is removed
 - ROM is non-volatile
- **Static vs. Dynamic Memory**
 - Static: holds data as long as power is applied (SRAM)
 - Dynamic: will lose data unless refreshed periodically (DRAM)




SRAM/DRAM Basics

- **SRAM: Static Random Access Memory**
 - **Static**: holds data as long as power is applied
 - **Volatile**: can not hold data if power is removed
 - 3 Operation States: hold, write, read
 - Basic 6T (6 transistor) SRAM Cell
 - bistable (cross-coupled) INVs for storage
 - access transistors MAL & MAR
 - word line, WL, controls access
 - WL = 0 (hold) = 1 (read/write)
- **DRAM: Dynamic Random Access Memory**
 - **Dynamic**: must be refreshed periodically
 - **Volatile**: loses data when power is removed
 - 1T DRAM Cell
 - single access transistor; storage capacitor
 - control input: word line (WL); data I/O: bit line
- **DRAM to SRAM Comparison**
 - DRAM is smaller & less expensive per bit
 - SRAM is faster
 - DRAM requires more peripheral circuitry

  

ROM/PROM Basics

- **ROM: Read Only Memory**
 - no capabilities for "online" memory Write operations
 - data programmed
 - during fabrication: **ROM**
 - with high voltages: **PROM**
 - by control logic: **PLA**
 - **Non-volatile**: data stored even when power is removed
- **PROM: Programmable Read Only Memory**
 - programmable by user -using special program tools/modes
 - read only memory -during normal use
 - non-volatile
 - Read Operation
 - like any ROM: address bits select output bit combinations
 - Write Operation
 - typically requires high voltage (~15V) control inputs to set data
 - stores charge to floating gate (see figure) to set to Hi or Low
 - Erase Operation
 - to change data
 - **EPROM**: erasable PROM: uses UV light to reset all bits
 - **EEPROM**: electrically-erasable PROM, erase with control voltage

 

EPROM device structure



Comparison of Memory Types

- **DRAM**
 - very high density → cheap data cache in computers
 - must be periodically refreshed → slower than SRAM
 - volatile; no good for program (long term) storage
- **SRAM (basically a Latch)**
 - fastest type of memory
 - low density → more expensive
 - generally used in small amounts (L2 cache) or expensive servers
- **EEPROM**
 - slow/complex to write → not good for fast cache
 - non-volatile; best choice for program memory
- **ROM**
 - hardware coded data; rarely used except for bootup code
- **Register (flip flop)**
 - functionally similar to SRAM but less dense (and thus more expensive)
 - reserved for data manipulation applications



Memory Arrays

- $N \times n$ array of 1-bit cells
 - n = byte "width"; 8, 16, 32, etc.
 - N = number of bytes = "length"
 - m = number of address bits
 - $\max N = 2^m$



Memory "size":

bytes = N , # bits = $N \times n$

 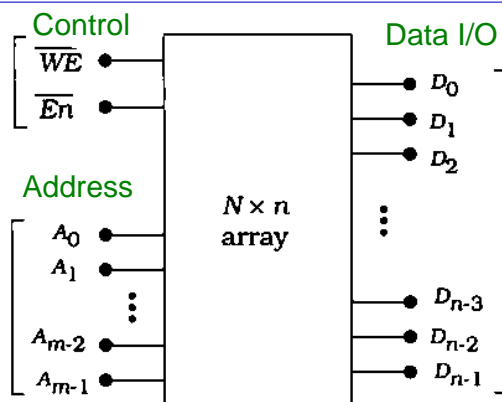Example:



1k x 8 RAM \rightarrow 10 addr lines, 8-bit bytes
 $2^{10} = 1k$ (1024) mem locations = length
 width = 8-bit, size = 1k-byte, 8k-bits

- Array I/O
 - data (in and out)
 - $D_{n-1} - D_0$
 - address
 - $A_{m-1} - A_0$
 - control
 - varies with design
 - WE = write enable (assert low)
 - WE=1=read, WE=0=write
 - En = block enable (assert low)
 - used as chip enable (CE) for an SRAM chip




Memory Array Addressing

 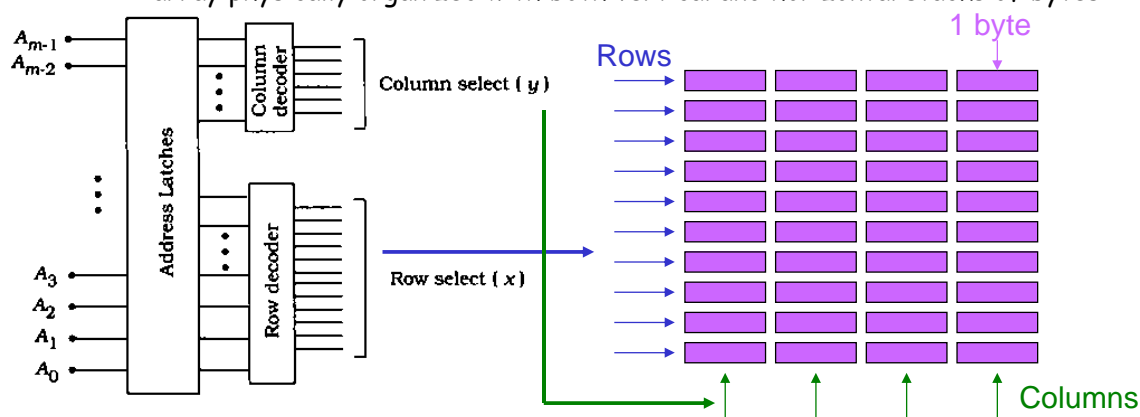- Standard Memory Addressing Scheme
 - m address bits are divided into x row bits and y column bits ($x+y=m$)
 - address bits are encoded so that $2^m = N$
 - array physically organized with both vertical and horizontal stacks of bytes





 Example byte:
 one word in an 8b-wide EPROM





Typical Memory Chip


- Data
 - x-bits in parallel, typically $x = 8, 16$
- Address signals
 - m address signals $\rightarrow M=2^m$ addresses
- Control signals
 - **/WE: write enable** - when activated, values on data lines are written to specified address
 - **/OE: output enable** - data at specified location placed on data pins of memory chip, data lines connected to data bus using tristate outputs
 - **/CS: chip select** - selects a specific chip in an array of memory chips
- Connection to HC12 ----->

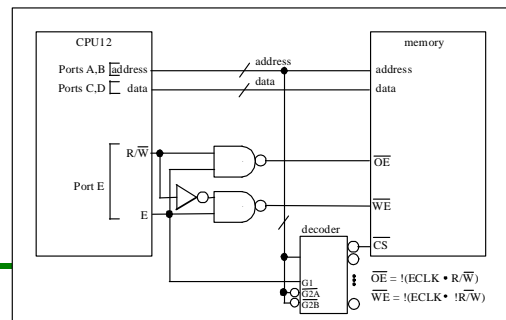 

Memory Expansion expanding memory length

 
 


Memory Expansion expanding memory width

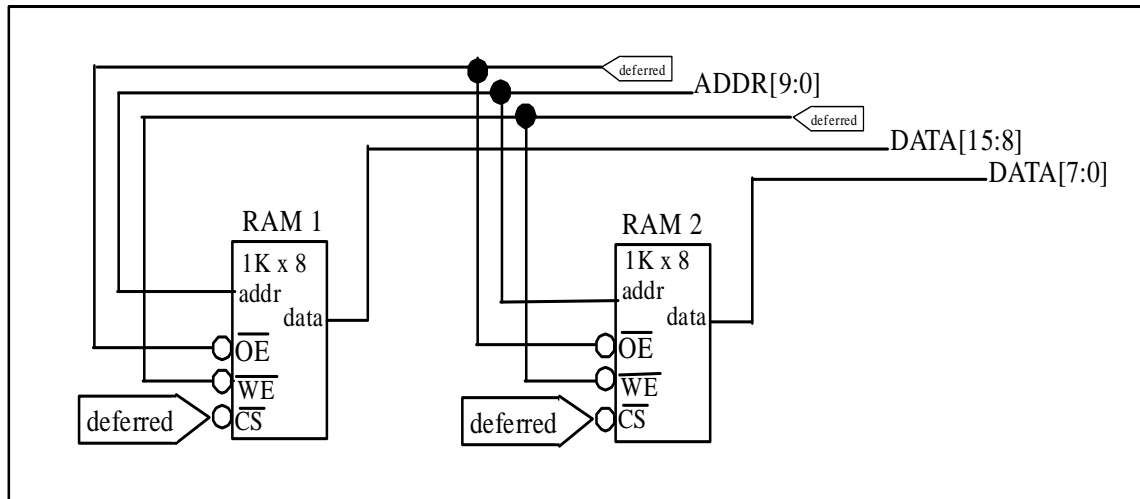

Memory Overview.9

 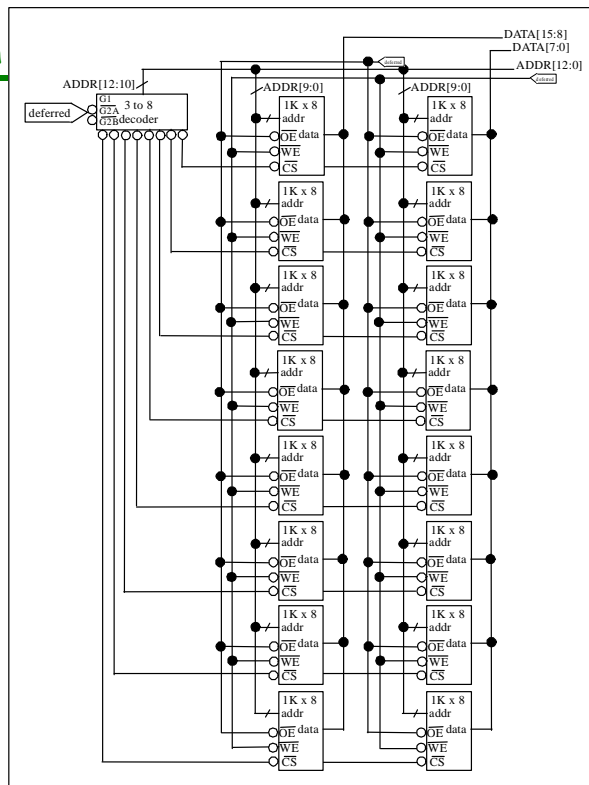Memory Expansion expanding memory length and width



Memory Overview.10